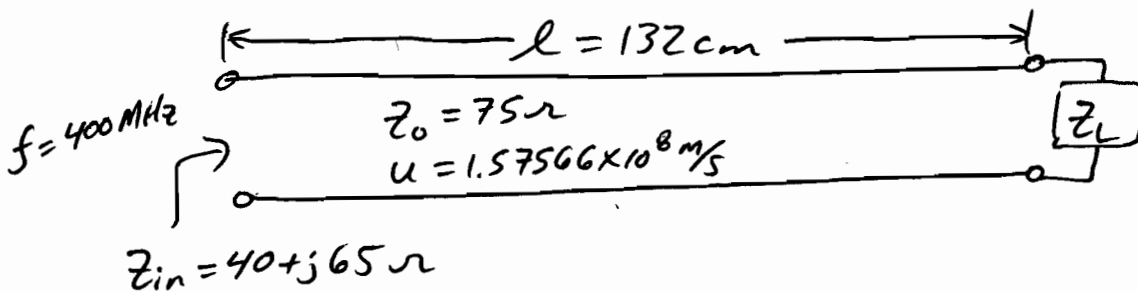


11.37 A 75Ω lossless transmission line is 132 cm long, with a dielectric constant $\epsilon_r = 3.62$. If the line operates at 400 MHz with an input impedance of $Z_{in} = 40 + j65 \Omega$, use the Smith chart to determine the terminating load.

$$u = \frac{c}{\sqrt{\epsilon_r}} = \frac{2.9979 \times 10^8 \text{ m/s}}{\sqrt{3.62}} = 1.57566 \times 10^8 \text{ m/s}$$

$$\lambda = \frac{u}{f} = \frac{1.57566 \times 10^8}{400 \times 10^6} = 0.393915315 \text{ m}$$

$$\frac{l}{\lambda} = \frac{132 \times 10^{-2}}{0.3939} = 3.351 \rightarrow \underline{0.351 \lambda = l}$$



* Normalize Z_{in} to 75Ω line $\gamma_{in} = \frac{40 + j65}{75} = 0.5\bar{3} + j0.8\bar{6} \Omega$

and plot on Smith Chart

* Move $l = 3.351 \lambda$ or 0.351λ from γ_{in} "WAVELENGTHS TOWARD LOAD" on circle of constant $|\Gamma|$ to arrive at $\gamma_L = 2.75 - j1.4 \Omega$

$$Z_L = \gamma_L Z_0 = (2.75 - j1.4) 75$$

$$\underline{\underline{Z_L = 206.25 - j105 \Omega}}$$

(Analytic soln $Z_L = 204.6 - j105.3 \Omega$)

$l = 3.351\lambda$

$Y_{in} = 0.53 + j0.867 \text{ } \Omega^{-1}$

$Z_L = 2.75 - j1.4 \text{ } \Omega$

Simple
Smith Chart

Problem 11.37

$Z_0 = 75 \Omega$

$f = 400 \text{ MHz}$

$u = \frac{c}{\sqrt{3.62}}$

