

11.39 A lossless 50Ω line is terminated by a load $Z_L = 75 + j60 \Omega$. Using a Smith chart, determine (a) the reflection coefficient Γ , (b) the standing wave ratio s , (c) the input impedance at 0.2λ from the load, (d) the location of the first minimum voltage from the load, (e) the shortest distance from the load at which the input impedance is purely resistive.

a) * Normalize Z_L to $50 \Omega \Rightarrow y_L = \frac{75 + j60 \Omega}{50 \Omega} = 1.5 + j1.2 \text{ } \Omega$

* Plot y_L on Smith Chart, use compass or straight edge to find distance from center of Smith Chart to y_L and "REFL. COEFF, V or I" scale to get

$$|\Gamma_L| = 0.47$$

* Draw radial line from center thru y_L to get

$$\angle \Gamma_L = +41.7^\circ \Rightarrow \underline{\underline{\Gamma_L = 0.47 \angle +41.7^\circ}}$$

b) Use compass & draw arc on SWR (VSWR) scale @ bottom. Read VSWR = S = 2.75

c) Use compass to draw circle of radius $|\Gamma| = 0.47$
Move 0.2λ "WAVELENGTHS TOWARD GENERATOR"
from y_L to $y_{in} = 0.55 - j0.65 \text{ } \Omega$

$$Z_{in} = 50(0.55 - j0.65) = \underline{\underline{27.5 - j32.5 \Omega}}$$

d) Plot $r_{min} = 1/S = 0.364$. Using "WAVELENGTHS TOWARD GENERATOR" scale $l_{min} = 0.5\lambda - 0.192\lambda$

$$\underline{\underline{l_{min} = 0.308\lambda}}$$

e) Plot $r_{max} = S = 2.75$. (Closest)

Use "WAVELENGTHS TOWARD GENERATOR"

$$l_{max} = 0.25\lambda - 0.192\lambda$$

$$\underline{\underline{l_{max} = 0.058\lambda}}$$

Simple Smith Chart

Problem 11.39
 $Z_0 = 50 \Omega$

