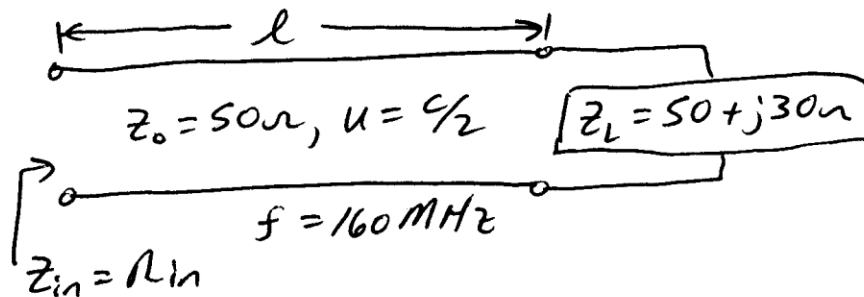


- 11.42 A 50Ω transmission line operates at 160 MHz and is terminated by a load of $50 + j30 \Omega$. If its wave speed is $c/2$ and the input impedance is to be made real, calculate the minimum possible length of the line and the corresponding input impedance.



- * Normalize the load impedance $z_L = \frac{z_L}{z_0} = \frac{50 + j30}{50}$
and plot on Smith Chart $z_L = 1 + j0.6 \frac{\Omega}{\Omega}$

- * Draw arc w/compass starting @ z_L in the "WAVELENGTHS TOWARD Generator" direction until it intersects horizontal/real axis.

- * Read $r_{in} = r_{max} = 1.8 \frac{\Omega}{\Omega} \Rightarrow z_{in} = r_{in} z_0 = 1.8(50)$
 $z_{in} = 90 \Omega$

- * Draw radial line through z_L and read off 0.1485λ on the "WAVELENGTHS TOWARD GENERATOR" Scale. Note that $r_{in} = r_{max}$ is at 0.25λ on this scale.

$$l = (0.25 - 0.1485) \lambda = 0.1015 \lambda$$

$$= 0.1015 \left(\frac{2.9979 \times 10^8 / 2}{160 \times 10^6} \right)$$

$$\underline{\underline{l = 0.0951 \text{ m} = 9.51 \text{ cm}}}$$

11.42

Simple Smith Chart

$Z_0 = 50 \Omega$, $u = \frac{1}{2}$
 $f = 160 \text{ MHz}$

