

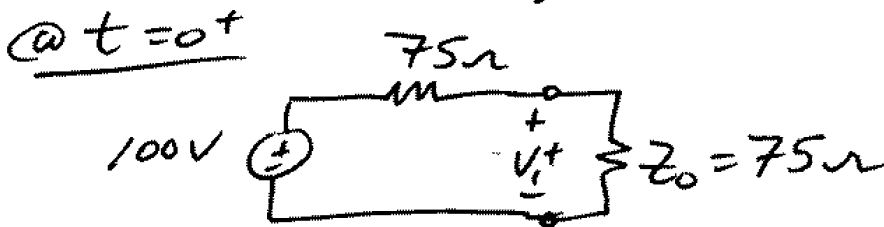


A TDR that has an open circuit voltage of $100 u(t)$ V and a Thevenin resistance of 75Ω is connected to a length of lossless transmission line ($Z_0 = 75 \Omega$, $u = 2.3 \times 10^8$ m/s) of unknown length with an unknown resistive load. At the TDR terminals, what voltage would initially be measured? If the voltage measured at the TDR terminals changes to 35 V at $1.2 \mu\text{s}$, what is the length of the cable and the load resistance?

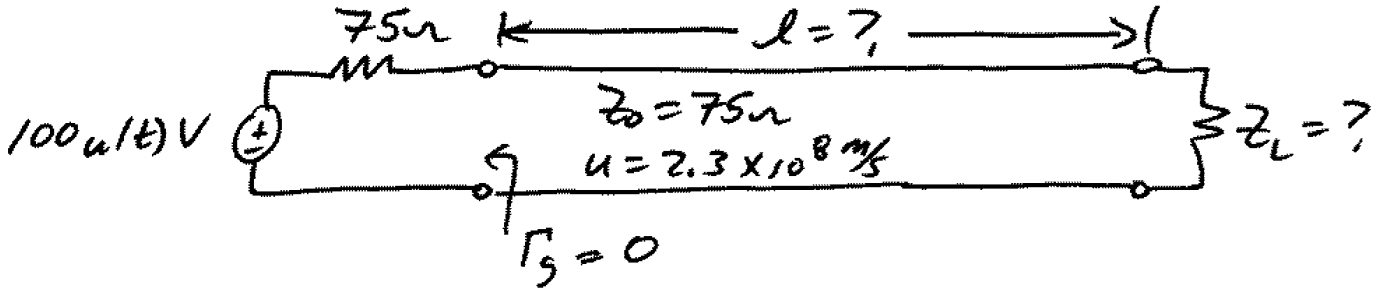
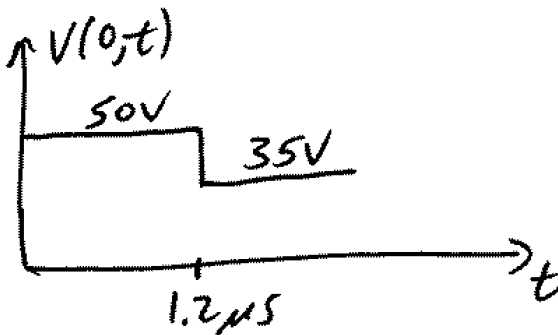
$$V_{init} = V_i^+ = (100 \text{ V}) \frac{75}{75+75} = \underline{\underline{50 \text{ V}}}$$




$$2T = 1.2 \mu\text{s}$$

$$T = 0.6 \mu\text{s} = \frac{l}{u}$$

$$l = 0.6 \mu\text{s} (2.3 \times 10^8 \text{ m/s})$$
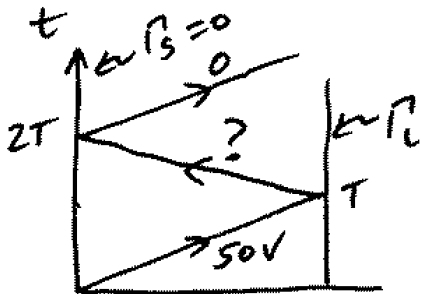
$$\underline{\underline{l = 138 \text{ m}}}$$



$$35 \text{ V} = 50 \text{ V} + \Gamma_L (50 \text{ V}) + 0(\Gamma_L)(50 \text{ V}) \Rightarrow \Gamma_L = \frac{35-50}{50} = -0.3$$

$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} = 75 \frac{1 - 0.3}{1 - (-0.3)} = \underline{\underline{40.3846 \Omega}}$$