

An RG-6 coaxial transmission line has the following parameters/specifications at 700 MHz: $L = 0.093 \mu\text{H}/\text{ft}$, $C = 16.5 \text{ pF}/\text{ft}$, $u = 0.82074c$, and $\alpha = 6.6 \text{ dB}/100\text{ft}$. (a) Determine the propagation constant, conductance per-unit-length and characteristic impedance of the transmission line if $R = 0.9 \Omega/\text{ft}$. (b) If a 3.6 m length of this line is terminated with a $145 + j30 \Omega$ load and is driven by a source where $v_g(t) = 100\cos(\omega t) \text{ V}$ and $Z_g = 75 + j5 \Omega$, determine the input impedance, input reflection coefficient, input voltage, input current, and time-average power delivered to the line. (c) Also, find the load voltage, load current, and time-average power delivered to the load. (d) How much power was dissipated in the transmission line? What fraction of the input power was delivered to the load? What fraction was lost in the transmission line?


Given:

$$\begin{aligned} \mu_0 &:= 4 \cdot \pi \cdot 10^{-7} \text{ H/m} & \epsilon_0 &:= 8.8541878 \cdot 10^{-12} \text{ F/m} & c &:= \frac{1}{\sqrt{\epsilon_0 \cdot \mu_0}} \\ f &:= 700 \cdot 10^6 \text{ Hz} & u &:= 0.82074 \cdot c & \alpha &:= \frac{6.6}{100 \cdot 0.3048 \cdot (20 \cdot \log(e))} \\ \underline{R} &:= \frac{0.9}{0.3048} \text{ } \Omega/\text{m} & \underline{L} &:= \frac{0.093 \cdot 10^{-6}}{0.3048} \text{ H/m} & \underline{C} &:= \frac{16.5 \cdot 10^{-12}}{0.3048} \text{ F/m} \end{aligned}$$

a) Propagation constant, conductance per unit length, & characteristic impedance

$$\begin{aligned} \omega &:= 2 \cdot \pi \cdot f & \beta &:= \frac{\omega}{u} & \underline{\alpha} &= 0.02493 \text{ np/m} & \underline{\beta} &= 17.87523 \text{ rad/m} \\ \gamma &:= \alpha + j \cdot \beta & & & \underline{\gamma} &= 0.02493 + 17.87523i \text{ 1/m} \\ \underline{G} &:= \text{Re} \left(\frac{\gamma^2}{R + j \cdot \omega \cdot L} \right) & & & \underline{G} &= 1.40238 \times 10^{-4} \text{ S/m} \\ Z_0 &:= \sqrt{\frac{(R + j \cdot \omega \cdot L)}{(G + j \cdot \omega \cdot C)}} & & & \underline{Z_0} &= 75.07578 - 0.06048i \text{ } \Omega \\ |Z_0| &= 75.0758 \text{ } \Omega & \arg(Z_0) \cdot \frac{180}{\pi} &= -0.0462 \text{ deg} \end{aligned}$$

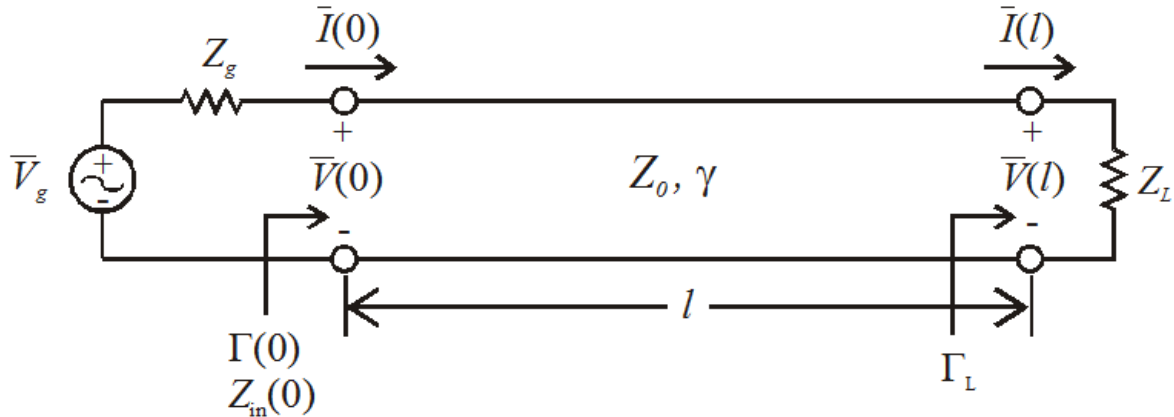b) Input impedance, reflection coefficient, voltage, current, time-average power delivered to the line.



$$V_g := 100 \cdot e^{j \cdot 0} \text{ V} \quad Z_g := 75 + j \cdot 5 \text{ } \Omega \quad Z_L := 145 + j \cdot 30 \text{ } \Omega \quad l := 3.6 \text{ m}$$

$$\Gamma_L := \frac{Z_L - Z_0}{Z_L + Z_0} \quad |\Gamma_L| = 0.34269 \quad \arg(\Gamma_L) \cdot \frac{180}{\pi} = 15.5158 \text{ deg}$$

$$\Gamma_0 := \Gamma_L \cdot e^{-2 \cdot \gamma \cdot l} \quad |\Gamma_0| = 0.28638 \quad \arg(\Gamma_0) \cdot \frac{180}{\pi} = -158.5453 \text{ deg}$$

$$Z_{in0} := Z_0 \cdot \frac{(1 + \Gamma_0)}{(1 - \Gamma_0)} \quad Z_{in0} = 42.66374 - 9.77265i \text{ } \Omega$$

$$|Z_{in0}| = 43.7687 \text{ } \Omega \quad \arg(Z_{in0}) \cdot \frac{180}{\pi} = -12.90172 \text{ deg}$$

$$I_0 := \frac{V_g}{Z_g + Z_{in0}} \quad |I_0| = 0.8492 \text{ A} \quad \arg(I_0) \cdot \frac{180}{\pi} = 2.3227 \text{ deg}$$

$$V_0 := \frac{V_g \cdot Z_{in0}}{Z_g + Z_{in0}} \quad |V_0| = 37.1676 \text{ V} \quad \arg(V_0) \cdot \frac{180}{\pi} = -10.579 \text{ deg}$$

$$\text{Power into trans. line} \quad P_0 := 0.5 \cdot \text{Re}(V_0 \cdot \bar{I}_0) \quad P_0 = 15.3826 \text{ W}$$

c) Load voltage, current, time-average power delivered to the load.

$$V0_fwd := \frac{V0}{1 + \Gamma0} \qquad V0_fwd = 50.11923 - 2.14556i \quad \text{V}$$

$$VL := V0_fwd \cdot e^{-\gamma \cdot l} \cdot (1 + \Gamma L) \quad \underline{|VL| = 61.1464 \quad \text{V}} \quad \underline{\arg(VL) \cdot \frac{180}{\pi} = -85.54 \quad \text{deg}}$$

$$IL := \frac{V0_fwd}{Z0} \cdot e^{-\gamma \cdot l} \cdot (1 - \Gamma L) \quad \underline{|IL| = 0.413 \quad \text{A}} \quad \underline{\arg(IL) \cdot \frac{180}{\pi} = -97.229 \quad \text{deg}}$$

$$\text{Power delivered to load-} \qquad PL := 0.5 \cdot \text{Re}(VL \cdot \overline{IL}) \qquad \underline{PL = 12.3635 \quad \text{W}}$$

d) Power lost in transmission line, %delivered to the load, and % lost in line.

$$Plost := P0 - PL \qquad \underline{Plost = 3.0191 \quad \text{W}}$$

$$\text{Power_delivered_fraction} := \frac{PL}{P0} \cdot 100 \qquad \underline{\text{Power delivered fraction} = 80.373 \quad \%}$$