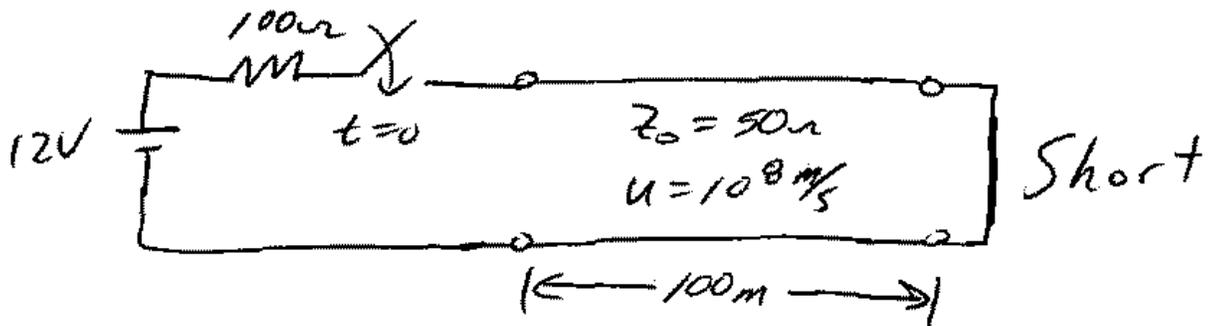


PE 11.8 Repeat Example 11.8 if the transmission line is (a) **Short-circuited**.

- Also, find steady-state currents and voltages at input and load.

ex. 11.8



plot voltage and current at load and generator ends for $0 < t < 6\mu\text{s}$

$$\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0} = \frac{100\Omega - 50\Omega}{100\Omega + 50\Omega} = \underline{\underline{\frac{1}{3}}}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0 - 50}{0 + 50} = \underline{\underline{-1}}$$

$$T = \frac{l}{u} = \frac{100\text{m}}{10^8\text{m/s}} = \underline{\underline{1\mu\text{s}}}$$

$$V^+ = V_g \frac{Z_0}{Z_0 + Z_g} = 12\text{V} \frac{50}{50 + 100} = \underline{\underline{4\text{V}}}$$

$$I^+ = \frac{V_g}{Z_0 + Z_g} = \frac{12\text{V}}{50 + 100} = \underline{\underline{80\text{mA}}}$$

$$V_{\infty, \text{sc}} = V(0, t \rightarrow \infty) = V_{\text{sc}}(l, t \rightarrow \infty) = V_g \frac{Z_L}{Z_g + Z_L} = \underline{\underline{0}}$$

$$I_{\infty, \text{sc}} = I_{\text{sc}}(0, t \rightarrow \infty) = I_{\text{sc}}(l, t \rightarrow \infty) = \frac{V_g}{Z_g + Z_L} = \frac{12\text{V}}{100\Omega} = \underline{\underline{120\text{mA}}}$$

Bounce Diagrams

