

At 1.6 GHz, match a load of $Z_L = 25 + j75 \Omega$ to a lossless transmission line ($Z_0 = 50 \Omega$, $u = 2 \times 10^8$ m/s) using a quarter-wave transformer (you may assume $u = 2 \times 10^8$ m/s). Find and sketch both possible solutions for smallest possible circuit. Use 50Ω transmission lines for everything but the quarter-wave transformers.

$$\rightarrow \lambda = \frac{u}{f} = \frac{2 \times 10^8}{1.6 \times 10^9} = 0.125 \text{ m}$$

$$\rightarrow \tilde{Z}_L = \frac{Z_L}{Z_0} = \frac{25 + j75 \Omega}{50 \Omega} = 0.5 + j1.5 \text{ } \Omega \text{ or plot on Smith Chart}$$

\rightarrow Find two possible match points

$$r_{\max} = 7 \text{ } \Omega \quad R_{\max} = 7(50) = \underline{350 \Omega}$$

$$r_{\min} = 0.145 \text{ } \Omega \quad R_{\min} = 0.145(50) = \underline{7.25 \Omega}$$

\rightarrow Find distances from \tilde{Z}_L to r_{\max} & r_{\min}
(λ toward generator)

$$l_{\max} = 0.25 \lambda - 0.1615 \lambda = \underline{\underline{0.0885 \lambda}} = \underline{\underline{0.01106 \text{ m}}}$$


$$l_{\min} = 0.5 \lambda - 0.1615 \lambda = \underline{\underline{0.3385 \lambda}} = \underline{\underline{0.04231 \text{ m}}}$$

\rightarrow Find impedances of the respective $\lambda/4$ transformers


$$(11.58) \quad Z_{0,\max} = \sqrt{50(350)} = \underline{\underline{132.29 \Omega}} \quad \lambda/4 = 0.03125 \text{ m}$$

$$Z_{0,\min} = \sqrt{50(7.25)} = \underline{\underline{19.04 \Omega}} \quad \lambda/4 = 0.03125 \text{ m}$$

r_{max} 50Ω

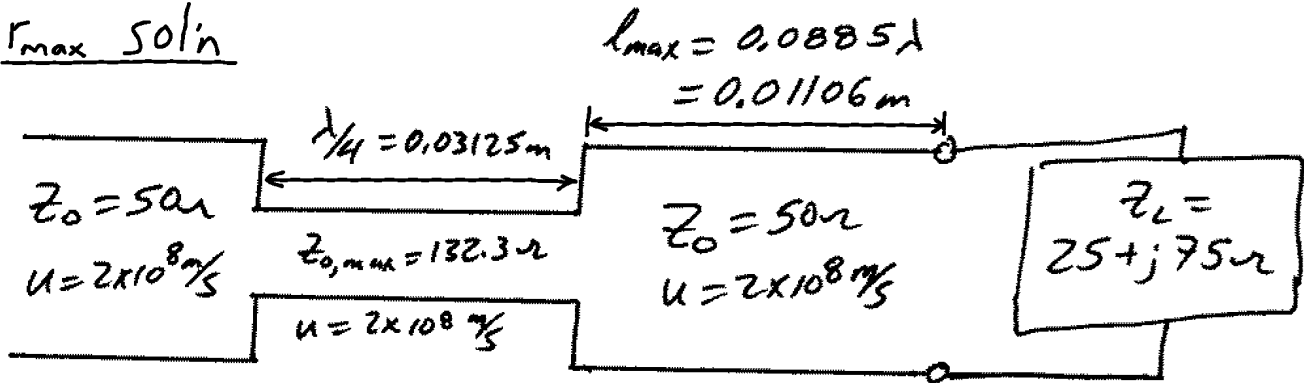

r_{min} 50Ω

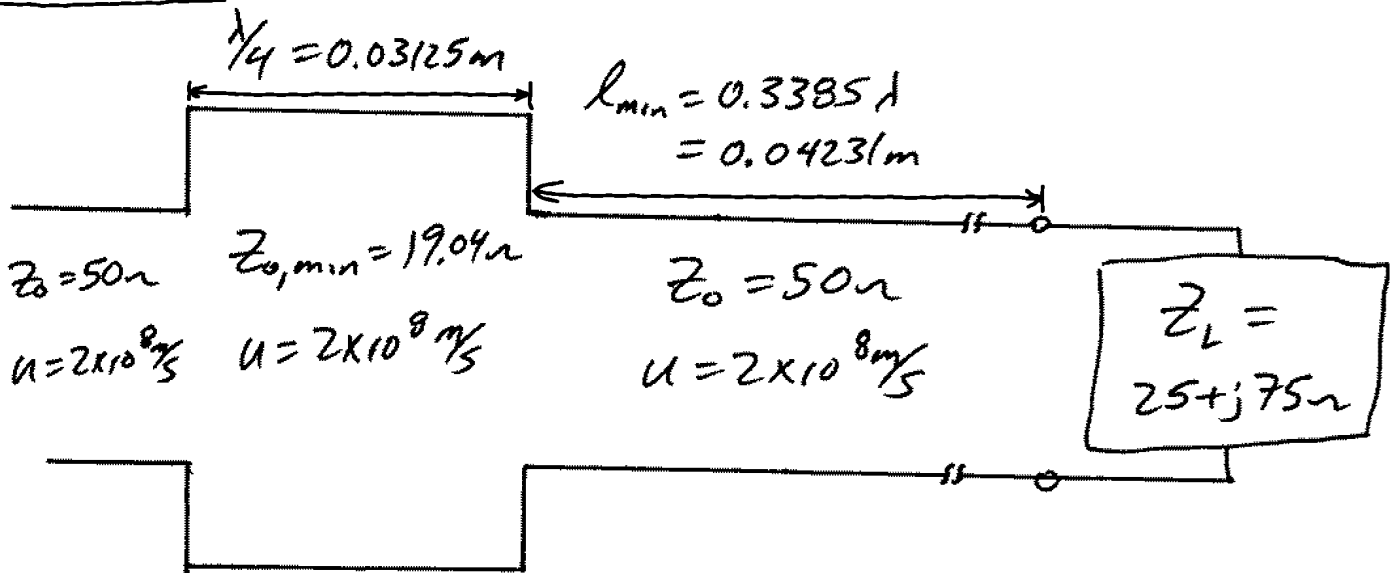

Simple Smith Chart

$$Z_0 = 50\Omega$$

$$u = 2 \times 10^8 \text{ m/s}$$

$$f = 1.6 \text{ GHz}$$

