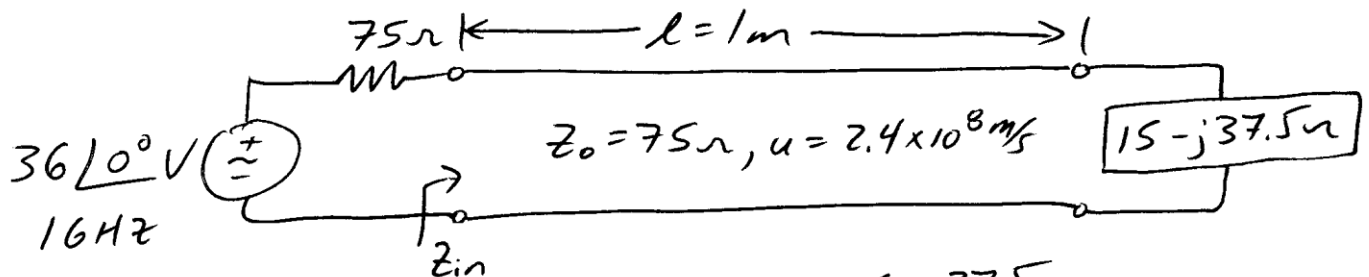


A load of $Z_L = 15 - j37.5 \Omega$ is connected to a 75Ω , $36 \angle 0^\circ \text{ V}$, 1 GHz , sinusoidal generator by a lossless, coaxial transmission line ($u = 2.4 \times 10^8 \text{ m/s}$, $Z_0 = 75 \Omega$) of length 1 m . With no matching, how much power is delivered to the load? Match the load to the generator by placing a single discrete capacitor in series with the transmission line as close to the load as possible. Sketch the resulting circuit with all relevant values. How much power is delivered to the load after matching?



→ Normalize load impedance $y_L = \frac{15 - j37.5}{75} = 0.2 - j0.5 \text{ } \Omega^{-1}$
and plot on Smith Chart

→ Calculate wavelength $\lambda = \frac{u}{f} = \frac{2.4 \times 10^8}{1 \times 10^9} = 0.24 \text{ m}$


No Match

→ Find $\frac{l}{\lambda} = \frac{1}{0.24} = 4.166$

→ Move 0.166λ from y_L to $y_{in, NM} = 0.22 + j0.62 \text{ } \Omega^{-1}$
"WAVELENGTHS TWD GENERATOR" on circle of $|r| = 0.725$

→ $Z_{in, NM} = y_{in, NM} Z_0 = 75(0.22 + j0.62) = 16.5 + j46.5 \Omega$

N.M. Equiv. Circuit

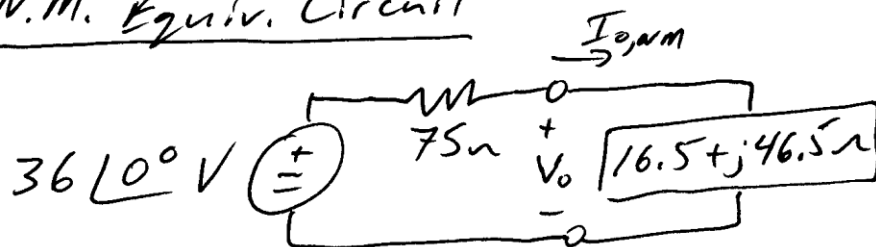

$$I_{0, NM} = \frac{36 \angle 0^\circ}{75 + (16.5 + j46.5)} = 0.35075 \angle -26.94^\circ \text{ A}$$

$$P_{L, NM} = P_{in, NM} = \frac{1}{2} |I_0|^2 \text{Re}\{Z_{in}\} = \frac{1}{2} (0.35075)^2 / 16.5$$

$$\underline{\underline{P_{L, NM} = 1.015 \text{ W}}}$$

Matching

→ Identify the two series match impedance points

$$\gamma_{m1} = 1 + j2.08 \sqrt{Z_0} \quad \text{and} \quad \gamma_{m2} = 1 - j2.08 \sqrt{Z_0}$$

↪ Inductive Reactance

→ Choose γ_{m1} and find distance $l_{m1} = (0.076 + 0.1085)\lambda$

$$l_{m1} = 0.2645\lambda = 0.2645(0.24\text{m}) = \underline{\underline{6.348\text{cm}}}$$

→ Calculate $Z_{m1} = Z_0 \gamma_{m1} = 75(1 + j2.08) = \underline{\underline{75 + j156\Omega}}$

→ $Z_{m1} + Z_{cap} = Z_0$ to find C_{series}

$$75 + j156 - \frac{j}{2\pi(1 \times 10^9)C_s} = 75$$

$$\hookrightarrow C_s = \frac{1}{2\pi(1 \times 10^9)156} \Rightarrow \underline{\underline{C_{series} = 1.0202\text{pF}}}$$


Equiv. CKT w/ Matching

$$I_{0,m} = \frac{36\angle 0^\circ}{75 + 75} = 0.24\angle 0^\circ \text{ A}$$

$$P_{IN,m} = P_{L,m} = \frac{1}{2} |I_{0,m}|^2 75 = \frac{1}{2} (0.24)^2 75 \Rightarrow \underline{\underline{P_{L,m} = 2.16\text{ W}}}$$

over twice
 $P_{L,NM}!!$

↓

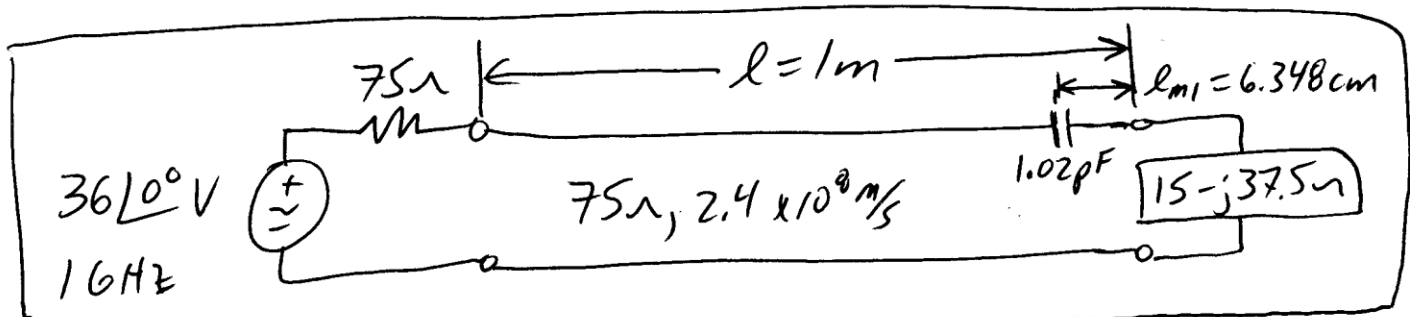

Simple Smith Chart

$Z_0 = 75 \Omega$
 $\mu = 2.4 \times 10^8 \text{ m/s}$
 $f = 16 \text{ Hz}$

