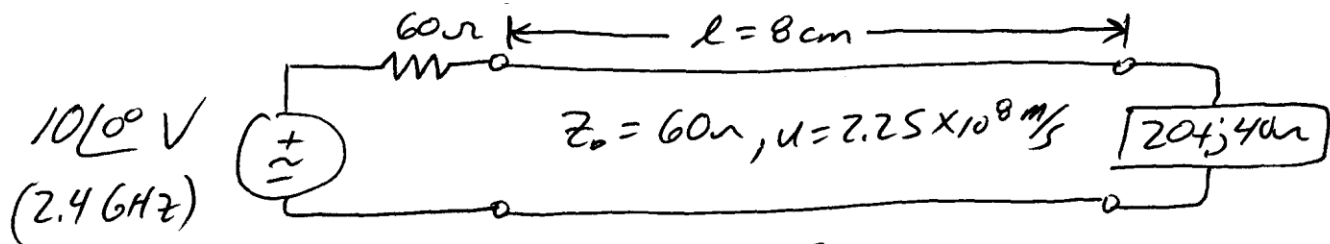


Match a load of $Z_L = 20 + j40 \Omega$ connected to a 60Ω , $10 \angle 0^\circ \text{ V}$, 2.4 GHz , sinusoidal generator with an 8 cm long, lossless transmission line ($Z_0 = 60 \Omega$, $u = 2.25 \times 10^8 \text{ m/s}$) and a **short circuit** single-stub tuner. Find and sketch both possible solutions. How much power is delivered to the load before matching? How much power is delivered to the load after matching? Use the 60Ω transmission line for everything.



$$\rightarrow \text{Calculate } \lambda = \frac{u}{f} = \frac{2.25 \times 10^8}{2.4 \times 10^9} \Rightarrow \underline{\lambda = 9.375 \text{ cm}}$$

$$\rightarrow \text{Normalize load impedance } \gamma_L = \frac{Z_L}{Z_0} = \frac{20 + j40}{60}$$

and plot $\gamma_L = 0.33 + j0.66$ on Smith Chart

and $\gamma_L = \frac{1}{\gamma_L} = 0.6 - j1.2$ (on circle thru γ_L 180° around)

No Match


$$\rightarrow \text{Move } \frac{l}{\lambda} = \frac{8 \text{ cm}}{9.375 \text{ cm}} = 0.8533 \rightarrow 0.3533 \lambda$$

"WAVELENGTHS TOWARD GENERATOR" from γ_L to

$$\gamma_{in, NM} = 0.245 - j0.29$$

$$\rightarrow Z_{in, NM} = Z_0 \gamma_{in, NM} = 60(0.245 - j0.29) \Rightarrow \underline{Z_{in, NM} = 14.7 - j17.4 \Omega}$$

No Match Equiv. CKT

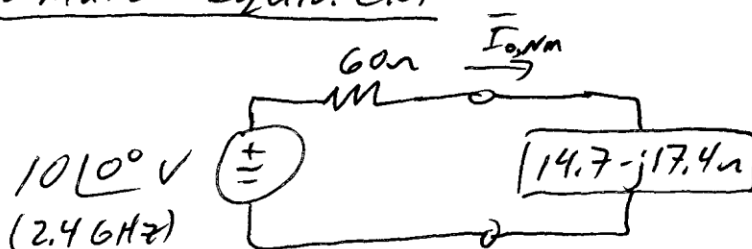

$$\bar{I}_{0, NM} = \frac{10 \angle 0^\circ}{60 + (14.7 - j17.4)} = 0.13038 \angle 13.11^\circ \text{ A}$$

$$P_{in, NM} = P_{L, NM} = \frac{1}{2} |\bar{I}_{0, NM}|^2 (14.7) = \frac{1}{2} (0.1304)^2 (14.7) \Rightarrow \underline{\underline{P_{L, NM} = 0.125 \text{ W}}}$$

Matching

→ On circle of constant $|r| = 0.63$, find two match points $y_{m1} = 1 + j1.63 \text{ S}$ @ $d_1 = 0.25 + 0.08 = 0.33 \lambda$

$$y_{m2} = 1 - j1.63 \text{ S} @ d_2 = 0.25 + 0.221 = 0.471 \lambda$$

→ Convert d_1 + d_2 into units of distance

$$d_1 = 0.33 (9.375 \text{ cm}) = \underline{3.094 \text{ cm}}$$

$$d_2 = 0.471 (9.375 \text{ cm}) = \underline{4.416 \text{ cm}}$$

→ Find length of short circuit stubs required to achieve $y_{\text{stub1}} = -j1.63 \text{ S}$ and $y_{\text{stub2}} = +j1.63 \text{ S}$ by starting @ $y_{\text{sc}} = \infty$ point and moving toward generator on perimeter of Smith chart

$$l_1 = (0.3375 - 0.25) \lambda \Rightarrow \underline{l_1 = 0.0875 \lambda = 0.820 \text{ cm}}$$

$$l_2 = (0.25 + 0.1625) \lambda \Rightarrow \underline{l_2 = 0.4125 \lambda = 3.867 \text{ cm}}$$


Matched Equiv. CKT.

$$\bar{I}_{0,m} = \frac{10\angle 0^\circ}{60 + 60} = 0.08\bar{3} \angle 0^\circ \text{ A}$$


$$P_{in,m} = P_{L,m} = \frac{1}{2} |\bar{I}_{0,m}|^2 60 = \frac{1}{2} (0.08\bar{3})^2 60$$

$$\underline{P_{L,m} = 0.208\bar{3} \text{ W}} \quad (166.6\% \text{ of } P_{L, \text{NM}})$$

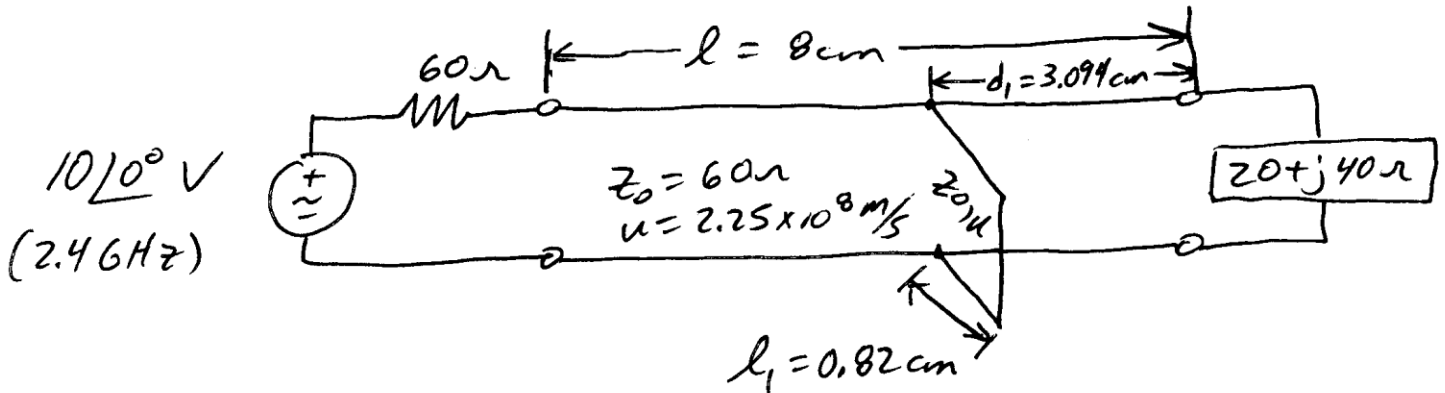Match #1 (use $y_{m1} = 1 + j1.63 \text{ S}$ match point)



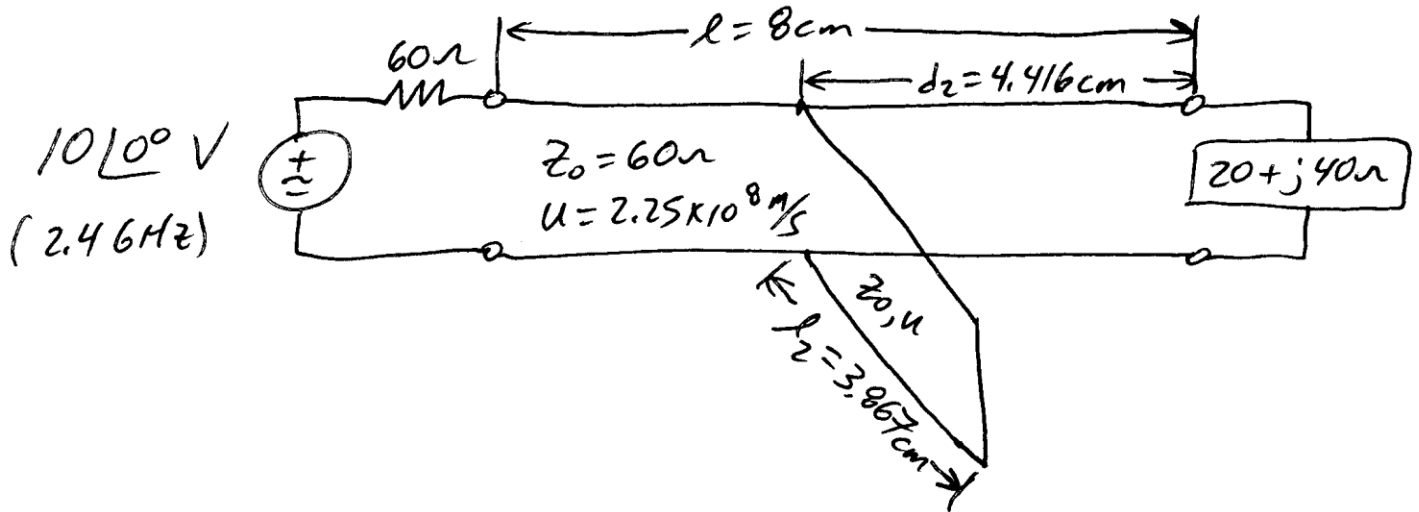Match #2 (use $y_{m2} = 1 - j1.63 \text{ S}$ match point)



Simple Smith Chart

$Z_0 = 60 \Omega$
 $\mu = 2.25 \times 10^8 \text{ m/s}$
 $f = 2.4 \text{ GHz}$

