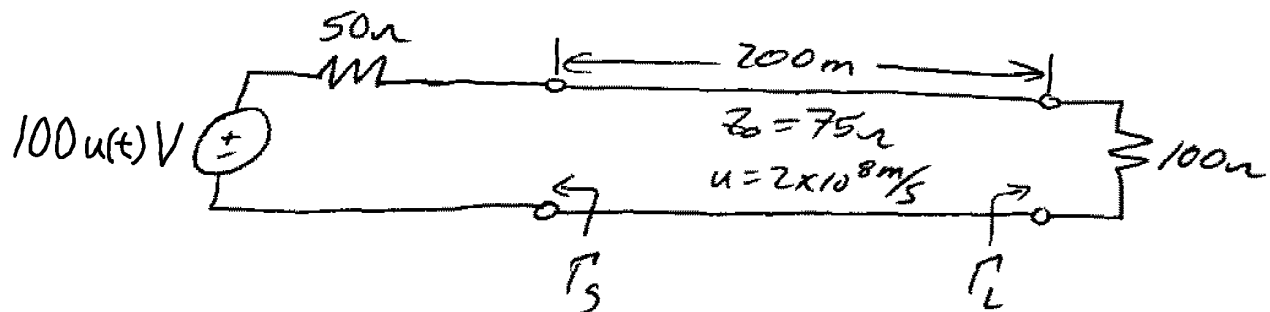


A 200 m long, lossless transmission line ($Z_0 = 75 \Omega$, $u = 2 \times 10^8$ m/s) is driven by a generator with an open circuit voltage of $100 u(t)$ V and a Thevenin resistance of 50Ω . It is terminated by a 100Ω resistive load. Calculate the expected steady-state load current and voltage. Then, find and sketch $V(l, t)$ and $I(l, t)$ for $0 < t < 6 \mu$ s.



$$\Gamma_S = \frac{50 - 75}{50 + 75} = -0.2$$

$$\Gamma_L = \frac{100 - 75}{100 + 75} = \frac{1}{7}$$



$$T = \frac{l}{u} = \frac{200}{2 \times 10^8} = 1 \mu\text{s}$$

$$V^+ = (100 \text{ V}) \frac{75 \Omega}{50 + 75 \Omega} = 60 \text{ V}$$

$$V_{L, \infty} = 100 \frac{100}{50 + 100} = 66.6 \text{ V}$$

$$I^+ = \frac{100 \text{ V}}{50 + 75 \Omega} = 0.8 \text{ A} = 800 \text{ mA}$$
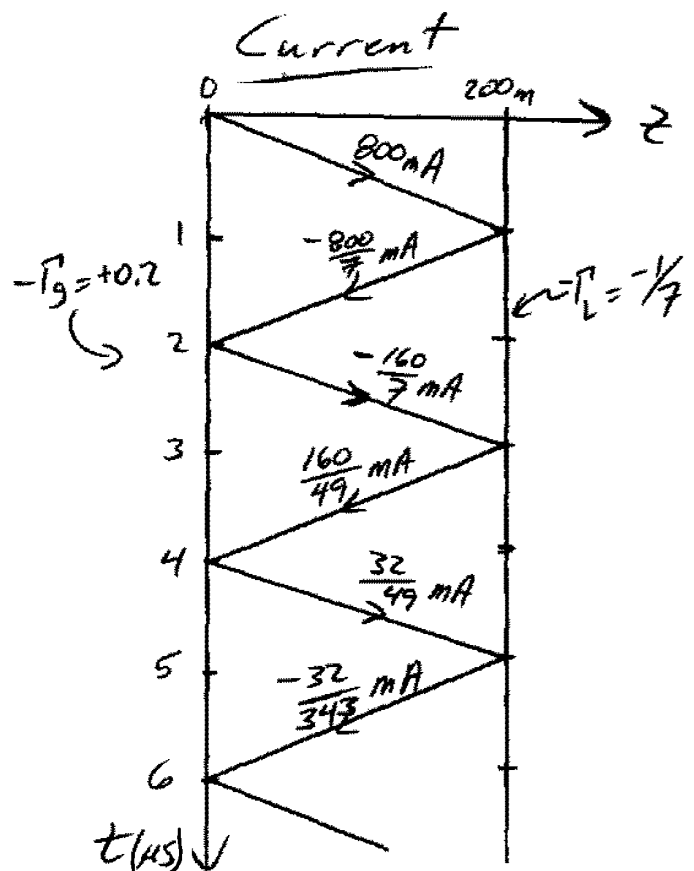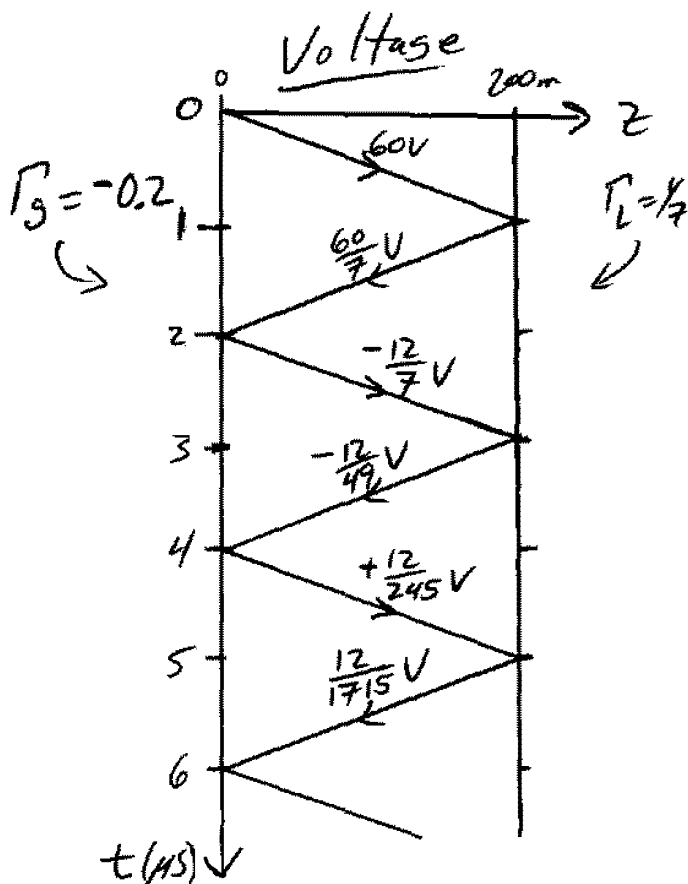
$$I_{L, \infty} = \frac{100}{50 + 100} = 666.6 \text{ mA}$$



→ Draw vertical lines @ $z = l = 200\text{m}$ on bounce diagrams.

→ Note (and add) voltage waves as they arrive

@ $z = l$

