



### EE 382 Applied Electromagnetics Examination #3 (Spring 2018)

Name Key A

**Instructions:** Place answers in indicated spaces. Use notation as given in class. Show all work for full credit. Turn in equation sheet with exam.

30pts

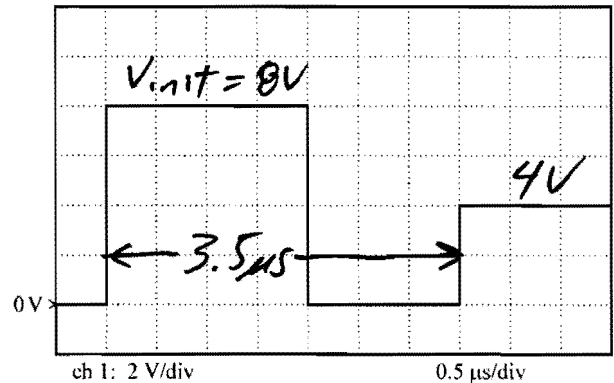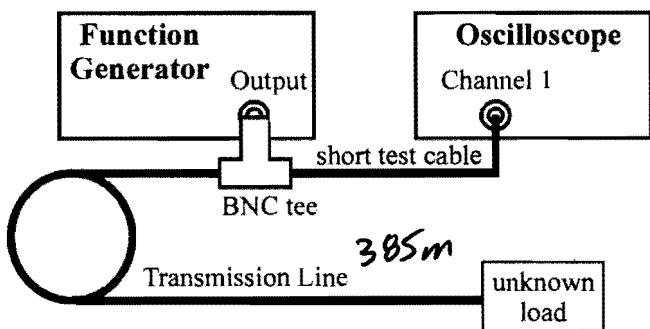- 1) A 385 m length of lossless transmission line is driven by a function generator with a measured open circuit voltage of  $V_{oc}(t) = 24[u(t) - u(t - 2\mu s)]$  V and impedance of  $100\ \Omega$ . Using an oscilloscope, the voltage at the input of the transmission line is measured. Assume the time delay from the short test cable is negligible and that the oscilloscope has a very large input impedance (i.e., does not distort input voltage). Using this information, determine the one-way transit time, transmission line characteristic impedance, phase velocity, generator & load reflection coefficients, and load impedance.




From voltage display,  $2T = 3.5\ \mu s \Rightarrow T = 1.75\ \mu s$

$$T = \frac{l}{u} \Rightarrow u = \frac{l}{T} = \frac{385}{1.75 \times 10^{-6}} = 2.2 \times 10^8\ \text{m/s}$$

$$V_{init} = 8\text{V} = V_{oc} \frac{z_0}{z_g + z_0} = 24\text{V} \frac{z_0}{100 + z_0} \Rightarrow z_0 = 50\ \Omega$$
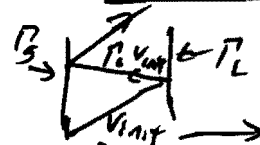
$$\Gamma_g = \frac{z_g - z_0}{z_g + z_0} = \frac{100 - 50}{100 + 50} = 0.33$$



$$4\text{V} = \Gamma_L V_{init} + \Gamma_g \Gamma_L V_{init} = \Gamma_L (8 + 0.33(8))$$

$$\Gamma_L = \frac{4}{8 + 8/3} = 0.375$$

$$z_L = z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} = 50 \frac{1 + 0.375}{1 - 0.375} = 110\ \Omega$$

one-way transit time = 1.75 μs

characteristic impedance = 50 Ω

generator reflection coeff. = 0.33

load reflection coeff. = 0.375

phase velocity = 2.2 × 10<sup>8</sup> m/s

load impedance = 110 Ω

30pts 2) A phasor electric field of  $\vec{E} = \hat{a}_x 60 e^{-\gamma y}$  V/m is propagating through a material where  $\epsilon = 3\epsilon_0$ ,  $\mu = \mu_0$ , and  $\sigma = 0.006$  S/m. If the TEM wave oscillates at 220 MHz, find the propagation constant, wavelength, velocity, intrinsic impedance, skin depth, and loss tangent. Then, determine the time-domain electric and magnetic fields (define all constants). Put all complex quantities in rectangular form.

$$\gamma = \sqrt{j\omega\mu(\sigma + j\omega\epsilon)} = \sqrt{j2\pi(220 \times 10^6)4\pi \times 10^{-7}(0.006 + j2\pi(220 \times 10^6)3(8.854 \times 10^{-12}))}$$

$$\gamma = 0.65036 + j8.01268 \text{ m}^{-1}$$

$$\text{loss tangent} = \frac{\sigma}{\omega\epsilon} = \frac{0.006}{2\pi(220 \times 10^6)3(8.854 \times 10^{-12})} = 0.16341$$

$$u = \frac{\omega}{\beta} = \frac{2\pi(220 \times 10^6)}{8.01268} = 1.72514 \times 10^8 \text{ m/s}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{8.01268} = 0.78416 \text{ m}$$

$$\delta = \frac{1}{\alpha} = \frac{1}{0.65} = 1.5376 \text{ m}$$

$$\eta = \sqrt{\frac{j\omega\mu}{\sigma + j\omega\epsilon}} = \sqrt{\frac{j2\pi(220 \times 10^6)4\pi \times 10^{-7}}{0.006 + j2\pi(220 \times 10^6)3(8.854 \times 10^{-12})}} = 215.3688 + j17.4808 \Omega$$

$$\vec{E} = \text{Re}\{\vec{E} e^{j\omega t}\} = \text{Re}\{\hat{a}_x 60 e^{-0.6504y} e^{-j8.01268y} e^{j2\pi(220 \times 10^6)t}\}$$

$$= \hat{a}_x 60 e^{-0.6504y} \cos(4.4\pi \times 10^8 t - 8.01268y) \text{ V/m}$$

$$\vec{H} = \frac{\hat{a}_k \times \vec{E}}{\eta} = \frac{\hat{a}_y \times \hat{a}_x 60 e^{-\gamma y}}{215.3688 + j17.4808} = -\hat{a}_z 0.27768 e^{-0.6504y} e^{-j8.0127y} e^{-j4.64^\circ} \text{ A/m}$$

$$\vec{H} = \text{Re}\{\vec{H} e^{j\omega t}\} = -\hat{a}_z 0.27768 e^{-0.6504y} \cos(4.4\pi \times 10^8 t - 8.0127y - 4.64^\circ) \text{ A/m}$$

propagation constant =  $0.65036 + j8.01268 \text{ m}^{-1}$

loss tangent =  $0.16341$

wave velocity =  $1.72514 \times 10^8 \text{ m/s}$

wavelength =  $0.78416 \text{ m}$


intrinsic impedance =  $215.3688 + j17.4808 \Omega$

skin depth =  $1.5376 \text{ m}$

time-domain electric field =  $\hat{a}_x 60 e^{-0.6504y} \cos(4.4\pi \times 10^8 t - 8.01268y) \text{ V/m}$

time-domain magnetic field =  $-\hat{a}_z 0.2777 e^{-0.6504y} \cos(4.4\pi \times 10^8 t - 8.01268y - 4.64^\circ) \text{ A/m}$


- 20  
pts
- 3) For the lossless transmission line ( $Z_0 = 50 \Omega$  and  $u = 2 \times 10^8$  m/s) circuit shown, the generator resistance is  $200 \Omega$ , the load resistance is  $25 \Omega$ , and  $V_g(t) = 20 [u(t) - u(t - 1.25 \mu\text{s})]$  V. If  $l = 500$  m, compute the one-way transit time  $T$ , load & generator voltage reflection coefficients, and the magnitude of the initial current & voltage waves at the input ( $z = 0$ ). Then, draw the current & voltage bounce diagrams (properly labeled with values) for  $0 \leq t \leq 5T$ . Using bounce diagrams, make **fully-labeled** sketches of the **load** voltage for  $0 \leq t \leq 4T$  and **current** along the transmission line (i.e.,  $0 \leq z \leq l$ ) at  $t = 2T$ .

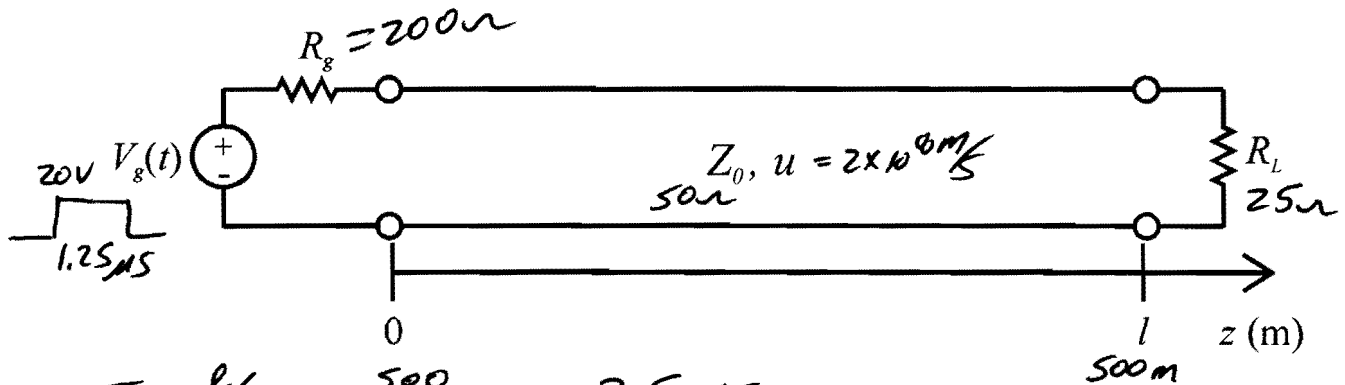

$$T = \frac{l}{u} = \frac{500}{2 \times 10^8} = \underline{2.5 \mu\text{s}}$$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{25 - 50}{25 + 50} = \underline{-\frac{1}{3} = -0.\overline{33}}$$
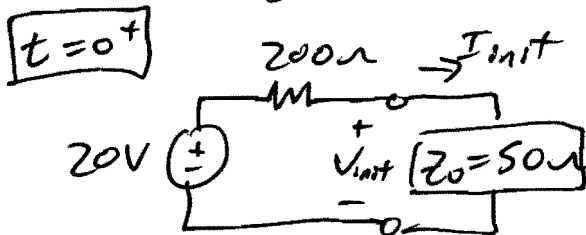
$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{200 - 50}{200 + 50} = \underline{0.6}$$



$$I_{\text{init}} = \frac{20}{200 + 50} = 0.08 \text{ A} = \underline{80 \text{ mA}}$$

$$V_{\text{init}} = 20 \frac{50}{200 + 50} = \underline{4 \text{ V}}$$

$T = \underline{2.5 \mu\text{s}} \quad \Gamma_L = \underline{-0.\overline{33}} \quad \Gamma_g = \underline{0.6}$

$I_{\text{init}} = \underline{80 \text{ mA}} \quad V_{\text{init}} = \underline{4 \text{ V}}$

