
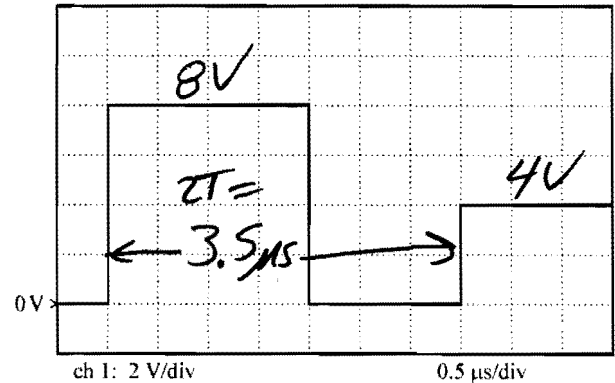


EE 382 Applied Electromagnetics Examination #3 (Spring 2018)

Name Key B

Instructions: Place answers in indicated spaces. Use notation as given in class. Show all work for full credit. Turn in equation sheet with exam.

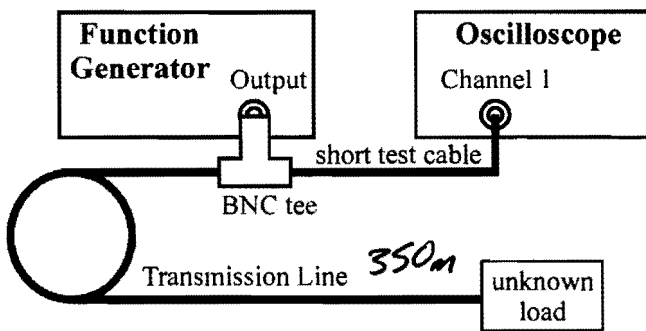- 1) A 350 m length of lossless transmission line is driven by a function generator with a measured open circuit voltage of $V_{oc}(t) = 12[u(t) - u(t - 2\mu s)]$ V and impedance of $100\ \Omega$. Using an oscilloscope, the voltage at the input of the transmission line is measured. Assume the time delay from the short test cable is negligible and that the oscilloscope has a very large input impedance (i.e., does not distort input voltage). Using this information, determine the one-way transit time, transmission line characteristic impedance, phase velocity, generator & load reflection coefficients, and load impedance.




From voltage display, $2T = 3.5\ \mu s \Rightarrow T = 1.75\ \mu s$

$l = uT \Rightarrow u = l/T = \frac{350\ m}{1.75 \times 10^{-6}} = 2 \times 10^8\ m/s$

$V_{init} = 8V = V_{oc} \frac{z_0}{z_g + z_0} = 12 \frac{z_0}{100 + z_0} \Rightarrow z_0 = 200\ \Omega$

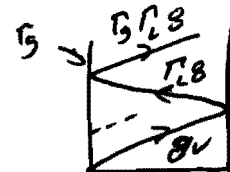$\Gamma_g = \frac{z_g - z_0}{z_g + z_0} = \frac{100 - 200}{100 + 200} = -0.33$



$4V = 8\Gamma_L + 8\Gamma_L\Gamma_g = \Gamma_L(8 - 8/3) \Rightarrow \Gamma_L = 0.75$

$z_L = z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} = 200 \frac{1 + 0.75}{1 - 0.75} = 1400\ \Omega$

one-way transit time = 1.75 μs

characteristic impedance = 200 Ω

generator reflection coeff. = -0.33

load reflection coeff. = 0.75

phase velocity = 2 × 10⁸ m/s

load impedance = 1400 Ω

2) A phasor electric field of $\vec{E} = \hat{a}_y 80 e^{-\gamma x}$ V/m is propagating through a material where $\epsilon = 4\epsilon_0$, $\mu = \mu_0$, and $\sigma = 0.005$ S/m. If the TEM wave oscillates at 180 MHz, find the propagation constant, wavelength, velocity, intrinsic impedance, skin depth, and loss tangent. Then, determine the time-domain electric and magnetic fields (define all constants). Put all complex quantities in rectangular form.

$$\gamma = \sqrt{j\omega\mu_0(\sigma + j\omega\epsilon)} = \sqrt{j2\pi(180 \times 10^6)4\pi \times 10^{-7}(0.005 + j2\pi(180 \times 10^6)4(8.854 \times 10^{-12}))}$$

$$= \underline{0.470002 + j7.55967 \text{ m}^{-1}}$$

$$\text{loss tangent} = \frac{\sigma}{\omega\epsilon} = \frac{0.005}{2\pi(180 \times 10^6)4(8.854 \times 10^{-12})} = \underline{0.12483}$$

$$u = \frac{\omega}{\beta} = \frac{2\pi(180 \times 10^6)}{7.55967} = \underline{1.49606 \times 10^8 \text{ m/s}}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{7.55967} = \underline{0.83115 \text{ m}}$$

$$\delta = \frac{1}{\alpha} = \frac{1}{0.47} = \underline{2.12765 \text{ m}}$$

$$\eta = \sqrt{\frac{j\omega\mu_0}{\sigma + j\omega\epsilon}} = \sqrt{\frac{j2\pi(180 \times 10^6)4\pi \times 10^{-7}}{0.005 + j2\pi(180 \times 10^6)4(8.854 \times 10^{-12})}} = 187.63845 \angle 3.5576^\circ \Omega$$

$$= \underline{187.2769 + j11.6434 \Omega}$$

$$\vec{E} = \text{Re}\{\vec{E} e^{j\omega t}\} = \text{Re}\{\hat{a}_y 80 e^{-0.47x} e^{-j7.56x} e^{j2\pi(180 \times 10^6)t}\}$$

$$= \hat{a}_y 80 e^{-0.47x} \cos(3.6\pi \times 10^8 t - 7.56x) \text{ V/m}$$

$$\vec{H} = \frac{\hat{a}_k \times \vec{E}}{\eta} = \frac{\hat{a}_x \times \hat{a}_y 80 e^{-\gamma x}}{187.63845 \angle 3.56^\circ} = \hat{a}_z 0.42635 e^{-0.47x} e^{-j7.56x} e^{-j3.56^\circ} \text{ A/m}$$

$$\vec{H} = \text{Re}\{\vec{H} e^{j\omega t}\} = \hat{a}_z 0.42635 e^{-0.47x} \cos(3.6\pi \times 10^8 t - 7.56x - 3.56^\circ) \text{ A/m}$$

propagation constant = $\underline{0.470 + j7.5597 \text{ m}^{-1}}$

loss tangent = $\underline{0.12483}$

wave velocity = $\underline{1.49606 \times 10^8 \text{ m/s}}$

wavelength = $\underline{0.83115 \text{ m}}$


intrinsic impedance = $\underline{187.277 + j11.643 \Omega}$

skin depth = $\underline{2.12765 \text{ m}}$

time-domain electric field = $\underline{\hat{a}_y 80 e^{-0.47x} \cos(3.6\pi \times 10^8 t - 7.56x) \text{ V/m}}$

time-domain magnetic field = $\underline{\hat{a}_z 0.42635 e^{-0.47x} \cos(3.6\pi \times 10^8 t - 7.56x - 3.56^\circ) \text{ A/m}}$

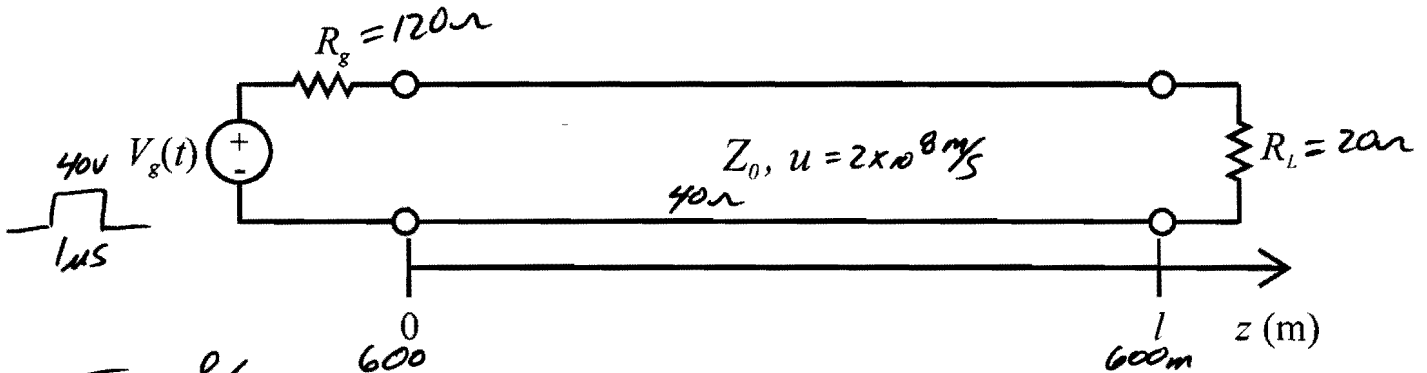3) For the lossless transmission line ($Z_0 = 40 \Omega$ and $u = 2 \times 10^8$ m/s) circuit shown, the generator resistance is 120Ω , the load resistance is 20Ω , and $V_g(t) = 40 [u(t) - u(t - 1 \mu s)]$ V. If $l = 600$ m, compute the one-way transit time T , load & generator voltage reflection coefficients, and the magnitude of the initial current & voltage waves at the input ($z = 0$). Then, draw the current & voltage bounce diagrams (properly labeled with values) for $0 \leq t \leq 5T$. Using bounce diagrams, make **fully-labeled** sketches of the load voltage for $0 \leq t \leq 4T$ and **current** along the transmission line (i.e., $0 \leq z \leq l$) at $t = 2T$.




$$T = \frac{l}{u} = \frac{600}{2 \times 10^8} = \underline{3 \mu s}$$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{20 - 40}{20 + 40} = -\frac{1}{3} = \underline{-0.33}$$

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{120 - 40}{120 + 40} = \underline{0.5}$$

@ $t = 0^+$

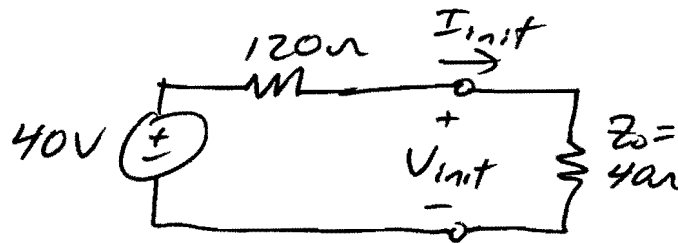

$$I_{init} = \frac{40}{120 + 20} = 0.25 \text{ A} = \underline{250 \text{ mA}}$$

$$V_{init} = I_{init} R_L = 0.25(20) = \underline{10 \text{ V}}$$

$$T = \underline{3 \mu s}$$

$$\Gamma_L = \underline{-0.33}$$

$$\Gamma_g = \underline{0.5}$$

$$I_{init} = \underline{250 \text{ mA}}$$

$$V_{init} = \underline{10 \text{ V}}$$

20 pts

