

**Homework 8**  
**EE 382/L Applied Electromagnetics (Spring 2018)**  
**Monday, March 19, 2018**

- 1) PE11.8a Also, find steady-state currents and voltages at input and load.
- 2) PE11.9
- 3) A 200 m long, lossless transmission line ( $Z_0 = 75 \Omega$ ,  $u = 2 \times 10^8$  m/s) is driven by a generator with an open circuit voltage of  $100 u(t)$  V and a Thevenin resistance of  $50 \Omega$ . It is terminated by a  $100 \Omega$  resistive load. Calculate the expected steady-state load current and voltage. Then, find and sketch  $V(l, t)$  and  $I(l, t)$  for  $0 < t < 6 \mu\text{s}$ .
- 4) A 200 m long, lossless transmission line ( $Z_0 = 75 \Omega$ ,  $u = 2 \times 10^8$  m/s) is driven by a generator with an open circuit voltage of  $100 u(t)$  V and a Thevenin resistance of  $50 \Omega$ . It is terminated by a  $100 \Omega$  resistive load. Find and sketch  $V(z, t = 1.25T)$  and  $I(z, t = 1.75T)$ .
- 5) An 800 m long, lossless transmission line ( $Z_0 = 75 \Omega$ ,  $u = 2 \times 10^8$  m/s) is driven by a generator with an open circuit voltage of  $100 [u(t) - u(t - 3 \mu\text{s})]$  V and a Thevenin resistance of  $50 \Omega$ . It is terminated by a  $125 \Omega$  resistive load. Sketch  $V(z = 0, 0 < t < 6T)$  and  $I(z, t = 2.25T)$ .
- 6) A TDR that has an open circuit voltage of  $100 u(t)$  V and a Thevenin resistance of  $75 \Omega$  is connected to a length of lossless transmission line ( $Z_0 = 75 \Omega$ ,  $u = 2.3 \times 10^8$  m/s) of unknown length with an unknown resistive load. At the TDR terminals, what voltage would initially be measured? If the voltage measured at the TDR terminals changes to 35 V at  $1.2 \mu\text{s}$ , what is the length of the cable and the load resistance?

**Due Monday, March 26, 2018.**