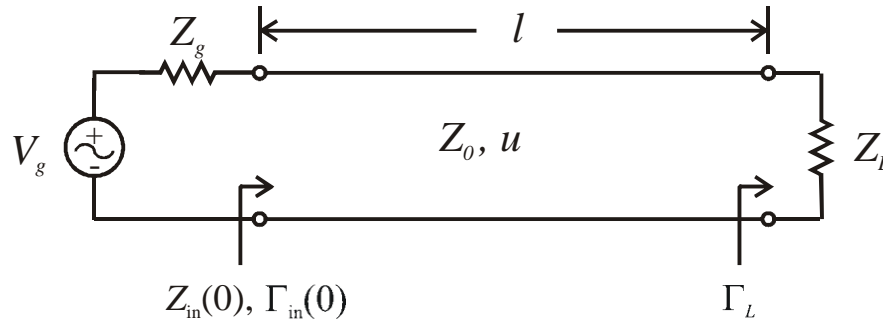


## EE382 Applied EM Quiz #3 (Spring 2018)

Name           KEY A          

**Closed book, notes, and calculators. Show all work, including that on Smith Chart, for credit.**

Consider a lossless transmission line circuit where  $Z_0 = 100 \Omega$ ,  $f = 500 \text{ MHz}$ ,  $u = 2 \times 10^8 \text{ m/s}$ ,  $l = 2.285\lambda$ , and  $Z_L = 30 - j70 \Omega$ . Using a **Smith Chart, compass, & straight-edge**, find the load & input reflection coefficients (i.e.,  $\Gamma_L$  &  $\Gamma_{in}(0)$ ), normalized input impedance  $z_{in}(0)$ , input impedance  $Z_{in}(0)$ , and VSWR. **Clearly label** all points/work on Smith chart. Express **impedances in rectangular form** and **reflection coefficients in polar form** (e.g.,  $A/\theta^\circ$ ).



- Normalize load impedance  $z_L = Z_L/Z_0 = (30 - j70)/100 \Rightarrow z_L = \underline{0.3 - j0.7 \Omega/\Omega}$ .
- Plot  $z_L$  on Smith Chart. Use straight-edge to draw line from center of Smith chart through  $z_L$  and 'ANGLE OF REFLECTION COEFFICIENT IN DEGREES' scale to get  $\Rightarrow \angle \Gamma_L = \underline{-106.8^\circ}$ .
- Use compass & scales at bottom of Smith Chart to get  $|\Gamma_L| = \underline{0.67}$  &  $\text{VSWR} = \underline{5.05}$ .
- Use compass to draw circle of  $|\Gamma| = 0.67$ , centered on Smith chart, through  $z_L$ .
- Move  $0.285\lambda$  from  $z_L$  point on Smith chart toward the generator on circle of  $|\Gamma| = 0.67$ . Mark and read  $\Rightarrow z_{in}(0) = \underline{1 + j1.8 \Omega/\Omega}$ .
- Use straight-edge to draw line from center of Smith chart through  $z_{in}(0)$  and the 'ANGLE OF REFLECTION COEFFICIENT IN DEGREES' scale. Read the angle to be  $\angle \Gamma_{in} = \underline{48.2^\circ}$ .
- Calculate  $Z_{in}(0) = z_{in}(0) Z_0 = (1 + j1.8)100 = \underline{100 + j180 \Omega}$ .

\*\*\*\*\*  
For comparison, analytic results:

$$\Gamma_L = 0.6705 \angle -106.699^\circ, \Gamma_{in}(0) = 0.6705 \angle 48.101^\circ, Z_{in}(0) = 99.357 + j180.156 \Omega,$$

$\text{VSWR} = 5.069$

\*\*\*\*\*


$$\Gamma_L = \underline{0.67 \angle -106.8^\circ} \quad \Gamma_{in}(0) = \underline{0.67 \angle 48.2^\circ} \quad z_{in}(0) = \underline{1 + j1.8 \Omega/\Omega}$$

$$Z_{in}(0) = \underline{100 + j180 \Omega} \quad \text{VSWR} = \underline{5.05}$$

### Simple Smith Chart


$Z_0 = 100 \Omega$   
 $u = 2 \times 10^8 \text{ m/s}$   
 $f = 500 \text{ MHz}$

$\angle \Gamma_{in} = 48.2^\circ$

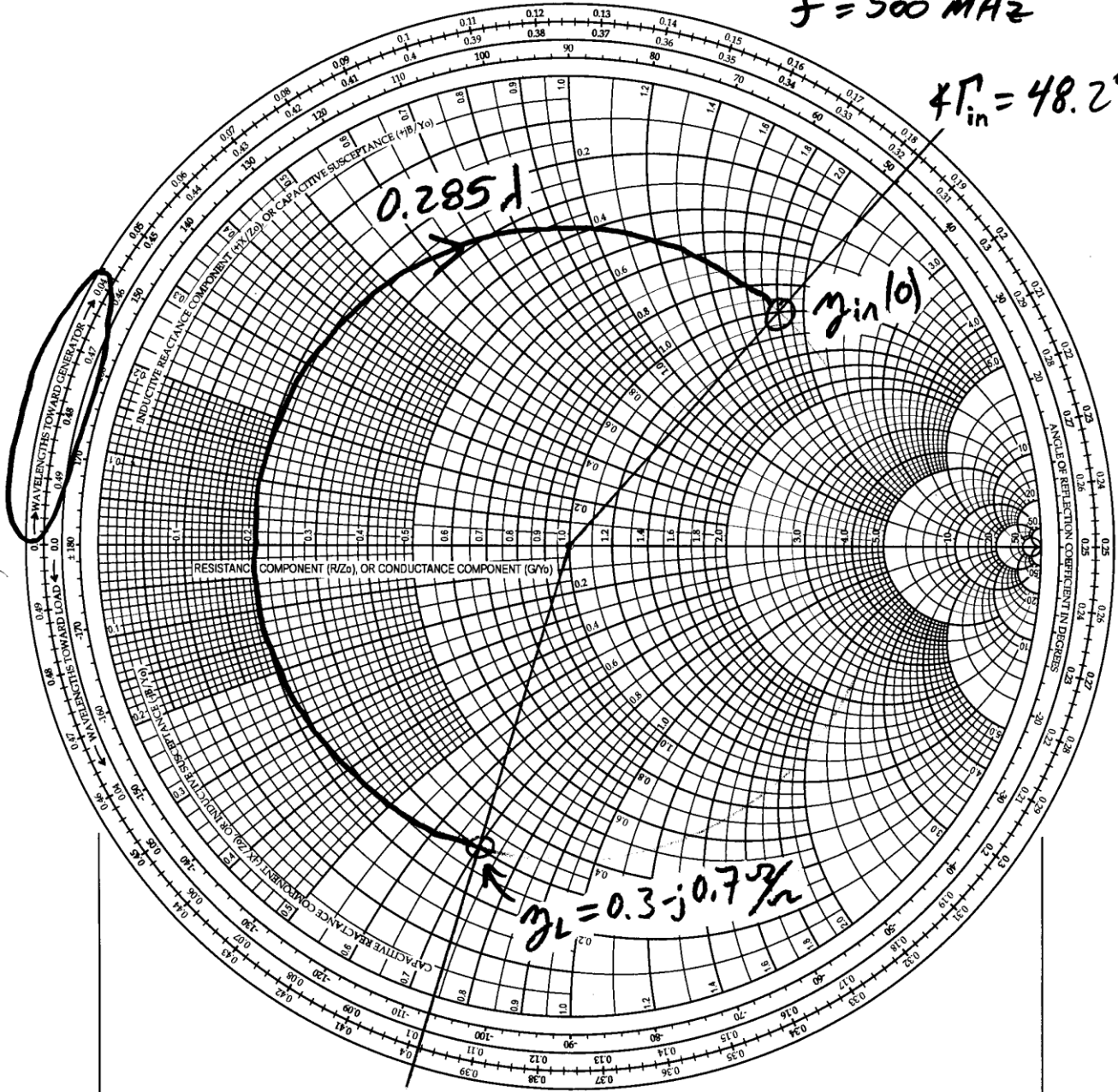

$\angle \Gamma_L = -106.8^\circ$

RADIALLY SCALED PARAMETERS

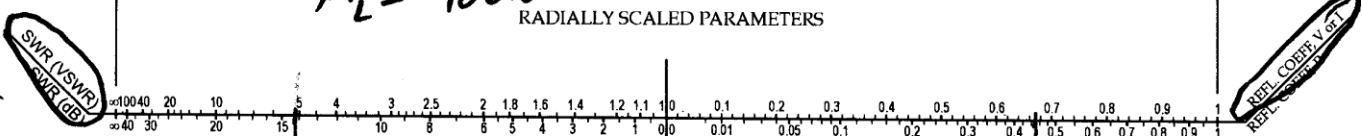

$V_{SWR} = 5.05$

$|\Gamma| = 0.67$