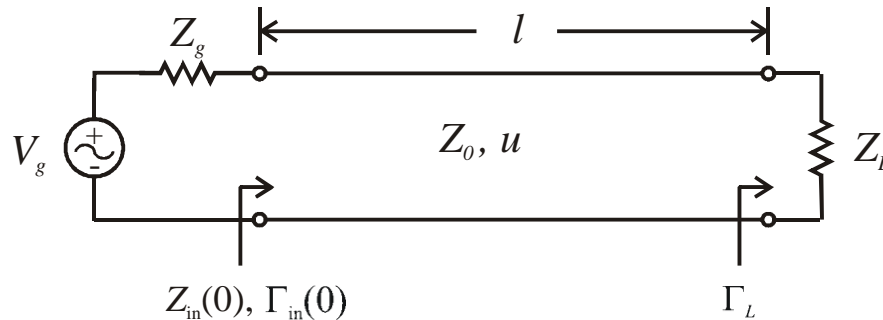


EE382 Applied EM Quiz #3 (Spring 2018)

Name KEY B

Closed book, notes, and calculators. Show all work, including that on Smith Chart, for credit.

Consider a lossless transmission line circuit where $Z_0 = 100 \Omega$, $f = 800 \text{ MHz}$, $u = 2 \times 10^8 \text{ m/s}$, $l = 2.285\lambda$, and $Z_L = 30 + j70 \Omega$. Using a **Smith Chart, compass, & straight-edge**, find the load & input reflection coefficients (i.e., Γ_L & $\Gamma_{in}(0)$), normalized input impedance $z_{in}(0)$, input impedance $Z_{in}(0)$, and VSWR. **Clearly label** all points/work on Smith chart. Express **impedances in rectangular form** and **reflection coefficients in polar form** (e.g., A/θ°).



- Normalize load impedance $z_L = Z_L/Z_0 = (30 + j70)/100 \Rightarrow z_L = \underline{0.3 + j0.7 \Omega/\Omega}$.
- Plot z_L on Smith Chart. Use straight-edge to draw line from center of Smith chart through z_L and 'ANGLE OF REFLECTION COEFFICIENT IN DEGREES' scale to get $\Rightarrow \angle \Gamma_L = \underline{106.7^\circ}$.
- Use compass & scales at bottom of Smith Chart to get $|\Gamma_L| = \underline{0.67}$ & $\text{VSWR} = \underline{5.05}$.
- Use compass to draw circle of $|\Gamma| = 0.67$, centered on Smith chart, through z_L .
- Move 0.285λ from z_L point on Smith chart toward the generator on circle of $|\Gamma| = 0.67$. Mark and read $\Rightarrow z_{in}(0) = \underline{0.33 - j0.805 \Omega/\Omega}$.
- Use straight-edge to draw line from center of Smith chart through $z_{in}(0)$ and the 'ANGLE OF REFLECTION COEFFICIENT IN DEGREES' scale. Read the angle to be $\angle \Gamma_{in} = \underline{-98.5^\circ}$.
- Calculate $Z_{in}(0) = z_{in}(0) Z_0 = (0.33 - j0.805)100 = \underline{33 - j80.5 \Omega}$.

For comparison, analytic results:

$$\Gamma_L = 0.6705 \angle 106.699^\circ, \Gamma_{in}(0) = 0.6705 \angle -98.501^\circ, Z_{in}(0) = 33.4064 - j80.4863 \Omega,$$

VSWR = 5.069


$$\Gamma_L = \underline{0.67 \angle 106.7^\circ} \quad \Gamma_{in}(0) = \underline{0.67 \angle -98.5^\circ} \quad z_{in}(0) = \underline{0.33 - j0.805 \Omega/\Omega}$$

$$Z_{in}(0) = \underline{33 - j80.5 \Omega} \quad \text{VSWR} = \underline{5.05}$$

Simple Smith Chart

$Z_0 = 100 \Omega$
 $f = 800 \text{ MHz}$
 $u = 2 \times 10^8 \text{ m/s}$

$\angle \Gamma_L = 106.7^\circ$

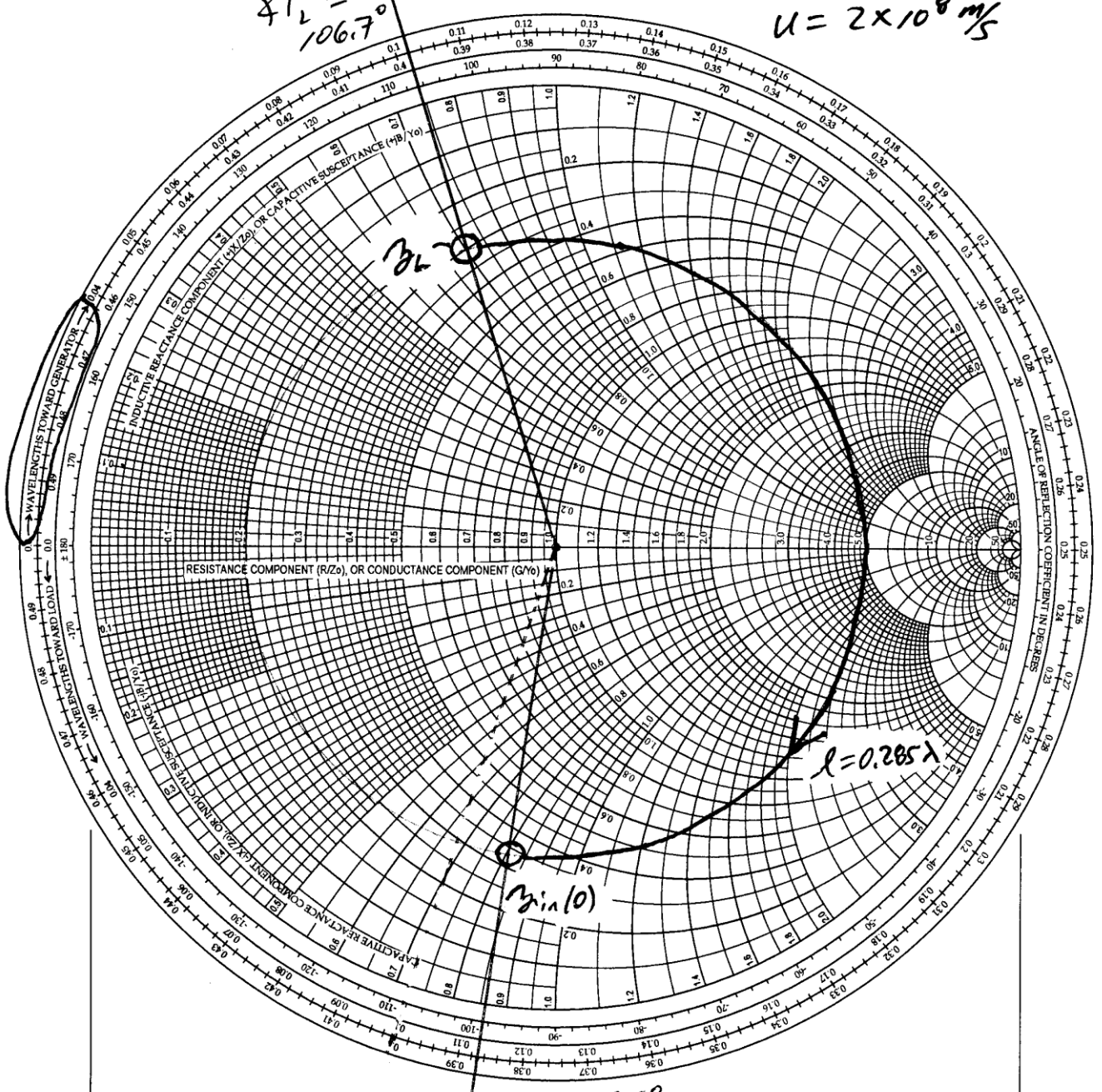

$\angle \Gamma_{in} = -98.5^\circ$

RADIALLY SCALED PARAMETERS

$V_{SWR} = 5.05$

$|\Gamma| = 0.67$

SWR (VSWR)
SWR (dB)

REF. COEFF. V_{ref}
Reflection

