


EE 382 Applied EM Quiz #5 (Spring 2018)

Name Key A

Instructions: Closed book. Place answers in indicated spaces and show all work for credit.

Equations: $\Gamma_x = \frac{Z_x - Z_0}{Z_x + Z_0}$, $SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$, $Z_{in}(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$, distance = velocity \times time, $V = IR$

For the transmission line circuit shown, calculate the load reflection coefficient Γ_L and generator reflection coefficient Γ_g , one-way transit time T , and initial & steady-state current & voltage at $z = 0$. Then, draw a voltage bounce diagram for $0 \leq t \leq 3T$, and sketch $V(0, t)$ for $0 \leq t \leq 3T$. Given: $V_g(t) = 50 u(t)$ V, $R_g = 50 \Omega$, $Z_0 = 75 \Omega$, $R_L = 175 \Omega$, $u = 1.25 \times 10^8$ m/s, and $l = 250$ m.

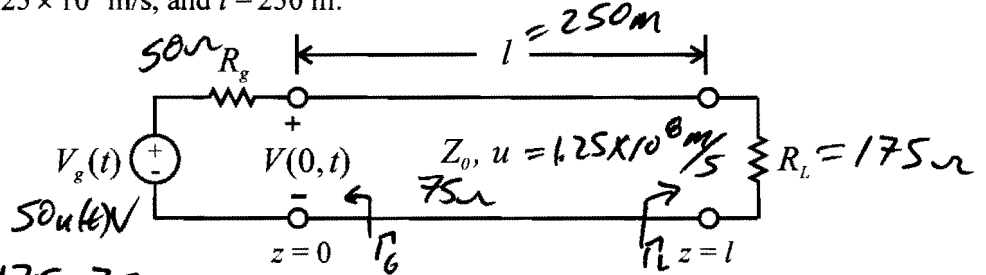

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{175 - 75}{175 + 75} = 0.4 ; \Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0} = \frac{50 - 75}{50 + 75} = -0.2$$

$$T = \frac{l}{u} = \frac{250}{1.25 \times 10^8} = 2 \times 10^{-6} = 2 \mu s$$



$$I_{initial} = \frac{V_g}{R_g + Z_0} = \frac{50}{50 + 75} = 0.4 A \quad V_{initial} = V_g \frac{Z_0}{Z_0 + R_g} = \frac{50(75)}{50 + 75} = 30V$$

$$I_{SS} = \frac{V_g}{R_g + R_L} = \frac{50}{50 + 175} = 0.22 A \quad V_{SS} = V_g \frac{R_L}{Z_0 + R_L} = \frac{50(175)}{50 + 175} = 38.8 V$$

$$0 \leq t < 4 \mu s \quad V(0,t) = V_{initial} = 30V \quad 4 \mu s \leq t < 8 \mu s \quad V(0,t) = 30 + 12 - 2.4 = 39.6V$$

$\Gamma_L = 0.4$ $\Gamma_g = -0.2$ $T = 2 \mu s$ Initial current = $0.4 A$

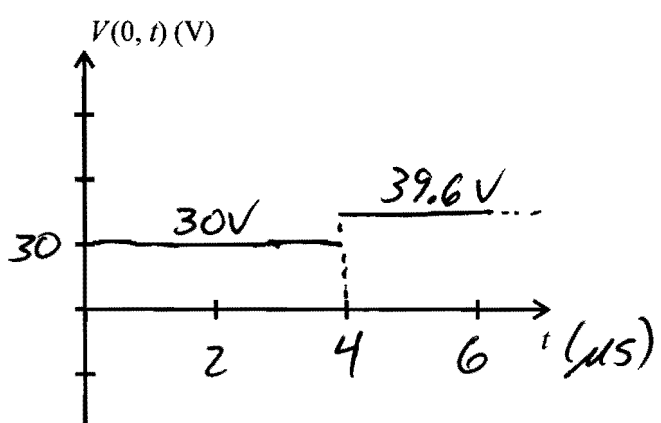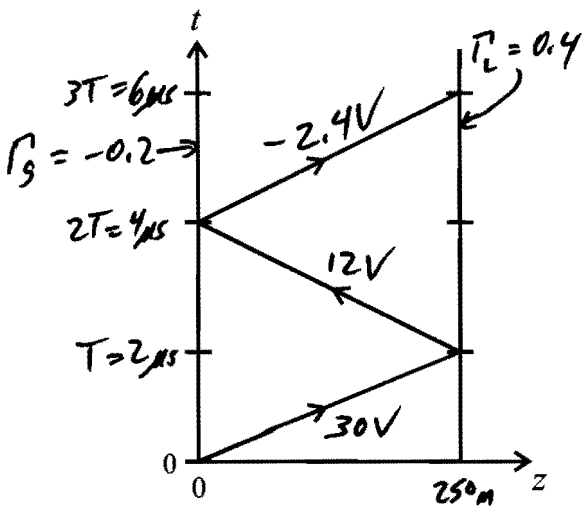Initial voltage = $30V$ S.S. current = $0.22 A$ S.S. voltage = $38.8 V$




EE 382 Applied EM Quiz #5 (Spring 2018)

Name Key B

Instructions: Closed book. Place answers in indicated spaces and show all work for credit.

Equations: $\Gamma_x = \frac{Z_x - Z_0}{Z_x + Z_0}$, $SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$, $Z_{in}(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$, distance = velocity \times time, $V = IR$

For the transmission line circuit shown, calculate the load reflection coefficient Γ_L and generator reflection coefficient Γ_g , one-way transit time T , and initial & steady-state current & voltage at $z = 0$. Then, draw a voltage bounce diagram for $0 \leq t \leq 3T$, and sketch $V(0, t)$ for $0 \leq t \leq 3T$. Given: $V_g(t) = 60 u(t)$ V, $R_g = 25 \Omega$, $Z_0 = 75 \Omega$, $R_L = 300 \Omega$, $u = 1.75 \times 10^8$ m/s, and $l = 525$ m.

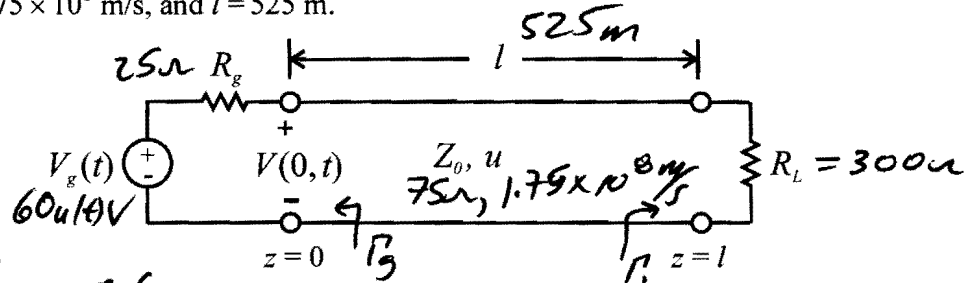

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{300 - 75}{300 + 75} = 0.6 ; \Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0} = \frac{25 - 75}{25 + 75} = -0.5$$

$$T = \frac{l}{u} = \frac{525}{1.75 \times 10^8} = 3 \times 10^{-6} = 3 \mu s$$

$$I_{initial} = \frac{V_g}{R_g + Z_0} = \frac{60}{25 + 75} = 0.6 A ; V_{initial} = V_g \frac{Z_0}{Z_0 + R_g} = \frac{60(75)}{25 + 75} = 45 V$$

$$I_{SS} = \frac{V_g}{R_g + R_L} = \frac{60}{25 + 300} = 0.184615 A ; V_{SS} = V_g \frac{R_L}{R_g + R_L} = \frac{60(300)}{25 + 300} = 58.3846 V$$

$$0 < t < 6 \mu s = V(0,t) = V_{initial} = 45 V \quad 6 \leq t < 12 \mu s \quad V(0,t) = 45 + 27 - 13.5 = 58.5 V$$

$\Gamma_L = 0.6$ $\Gamma_g = -0.5$ $T = 3 \mu s$ Initial current = 0.6 A

Initial voltage = 45 V S.S. current = 0.1846 A S.S. voltage = 58.385 V

