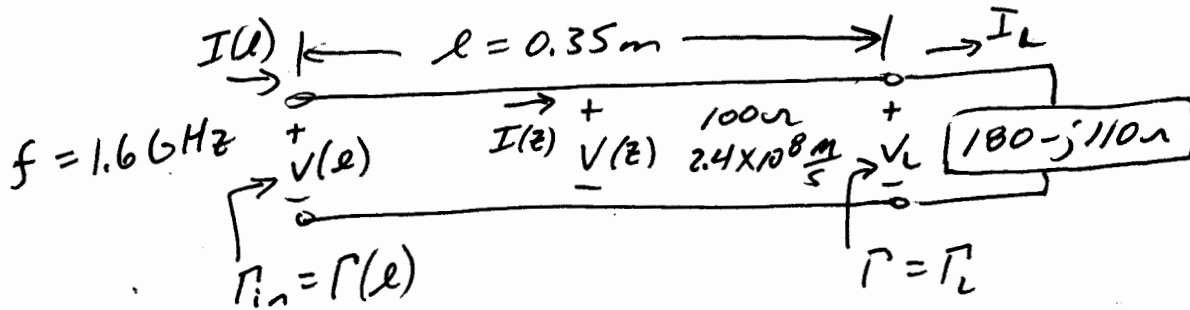


2.3 cont.

15

ex. Calculate various quantities for a lossless TL ($Z_0 = 100\Omega$, $v_p = 2.4 \times 10^8 \text{ m/s}$) of length $l = 0.35 \text{ m}$ terminated in a load $Z_L = 180 - j110\Omega$ operating @ 1.6 GHz w/ $V_0^+ = 10 \angle 40^\circ \text{ V}$ @ $z = 0$.



$$\lambda = \frac{v_p}{f} = \frac{2.4 \times 10^8}{1.6 \times 10^9} = \underline{0.15 \text{ m}}$$

$$\frac{l}{\lambda} = \frac{0.35}{0.15} = \underline{2.33} \leftarrow \text{TL length in terms of } \lambda$$

$$\beta = \frac{2\pi}{\lambda} = \frac{\omega}{v_p} = \frac{2\pi(1.6 \times 10^9)}{2.4 \times 10^8} = \underline{41.8879 \frac{\text{rad}}{\text{m}}}$$

$$\Gamma = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(180 - j110) - 100}{(180 - j110) + 100} = \underline{0.4521 \angle -32.525^\circ}$$

$$\Gamma(l) = \Gamma_{in} = \Gamma e^{-j2\beta l} = (0.4521 \angle -32.525^\circ) e^{-j2(41.89)(0.35)}$$

$$\underline{\Gamma(l) = \Gamma_{in} = 0.4521 \angle 87.475^\circ}$$

$$Z_{in} = Z_0 \left(\frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \right) = 100 \left(\frac{1 + 0.4521 \angle 87.5^\circ}{1 - 0.4521 \angle 87.5^\circ} \right) = \underline{68.3145 + j77.57\Omega}$$

$$RL = -20 \log_{10} 0.4521 = \underline{6.895 \text{ dB}}$$

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.4521}{1 - 0.4521} = \underline{2.6505}$$

Not a good match

ex. cont. Find various voltage-related items

$$V_0^- = V_0^+ \Gamma = (10 \angle 40^\circ)(0.4521 \angle -32.525^\circ) = \underline{4.5213 \angle 7.475^\circ V}$$

$$V_L = V_0^+ e^{-j\beta l} + V_0^- e^{+j\beta l} = (10 \angle 40^\circ) + (4.5213 \angle 7.475^\circ)$$

$$\underline{V_L = 14.0244 \angle 30.018^\circ V}$$

$$V_{\max} = |V_0^+| (1 + |\Gamma|) = (10 \angle 40^\circ) (1 + 0.4521) = \underline{14.521 V}$$

$$V_{\min} = |V_0^+| (1 - |\Gamma|) = 10 (1 - 0.4521) = \underline{5.479 V}$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$\underline{V(z) = (10 \angle 40^\circ) e^{-j41.89z} + (4.52 \angle 7.5^\circ) e^{+j41.89z} V}$$

for $-0.35 \text{ m} \leq z \leq 0$

Find various current-related items

$$I_0^+ = \frac{V_0^+}{Z_0} = \frac{10 \angle 40^\circ}{100} = \underline{0.1 \angle 40^\circ A}$$

$$I_0^- = -\frac{V_0^-}{Z_0} = -\frac{(4.52 \angle 7.5^\circ)}{100} = \underline{0.0452 \angle -172.525^\circ A}$$

$$I_L = I_0^+ e^0 + I_0^- e^0 = (0.1 \angle 40^\circ) + (0.0452 \angle -172.525^\circ)$$

$$\underline{I_L = 0.0665 \angle 61.448^\circ A} \quad (\text{or } I_L = V_L / Z_L)$$

$$I_{\max} = \frac{|V_0^+|}{Z_0} (1 + |\Gamma|) = |I_0^+| (1 + |\Gamma|) = 0.1 (1 + 0.452) = \underline{0.1452 A}$$

$$I_{\min} = |I_0^-| (1 - |\Gamma|) = 0.0452 (1 - 0.452) = \underline{0.0548 A}$$

$$\underline{I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z} = (0.1 \angle 40^\circ) e^{-j41.89z} + (0.0452 \angle -172.5^\circ) e^{+j41.89z} A}$$

$-0.35 \text{ m} \leq z \leq 0$

ex. cont. Find some power-related quantities

$$P_{ave,L} = \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} = 0.5 \operatorname{Re}\{(14.02 \angle 30^\circ)(0.0665 \angle -61.45^\circ)\}$$

$$\underline{P_{ave,L} = 0.3978 \text{ W}}$$

$$P_{avg} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma|^2) = \frac{1}{2} \frac{10^2}{100} (1 - 0.4521^2)$$

$$\underline{P_{avg} = 0.3978 \text{ W}} \quad \text{Same!}$$

$$P_{avg,inc} = P_{avg}^+ = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} = \frac{1}{2} \frac{10^2}{100} = \underline{0.5 \text{ W}}$$

$$P_{avg,ref} = P_{avg}^- = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} |\Gamma|^2 = \frac{1}{2} \frac{10^2}{100} 0.4521^2 = \underline{0.1022 \text{ W}}$$

see following MathCad pages for confirmation of numbers/calculations as well as plots of $|V(z)|$, $|I(z)|$, and $P_{ave}(z)$ for $-0.35 \text{ m} \leq z \leq 0$.

Find location of V_{max} (& I_{min}) closest to load

$$\text{For } V_{max} \text{ (& } I_{min}), \quad \Gamma e^{j2\beta z} = |\Gamma|(1) \Rightarrow |1 \angle -32.525^\circ| e^{j2\beta z} = 1$$

$$e^{j(-32.525 \frac{\pi}{180} + 2(41.888)z)} = e^{j0}$$

$$\hookrightarrow -32.525 \frac{\pi}{180} + 2(41.888)z = 0$$

$$z = 0.006776 \text{ m} \leftarrow \text{NOT possible}$$

$$z = 0.006776 - \lambda/2 = 0.006776 - \frac{0.15}{2}$$

$$\underline{\underline{z = -0.068224 \text{ m}}}$$

Enter given information

$$V_{0p} := 10 \cdot e^{j \cdot 40 \cdot \frac{\pi}{180}} \text{ V} \quad f := 1.6 \cdot 10^9 \text{ Hz} \quad Z_L := 180 - j \cdot 110 \quad \Omega$$

$$l := 0.35 \text{ m} \quad v_p := 2.4 \cdot 10^8 \text{ m/s} \quad Z_0 := 100 \quad \Omega$$

Calculate variables related to transmission line

$$\omega := 2 \cdot \pi \cdot f \quad \lambda := \frac{v_p}{f} \quad \boxed{\lambda = 0.15} \text{ m} \quad l\lambda := \frac{l}{\lambda} \quad \boxed{l\lambda = 2.333}$$

$$\beta := \frac{\omega}{v_p} \quad \boxed{\beta = 41.8879} \text{ rad/m} \quad n := 0..466 \quad z_n := \frac{-n}{466} \cdot l$$

Calculate reflection coefficients, return loss, SWR, & input impedance

$$\Gamma := \frac{Z_L - Z_0}{Z_L + Z_0} \quad \boxed{|\Gamma| = 0.4521} \quad \boxed{\arg(\Gamma) \cdot \frac{180}{\pi} = -32.525} \text{ deg}$$

$$RL := -20 \cdot \log(|\Gamma|) \quad \boxed{RL = 6.895} \text{ dB}$$

$$\Gamma_l := \Gamma \cdot e^{-j \cdot 2 \cdot \beta \cdot l} \quad \boxed{|\Gamma_l| = 0.4521} \quad \boxed{\arg(\Gamma_l) \cdot \frac{180}{\pi} = 87.475} \text{ deg}$$

$$Z_{in} := Z_0 \cdot \frac{(1 + \Gamma_l)}{(1 - \Gamma_l)} \quad \boxed{Z_{in} = 68.3145 + 77.5709i} \quad \Omega$$

$$SWR := \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad \boxed{SWR = 2.6505}$$

Calculate V0m, VL, Vmax, Vmin, & phasor voltage

$$V_{0m} := V_{0p} \cdot \Gamma \quad \boxed{|V_{0m}| = 4.5213} \text{ V} \quad \boxed{\arg(V_{0m}) \cdot \frac{180}{\pi} = 7.475} \text{ deg}$$

$$V_L := V_{0p} + V_{0m} \quad \boxed{|V_L| = 14.0244} \text{ V} \quad \boxed{\arg(V_L) \cdot \frac{180}{\pi} = 30.018} \text{ deg}$$

$$V_n := V_{0p} \cdot e^{-j \cdot \beta \cdot z_n} + V_{0m} \cdot e^{j \cdot \beta \cdot z_n} \quad \text{Phasor voltage versus position along TL.}$$

$$V_{max} := |V_{0p}| \cdot (1 + |\Gamma|) \quad \boxed{V_{max} = 14.5213} \text{ V}$$

$$V_{min} := |V_{0p}| \cdot (1 - |\Gamma|) \quad \boxed{V_{min} = 5.4787} \text{ V} \quad \frac{V_{max}}{V_{min}} = 2.6505$$

Calculate I0p, I0m, IL, Imax, Imin, & phasor current

$$I_{0p} := \frac{V_{0p}}{Z_0} \quad \boxed{|I_{0p}| = 0.1} \quad \text{A} \quad \boxed{\arg(I_{0p}) \cdot \frac{180}{\pi} = 40} \quad \text{deg}$$

$$I_{0m} := \frac{-V_{0m}}{Z_0} \quad \boxed{|I_{0m}| = 0.0452} \quad \text{A} \quad \boxed{\arg(I_{0m}) \cdot \frac{180}{\pi} = -172.525} \quad \text{deg}$$

$$I_L := I_{0p} + I_{0m} \quad \boxed{|I_L| = 0.0665} \quad \text{A} \quad \boxed{\arg(I_L) \cdot \frac{180}{\pi} = 61.448} \quad \text{deg}$$

$$I_{Lalt} := \frac{V_L}{Z_L} \quad \boxed{|I_{Lalt}| = 0.0665} \quad \text{A} \quad \boxed{\arg(I_{Lalt}) \cdot \frac{180}{\pi} = 61.448} \quad \text{deg}$$

$$I_n := \frac{V_{0p}}{Z_0} \cdot e^{-j \cdot \beta \cdot z_n} - \frac{V_{0m}}{Z_0} \cdot e^{j \cdot \beta \cdot z_n} \quad \text{Phasor current versus position along TL.}$$

$$I_{max} := \frac{|V_{0p}|}{Z_0} \cdot (1 + |\Gamma|) \quad \boxed{I_{max} = 0.1452} \quad \text{A}$$

$$I_{min} := \frac{|V_{0p}|}{Z_0} \cdot (1 - |\Gamma|) \quad \boxed{I_{min} = 0.0548} \quad \text{A}$$

Calculate time-average total, incident, & reflected powers


$$P_{avg1} := 0.5 \cdot \text{Re}(V_L \cdot \bar{I}_L) \quad \boxed{P_{avg1} = 0.3978} \quad \text{W}$$

$$P_{avg} := 0.5 \cdot \frac{(|V_{0p}|)^2}{Z_0} \cdot [1 - (|\Gamma|)^2] \quad \boxed{P_{avg} = 0.3978} \quad \text{W}$$


$$P_{avg_inc} := 0.5 \cdot \frac{(|V_{0p}|)^2}{Z_0} \quad \boxed{P_{avg_inc} = 0.5} \quad \text{W}$$

$$P_{avg_ref} := 0.5 \cdot \frac{(|V_{0p}|)^2}{Z_0} \cdot (|\Gamma|)^2 \quad \boxed{P_{avg_ref} = 0.1022} \quad \text{W}$$
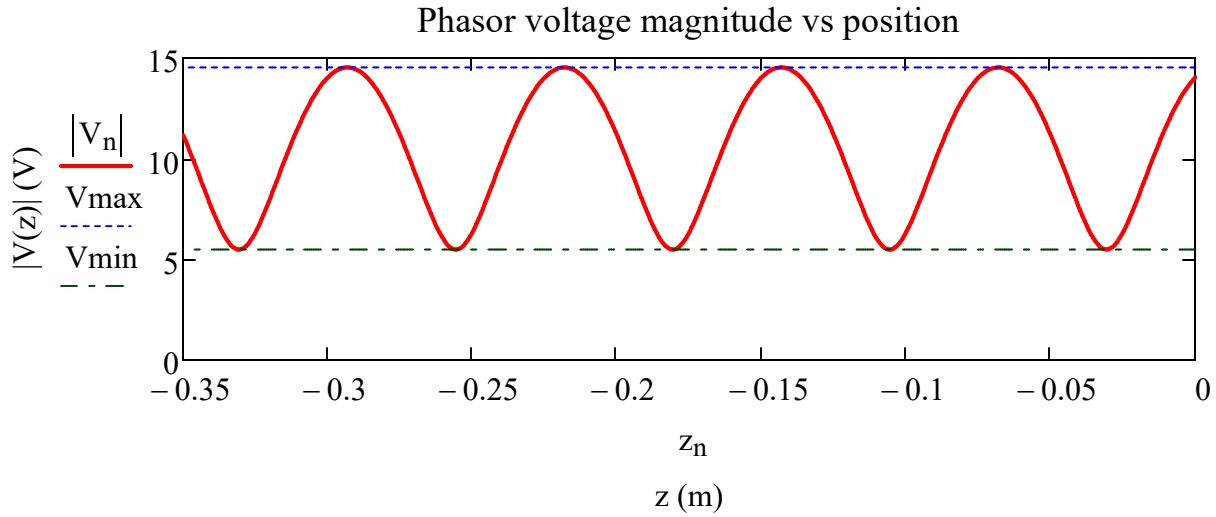
$$P_{ave_n} := 0.5 \cdot \text{Re}(V_n \cdot \bar{I}_n) \quad \text{Check to see if power is really constant.}$$



$$|V_{91}| = 14.521 \text{ V} \quad z_{91} = -0.0683 \text{ m} \quad |V_{41}| = 5.479 \text{ V} \quad z_{41} = -0.0308 \text{ m}$$

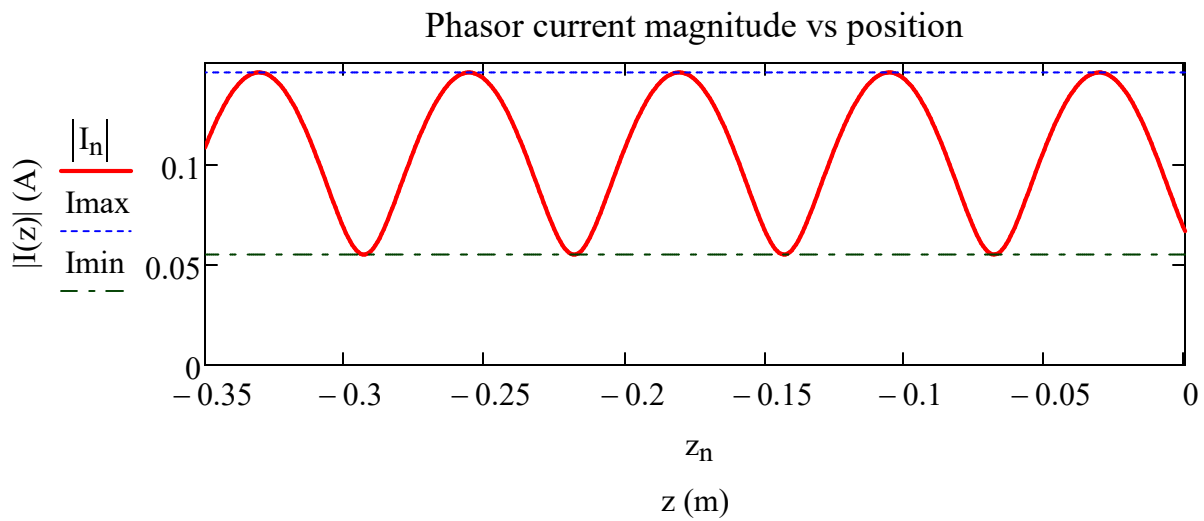

$$|I_{41}| = 0.145 \text{ A} \quad z_{41} = -0.0308 \text{ m} \quad |I_{91}| = 0.0548 \text{ A} \quad z_{91} = -0.0683 \text{ m}$$

