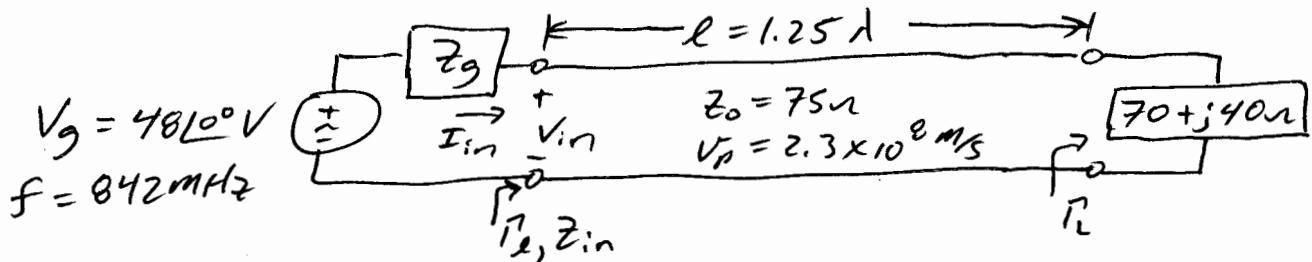


2.6 cont.

ex. Find powers and related quantities for various match conditions for the circuit shown.



$$V_g := 48 \cdot e^{j \cdot 0 \cdot \frac{\pi}{180}} \quad V \quad f := 842 \cdot 10^6 \quad \text{Hz} \quad Z_L := 70 + j \cdot 40 \quad \Omega$$

$$l\lambda := 1.25 \quad v_p := 2.3 \cdot 10^8 \quad \text{m/s} \quad Z_0 := 75 \quad \Omega$$

### Calculate variables related to transmission line

$$\omega := 2 \cdot \pi \cdot f \quad \lambda := \frac{v_p}{f} \quad \boxed{\lambda = 0.273} \quad \text{m} \quad l := l\lambda \cdot \lambda \quad \boxed{l = 0.3414} \quad \text{m}$$

$$\beta := \frac{\omega}{v_p} \quad \boxed{\beta = 23.0019} \quad \text{rad/m}$$

### Calculate reflection coefficients & input impedance

$$\Gamma_L := \frac{Z_L - Z_0}{Z_L + Z_0} \quad \boxed{|\Gamma_L| = 0.268} \quad \arg(\Gamma_L) \cdot \frac{180}{\pi} = 81.703 \quad \text{deg}$$

$$\Gamma_l := \Gamma_L \cdot e^{-j \cdot 2 \cdot \beta \cdot l} \quad \boxed{|\Gamma_l| = 0.268} \quad \arg(\Gamma_l) \cdot \frac{180}{\pi} = -98.297 \quad \text{deg}$$

$$Z_{in} := Z_0 \cdot \frac{(1 + \Gamma_l)}{(1 - \Gamma_l)} \quad \boxed{Z_{in} = 60.5769 - 34.6154i} \quad \Omega$$

1) Assume we used matching network on load & matched source, i.e.,  $Z_g = Z_{in} = Z_0$  and  $\Gamma_{L1} = 0$ .

$$\Gamma_{L1} := 0 \quad Z_{in1} := Z_0 \quad Z_{g1} := Z_0$$

$$V_{in1} := V_g \cdot \left( \frac{Z_{in1}}{Z_{in1} + Z_{g1}} \right) \quad \boxed{|V_{in1}| = 24} \quad V \quad \arg(V_{in1}) \cdot \frac{180}{\pi} = 0 \quad \text{deg}$$

$$V_{0p1} := \frac{V_{in1}}{e^{j \cdot \beta \cdot l} + \Gamma_{L1} \cdot e^{-j \cdot \beta \cdot l}} \quad \boxed{|V_{0p1}| = 24} \quad V \quad \arg(V_{0p1}) \cdot \frac{180}{\pi} = -90 \quad \text{deg}$$

$$I_{in1} := \frac{V_{in1}}{Z_{in1}} \quad \boxed{|I_{in1}| = 0.32} \quad A \quad \arg(I_{in1}) \cdot \frac{180}{\pi} = 0 \quad \text{deg}$$

$$Pin1 := 0.5 \cdot \operatorname{Re}(Vin1 \cdot \overline{Iin1}) \quad Pavg1 := 0.5 \cdot \frac{(|V0p1|)^2}{Z0} \cdot [1 - (|\Gamma L1|)^2] \quad P1 := \frac{(|Vg|)^2}{8 \cdot Z0}$$

$$\boxed{Pin1 = 3.84} \quad W \quad \boxed{Pavg1 = 3.84} \quad W \quad \boxed{P1 = 3.84} \quad W$$

$$Pavg\_inc1 := 0.5 \cdot \frac{(|V0p1|)^2}{Z0} \quad \boxed{Pavg\_inc1 = 3.84} \quad W$$

$$Pavg\_refl1 := 0.5 \cdot \frac{(|V0p1|)^2}{Z0} \cdot (|\Gamma L1|)^2 \quad \boxed{Pavg\_refl1 = 0} \quad W$$

$$PVg1 := 0.5 \cdot \operatorname{Re}(Vg \cdot \overline{Iin1}) \quad \boxed{PVg1 = 7.68} \quad W$$

$$VSWR1 := \frac{1 + |\Gamma L1|}{1 - |\Gamma L1|} \quad \boxed{VSWR1 = 1}$$

$$RL1 = 20 \log(0) = \infty \quad \eta1 := \frac{P1}{PVg1} \quad \boxed{\eta1 \cdot 100 = 50} \quad \%$$

## 2) Choose $Zg = Zin$ .

$$Zg2 := Zin \quad \boxed{Zg2 = 60.577 - 34.615i} \quad \Omega \quad Rg2 := \operatorname{Re}(Zg2) \quad Xg2 := \operatorname{Im}(Zg2)$$

$$Vin2 := Vg \cdot \left( \frac{Zin}{Zin + Zg2} \right) \quad \boxed{Vin2 = 24} \quad V \quad \arg(Vin2) \cdot \frac{180}{\pi} = 0 \quad \text{deg}$$

$$V0p2 := \frac{Vin2}{e^{j \cdot \beta \cdot l} + \Gamma L \cdot e^{-j \cdot \beta \cdot l}} \quad \boxed{|V0p2| = 24.067} \quad V \quad \arg(V0p2) \cdot \frac{180}{\pi} = -74.58 \quad \text{deg}$$

$$Iin2 := \frac{Vin2}{Zin} \quad \boxed{|Iin2| = 0.344} \quad A \quad \arg(Iin2) \cdot \frac{180}{\pi} = 29.745 \quad \text{deg}$$

$$Pin2 := 0.5 \cdot \operatorname{Re}(Vin2 \cdot \overline{Iin2}) \quad P2 := \frac{(|Vg|)^2}{8} \cdot \frac{Rg2}{Rg2^2 + Xg2^2}$$

$$\boxed{Pin2 = 3.584} \quad W \quad \boxed{P2 = 3.584} \quad W$$

$$Pavg\_inc2 := 0.5 \cdot \frac{(|V0p2|)^2}{Z0} \quad \boxed{Pavg\_inc2 = 3.8613} \quad W$$

$$Pavg\_refl2 := 0.5 \cdot \frac{(|V0p2|)^2}{Z0} \cdot (|\Gamma L|)^2 \quad \boxed{Pavg\_refl2 = 0.2773} \quad W$$

$$PVg2 := 0.5 \cdot \operatorname{Re}(Vg \cdot \overline{Iin2}) \quad \boxed{PVg2 = 7.168} \quad W$$

$$\text{VSWR2} := \frac{1 + |\Gamma L|}{1 - |\Gamma L|}$$

VSWR2 = 1.732

$$\text{RL2} := 20 \cdot \log(|\Gamma L|)$$

RL2 = -11.437 dB

$$\eta_2 := \frac{P2}{PVg2}$$

η2 · 100 = 50 %

### 3) Choose $Z_g = Z_{in^*}$ .

$$Zg3 := \overline{Z_{in}}$$

Zg3 = 60.577 + 34.615i Ω

$$Rg3 := \text{Re}(Zg3) \quad Xg3 := \text{Im}(Zg3)$$

$$Vin3 := Vg \cdot \left( \frac{Z_{in}}{Z_{in} + Zg3} \right)$$

Vin3 = 27.642 V

arg(Vin3) ·  $\frac{180}{\pi} = -29.74$  deg

$$V0p3 := \frac{Vin3}{e^{j \cdot \beta \cdot l} + \Gamma L \cdot e^{-j \cdot \beta \cdot l}}$$

|V0p3| = 27.719 V

arg(V0p3) ·  $\frac{180}{\pi} = -104.32$  deg

$$Iin3 := \frac{Vin3}{Z_{in}}$$

|Iin3| = 0.3962 A

arg(Iin3) ·  $\frac{180}{\pi} = 0$  deg

$$Pin3 := 0.5 \cdot \text{Re}(Vin3 \cdot \overline{Iin3})$$

P3 :=  $\frac{(|Vg|)^2}{8 \cdot Rg3}$

$$Pin3 = 4.7543 W$$

P3 = 4.7543 W

$$Pavg\_inc3 := 0.5 \cdot \frac{(|V0p3|)^2}{Z_0}$$

Pavg\_inc3 = 5.1222 W

$$Pavg\_refl3 := 0.5 \cdot \frac{(|V0p3|)^2}{Z_0} \cdot (|\Gamma L|)^2$$

Pavg\_refl3 = 0.3679 W

$$PVg3 := 0.5 \cdot \text{Re}(Vg \cdot \overline{Iin3})$$

PVg3 = 9.5086 W

$$\text{VSWR3} := \frac{1 + |\Gamma L|}{1 - |\Gamma L|}$$

VSWR3 = 1.732

$$\text{RL3} := 20 \cdot \log(|\Gamma L|)$$

RL3 = -11.437 dB

$$\eta_3 := \frac{P3}{PVg3}$$

η3 · 100 = 50 %

$P_3 = 4.754 W > P_1 = 3.84 W > P_2 = 3.584 W$   
 $VSWR = 1.73$        $VSWR = 1.73$   
 $\eta = 50\% \text{ in all cases.}$