## EE 481/581 Microwave Engineering Examination #1 (Fall 2024)

Name <mark>KEY</mark>

Instructions: Place answers in indicated spaces, use notation as given in class, and show/explain all work for credit. All Smith charts should be fully labeled. Turn-in equation sheet(s) with exam.

1) A material has a relative permittivity of 8 and a loss tangent of 0.03 at 3 GHz. Determine the complex permittivity and effective conductivity of the material at 3 GHz. A 3 GHz plane wave propagates through this material in the +x-direction. Find the propagation constant, phase velocity, wavelength, skin depth, and intrinsic impedance. The electric field has an amplitude of 16 V/m at x = 0 and is oriented in the +z-direction, write the equation for the phasor vector electric field.

$$\begin{aligned} \tan \delta &= \frac{\sigma}{\omega_{er}} = 0.03 \quad \text{and} \quad \epsilon_{r} = \frac{e_{r}}{\epsilon_{0}} = 8, \\ Assume \quad \mathcal{M} = \mathcal{M}_{0} \quad (mon - magnet.c) \\ Notes : \quad \epsilon' = \epsilon_{r} \epsilon_{0} = 8(8.954/878\times10^{-12}) = 70.8335 \times10^{-12} \text{m} \\ \epsilon'' = \epsilon' \tan \delta = 70.8335 \times10^{-12}(0.03) = 2.125005 \times10^{12} \text{fm} \\ \epsilon_{c} = \epsilon' - 1 \epsilon'' = 70.8335 - \frac{1}{2}2.(25 \text{ p}^{f}/\text{m}) \\ \epsilon_{c} = \epsilon' - 1 \epsilon'' = 70.8335 - \frac{1}{2}2.(25 \text{ p}^{f}/\text{m}) \\ \epsilon_{c} = \epsilon' - 1 \epsilon'' = 70.8335 - \frac{1}{2}2.(25 \text{ p}^{f}/\text{m}) \\ \epsilon_{c} = \epsilon' - 1 \epsilon'' = 70.8335 - \frac{1}{2}2.(25 \text{ p}^{f}/\text{m}) \\ \epsilon_{c} = \epsilon' - 1 \epsilon'' = 70.8335 - \frac{1}{2}2.(25 \text{ p}^{f}/\text{m}) \\ \epsilon_{c} = \epsilon' - 1 \epsilon'' = 70.8335 - \frac{1}{2}2.(25 \text{ p}^{f}/\text{m}) \\ \epsilon_{c} = \epsilon' - 1 \epsilon'' = 70.8335 - \frac{1}{2}2.(25 \text{ p}^{f}/\text{m}) \\ \epsilon_{c} = \epsilon' - 1 \epsilon'' = 70.8335 - \frac{1}{2}2.(25 \text{ p}^{f}/\text{m}) \\ \epsilon_{c} = \epsilon' - 1 \epsilon'' = 70.8335 - \frac{1}{2}2.(25 \text{ p}^{f}/\text{m}) \\ \epsilon_{c} = 1 \epsilon' - 1 \epsilon'' = 2\pi (3 \times 10^{9}) (79.8585 \times 10^{-12} - 0.040055 \text{ s}/\text{m}) \\ \epsilon_{c} = 2\pi (3 \times 10^{9}) (79.8585 \times 10^{-12} - 10.040055 \text{ s}/\text{m}) \\ \epsilon_{c} = 2.667275 + \frac{1}{2} (77.8585 \times 10^{-12} - 10.038 \text{ m}) \\ \epsilon_{c} = 2.6677275 + \frac{1}{2} (77.858 \times 10^{-12} - 10.038 \text{ m}) \\ \epsilon_{c} = 2.77/187.858 = 0.0353277 \text{ m} \\ \epsilon_{c} = 2.77/187.858 = 0.37491 \text{ m} \\ r_{c} = \frac{1}{2.667} + \frac{1}{2.77.858} = 133.14936 + \frac{1}{1.9916791} \\ \epsilon_{c} = \frac{1}{2.667} + \frac{1}{1.77.858} \text{ m} \\ roopen \text{ prop. const.} = \frac{2.6677}{2.667} + \frac{1}{2.77.858} \text{ m} \\ root = \frac{1.006 \times 10^{8} \text{ m}}{1.068 \text{ m}} \text{ s} \text{ s} = \frac{3.2332 \text{ cm}}{1.068 \text{ m}} \\ skin depth = \frac{37.49 \text{ cm}}{37.49 \text{ cm}} \text{ intr. imped.} = \frac{133.15 + \frac{1}{1.99771} \text{ a} \epsilon = \frac{2}{2}16e^{-(2.467+\frac{1}{177.91})} \\ \epsilon_{c} / \frac{1}{2} + \frac{1}{2$$

2) A two-wire transmission line (TL) is made using a platinum-gold alloy ( $\varepsilon_0$ ,  $\mu_0$ ,  $\sigma = 1.3 \times 10^7$  S/m) for the conductors and a plastic for the insulator ( $\varepsilon_r = 1.4$ ,  $\mu_0$ , tan  $\delta = 0.003$ ) for operation at 4 GHz. If the conductors have diameters of 3 mm and are separated center-to-center by 12 mm respectively, find the complex permittivity of the insulator, the distributed parameters *R*, *L*, *G*, & *C*, and characteristic impedance of the transmission line.

$$\begin{aligned} \varepsilon' &= \varepsilon_{r} \varepsilon_{o} = 1.4(8.8542 \times 10^{-12}) = 12.396 \times 10^{-12} F_{m} \\ \varepsilon'' &= \varepsilon' + \sigma_{0} f = 12.396 \times 10^{-12} / (0.003) = 0.037/89 \times 10^{-12} F_{m} \\ \varepsilon_{c} &= \varepsilon' - 5 \varepsilon'' = 12.396 - 5 0.0372 PF_{m} \\ (1.60) f_{s} &= \sqrt{\frac{2}{\omega_{M}\sigma_{c}}} = \sqrt{\frac{2}{2\pi(4\pi/0^{9})(4\pi\times10^{-9})(1.3\pi/0^{-7})}} = 2.20703 \times 10^{6} m \\ A_{s} &= \frac{1}{0} + \frac{1}{1.3\times10^{2}(2.207\times0^{-6})} = 0.034853 n \\ Table 2.1 \\ M &= \frac{M_{s}}{\pi\pi} = \frac{0.034853}{\pi(3\pi/0^{3}/2)} = \frac{7.396}{\pi} \frac{5}{000} \\ L &= \frac{M_{0}}{\pi} \cosh^{-1}(\frac{d}{2\pi}) = \frac{4\pi\times10^{-7}}{\pi} \cosh^{-1}(\frac{12}{3}) = 8.25375 \times 10^{-7} H_{c} \\ G &= \frac{\pi\omega}{\cosh^{-1}(d/2\pi)} = \frac{\pi(2\pi)^{4}\times10^{9}(3.7198\times10^{-12})}{\cosh^{-1}(12/3)} = 1.42297 \times 10^{-3} S_{m} \\ C &= \frac{\pi\varepsilon}{\cosh^{-1}(d/2\pi)} = \frac{\pi(2\pi)^{4}\times10^{9}(3.7198\times10^{-12})}{\cosh^{-1}(12/3)} = \frac{18.8728 \times 10^{-12} F_{m}}{6} \\ Z.7) Z_{0} &= \sqrt{\frac{7.396}{6+5}\omega c} = \sqrt{\frac{7.396}{1.4723}\times10^{-3}+5} 2\pi(4\pi/0^{9})(8.873\times0^{-12})} \\ Z_{0} &= 207.1253 + 50.276407 \\ \end{array}$$



3) A generator ( $V_g = 16 \angle 0^\circ V$ ,  $Z_g = 300 \Omega$ ) operating at 3 GHz drives a lossless TL ( $300 \Omega$ ,  $2.1 \times 10^8$  m/s) of length 9.6 cm connected to a  $60 + j120 \Omega$  load. Using a Smith chart, find the <u>unmatched</u> input impedance and power delivered to the load. Then, design and sketch (fully labeled) a shunt single inductor matching network. Place the inductor as close as possible to the load. Find the <u>matched</u> input impedance and power delivered to the load.

$$\begin{split} \lambda = \frac{V_{F}}{S} = \frac{2.1 \times 10^{8}}{3 \times 10^{9}} = 0.07 \text{ m} = 7 \text{ cm} \qquad P_{A} = \frac{9.6}{7} = 1.3714 \Rightarrow 0.3714 \\ \Rightarrow g_{L} = \frac{2}{20} = \frac{60 + j120}{300} = 0.2 + j0.4 \ \% \in 1/0t \text{ on } \text{Smith Cht} \\ \Rightarrow Move 0.3714 WTG on circle of constant /(11/to) \\ \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & \exists in, NM = 0.205 - j0.425 \ \%. \\ & = 0.205 - j127.5 \ = 0.04174 \ M. \\ & = 0.04174 \ M. \ M = \frac{10}{20 + 2.000} \ M = \frac{10}{300 + 615 - j127.5} \ = 0.04174 \ M. \ M = \frac{10}{20 + 2.000} \ M = \frac{10}{20 + 2$$

 $Z_{in,M} = 300 r$ 

PL,M= 106.67 mW



4) A lossless 40  $\Omega$  microstrip TL ( $v_p = 2.25 \times 10^8$  m/s) is terminated by a load with reflection coefficient  $0.6 \angle 114^\circ \Omega$  at 1.5 GHz. Find the load impedance and SWR as well as the maximum and minimum impedances along the <u>unmatched</u> TL. Using a Smith chart, design a quarter-wave transformer (QWT) to match the load to the TL. Place the QWT as close as possible to the load. Assume the QWT section has a phase velocity of  $2.3 \times 10^8$  m/s. Sketch the fully labeled result in box provided.

$$= \int_{1}^{1} \int_{1}^{1} = 0.6 \text{ circle on Smith Cht}$$

$$= \int_{1}^{1} \int_{1}^{1} = 0.6 \text{ circle on Smith Cht}$$

$$= \int_{1}^{1} \int_{1}^{1}$$





## EE 481/581 Microwave Engineering Examination #1R (Fall 2024)

Name <u>KEY R</u>

- Instructions: Place answers in indicated spaces, use notation as given in class, and show/explain all work for credit. Smith chart should be clearly & fully labeled. Turn-in equation sheet(s) with this work.
- 1) Problem to replace (i.e, 1, 2, 3, or 4).
- 2) (20 points) A generator ( $V_g = 8 \angle 0^\circ \text{ V}$ ,  $Z_g = 50 \Omega$ ) operating at 600 MHz drives a lossless TL (50  $\Omega$ ,  $2.4 \times 10^8 \text{ m/s}$ ) of length 130.8 cm connected to a load with a reflection coefficient  $0.62 \angle 97.1^\circ$ . Using a Smith chart, find the load impedance  $Z_L$  and the <u>unmatched</u> input impedance  $Z_{\text{in,NM}}$ , reflection coefficient  $\Gamma_{\text{in,NM}}$ , and SWR. Also, calculate the time-average power delivered to the load  $P_{L,\text{NM}}$  without matching.

 $\blacktriangleright$  Wavelength  $\lambda = v_p/f = 2.4 \times 10^8/600 \times 10^6 \Rightarrow \lambda = 0.4 \text{ m} = 40 \text{ cm}.$ 

## Smith chart steps

1) Plot  $\Gamma_L = 0.62 \angle 97.1^\circ$  on Smith chart.

- 2) Read  $z_L = 0.4 + j \ 0.8 \ \Omega/\Omega$ . Compute  $Z_L = Z_0 \ z_L = 50 \ (0.4 + j \ 0.8) \Rightarrow Z_L = 20 + j \ 40 \ \Omega$ .
- 3) Draw circle, centered on Smith chart, through  $\Gamma_L/z_L$  point and arc on SWR scale. Read <u>SWR = 4.25</u>.
- 4) Calculate  $\ell/\lambda = 130.8/40 = 3.27 \implies$  move 0.27 $\lambda$  toward generator on arc of constant

 $|\Gamma|$  to arrive at  $z_{in,NM}$  and  $\Gamma_{in,NM}$  point. Since 0.115+0.27=0.385, draw radial line from center of Smith chart to 0.385 on the "WAVELENGTHS TOWARD GENERATOR" scale.

5) Read  $z_{in,NM} = 0.4 - j \ 0.8 \ \Omega/\Omega$  and  $\Gamma_{in,NM} = 0.62 \angle -97.3^{\circ}$ . Compute  $Z_{in,NM} = Z_0 \ z_{in,NM} = 50 \ (0.4 - j \ 0.8) \implies Z_{in,NM} = 20 - j \ 40 \ \Omega$ .

Use circuit analysis to compute  $P_{in,NM} = P_{L,NM}$  (lossless TL).

$$I_{0,\text{NM}} = V_g / (Z_g + Z_{\text{in,NM}}) = 8 \angle 0^\circ / (50 + 20 - j \, 40) = 0.099227788 \angle 29.745^\circ \text{ A}$$

$$P_{\text{in,NM}} = 0.5 | I_{0,\text{NM}} |^2 R_{\text{in,NM}} = 0.5 | 0.099228 |^2 20$$
  
$$\Rightarrow \underline{P_{\text{in,NM}}} = \underline{P_{L,\text{NM}}} = 0.0984615 \text{ W} = 98.4615 \text{ mW}.$$

Not matched

 $Z_L = 20 + j \, 40 \, \Omega$   $Z_{in,NM} = 20 - j \, 40 \, \Omega$ 

 $\Gamma_{\text{in,NM}} = \underline{0.62 \angle -97.3^{\circ}}_{\text{SWR}} = \underline{4.25}_{\text{P}_{L,NM}} = \underline{0.0984615 \text{ W}} = \underline{98.4615 \text{ mW}}_{\text{SWR}}$ 

Design and sketch (fully labeled) a matching network using a **shunt single capacitor** *C* placed at a distance d (cm) as close as possible to the load. As part of the process, determine the normalized load admittance  $y_L$  and appropriate match point admittance  $y_M$ . Find the power delivered to the load after matching  $P_{L,M}$ .

- 6) Move 180° around circle of constant  $|\Gamma|$  to arrive at  $y_L = 0.5 j1 S/S$ .
- 7) The two points are  $y_{m,i} = 1 \pm j1.58$  S/S. Choose  $y_{m,2} = 1 j1.58$  S/S (inductive y) to match with a shunt capacitor.
- 8) The distance in "WAVELENGTHS TOWARD GENERATOR" from  $y_L$  to  $y_{m,2}$  is  $d = 0.135 + 0.322 \implies d = 0.457\lambda = 0.457(40) = 18.28 \text{ cm}$ .
- 9) At  $y_{m,2}$  add a shunt capacitor with susceptance  $Y_{cap} = j1.58/50 \text{ S} = j\omega C$ . Solving for  $C = 1.58/(2\pi 600 \times 10^6 50) \Rightarrow C = 8.38216 \text{ pF}$ .

After matching,  $Z_{in,M} = Z_0 = 50 \Omega$ . Use circuit analysis to compute  $P_{in,M} = P_{L,M}$  (lossless TL).

$$I_{0,M} = V_g / (Z_g + Z_{in,M}) = 8 \angle 0^\circ / (50 + 50) = 0.08 \angle 0^\circ A$$

$$P_{\text{in},M} = 0.5 | I_{0,M} |^2 R_{\text{in},M} = 0.5 | 0.08 |^2 50 \implies \underline{P_{\text{in},M} = P_{L,M} = 0.16 \text{ W} = 160 \text{ mW}}.$$

$$y_L = \_0.5 - j1 \ S/S$$
  $y_M = \_1 - j1.58 \ S/S$ 



**Matched-**  $P_{L,M} = 0.16 \text{ W} = 160 \text{ mW}$ 

