

EE 481/581 Microwave Engineering Examination #3 (Fall 2024)

Name

Key

Instructions: Place answers in indicated spaces, use notation as given in class, and show/explain all work (including that on design figures/tables) for credit. Turn-in equation sheet(s) with exam.

- 1) For a $75\ \Omega$ system connected port 1, design a Wilkinson power divider to operate at 1.499 GHz where $3/5$ of the power input into Port 1 goes to Port 2 and $2/5$ of the power input into Port 1 goes to Port 3. First, assuming all the transmission lines use an air dielectric, find the phase velocity and wavelength. Then, find and fill-in all values indicated on the figure.

For air dielectric, $v_p = c = \underline{2.9979 \times 10^8\ \text{m/s}}$

$$\lambda = \frac{c}{f} = \frac{2.9979 \times 10^8}{1.499 \times 10^9} = \underline{0.2000\ \text{m}}$$

$$0.332, \quad k^2 = P_3/P_2 = \frac{0.4P_1}{0.6P_1} = \frac{2}{3} = 0.66 \Rightarrow k = \underline{0.8165}$$

$$(7.37a) \quad Z_{03} = Z_0 \sqrt{\frac{1+k^2}{k^3}} = 75 \sqrt{\frac{1+2/3}{0.8165^3}} = \underline{131.2363\ \Omega}$$

$$(7.37b) \quad Z_{02} = k^2 Z_{03} = \frac{2}{3} (131.2363) = \underline{87.4909\ \Omega}$$

$$(7.37c) \quad R = Z_0 \left(k + \frac{1}{k} \right) = 75 \left(0.8165 + \frac{1}{0.8165} \right) = \underline{153.0931\ \Omega}$$


Per F.g 7.8, the arm lengths are $\lambda/4 \Rightarrow l_2 = l_3 = \frac{0.2}{4} = \underline{0.05\ \text{m}}$

Per F.g 7.13, $Z_{01} = Z_0 = 75\ \Omega$

$$R_2 = Z_{01} k = 75 (0.8165) = \underline{61.2372\ \Omega}$$


$$R_3 = Z_{01} / k = 75 / 0.8165 = \underline{91.855065\ \Omega}$$

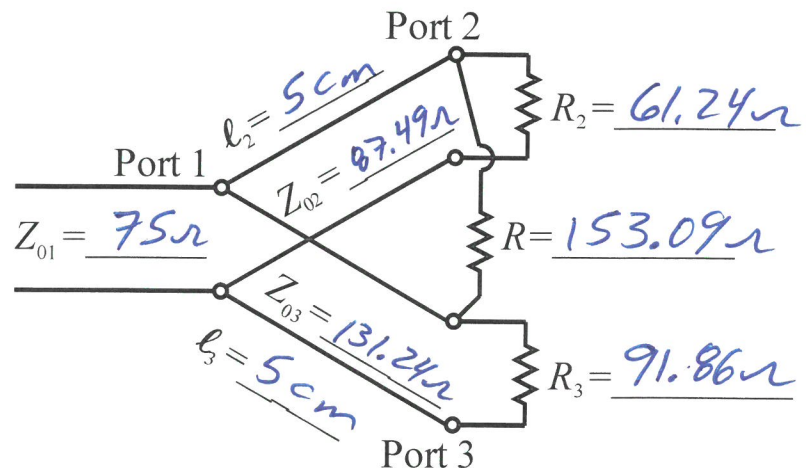phase velocity = $2.9979 \times 10^8\ \text{m/s}$ wavelength = $0.2\ \text{m}$



- 2) Design the lowest-order, maximally flat, lumped-element, **high-pass filter** (HPF) with a cutoff frequency of 2 GHz having at least 28 dB of attenuation at 1 GHz for use in a 75Ω system. First, determine the order N and the low-pass prototype immittance values g_0 to g_{N+1} . Then, find the component values and draw a fully labeled sketch of the HPF. Minimize the use of inductors in the final design.

For LPF prototype, $|\frac{\omega}{\omega_c}| - 1 = |\frac{2}{1}| - 1 = 1$. Plot on Fig 8.26 along w/ 28 dB attenuation. Need $N=5$,
 Per HPF transformation $L \rightarrow C$ and $C \rightarrow L$. To minimize inductors in HPE, choose LPF architecture of Fig 8.25b

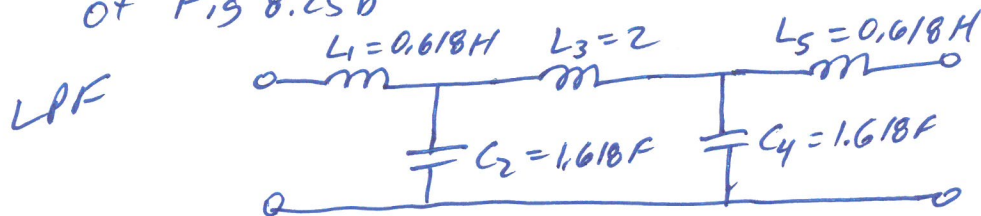

$$\underline{R_0 = 75 \Omega} \quad \& \quad \underline{\omega_c = 2\pi(2 \times 10^9) \text{ rad/s}}$$

$$N = \underline{5}$$

immittances: $\underline{g_0=1, g_1=0.618, g_2=1.618, g_3=2, g_4=1.618, g_5=0.618}$
 $\underline{+g_6=1}$

Per (8.70a), the series capacitors which replace

The series inductors are $C_{1c}' = \frac{1}{R_0 \omega_c L_{1c}}$

$$C_1' = C_5' = \frac{1}{75(2\pi)2 \times 10^9(0.618)} = \underline{1.716882 \text{ pF}}$$

$$C_3' = \frac{1}{75(2\pi)2 \times 10^9(2)} = \underline{0.5305165 \text{ pF}}$$

Per (8.70b), the shunt inductors which replace

the shunt capacitors are $L_{1c}' = \frac{R_0}{\omega_c C_{1c}}$

$$L_2' = L_4' = \frac{75}{2\pi(2 \times 10^9)(1.618)} = \underline{3.688696 \text{ nH}}$$

$$R_s = R_L = 75(1) = \underline{75 \Omega} \quad \text{per (8.64c) \& (8.64d)}$$

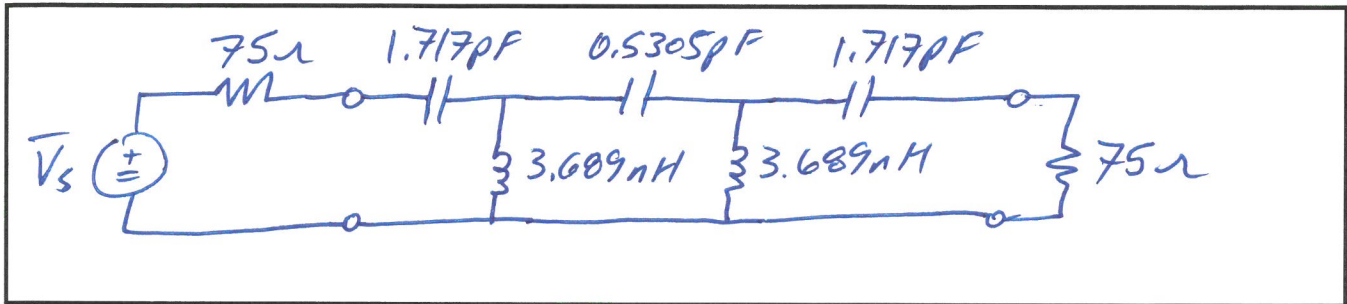


TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

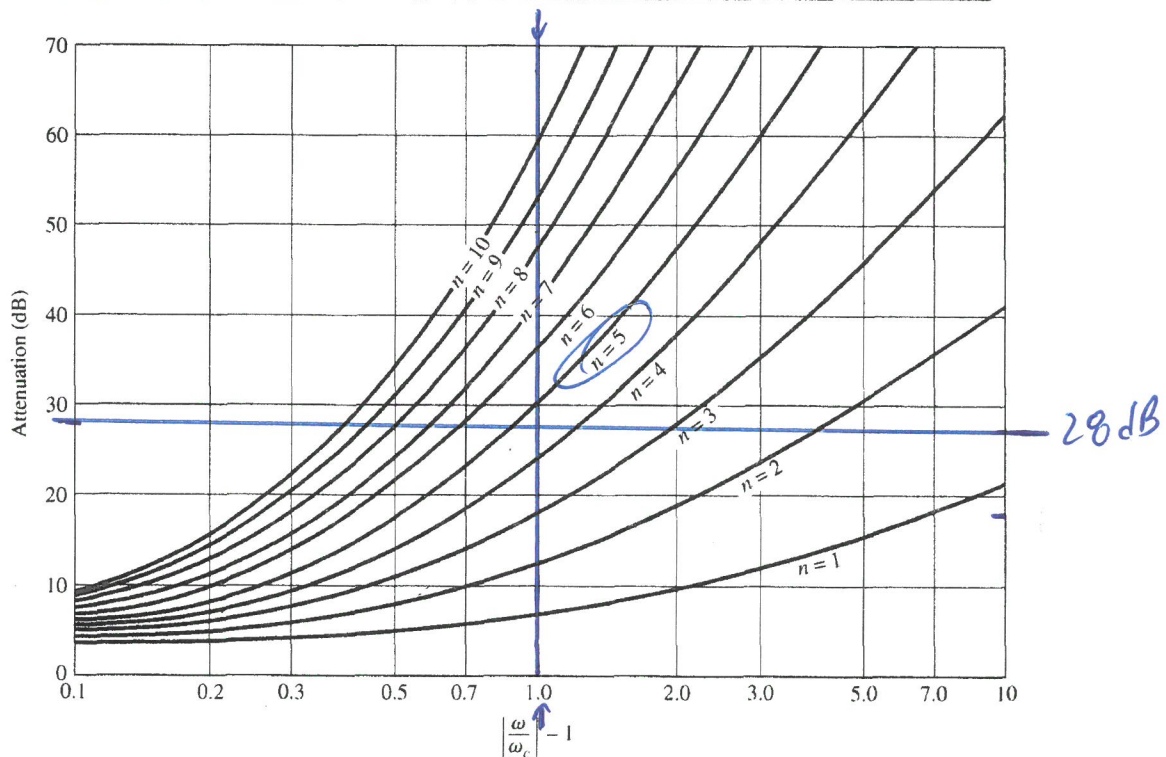


FIGURE 8.26

Attenuation versus normalized frequency for maximally flat filter prototypes.

Adapted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

- 3) A directional coupler has the $[S]$ -matrix shown below. In **decibels**, determine the return loss, coupling factor, directivity, isolation, and insertion loss.

$$[S] = \begin{bmatrix} 0.08 \angle 16^\circ & 0.96 \angle 88^\circ & 0.2 \angle 180^\circ & 0.006 \angle 90^\circ \\ 0.96 \angle 88^\circ & 0.08 \angle 16^\circ & 0.006 \angle 90^\circ & 0.2 \angle 180^\circ \\ \underline{0.2 \angle 180^\circ} & 0.006 \angle 90^\circ & 0.08 \angle 16^\circ & 0.96 \angle 88^\circ \\ \underline{0.006 \angle 90^\circ} & 0.2 \angle 180^\circ & 0.96 \angle 88^\circ & 0.08 \angle 16^\circ \end{bmatrix}$$

Per (2.38), $RL = -20 \log |F| = -20 \log |S_{11}|$ $S_{11} = 0.08 \angle 16^\circ$
 $= -20 \log (0.08) = \underline{21.9382 \text{ dB}}$

Coupling (7.20a), $C = -20 \log \beta = -20 \log |S_{13}|$ $S_{13} = 0.2 \angle 180^\circ$
 $= -20 \log 0.2 = \underline{13.9794 \text{ dB}}$

Directivity (7.20b), $D = 20 \log \frac{\beta}{|S_{14}|} = 20 \log \frac{|S_{13}|}{|S_{14}|}$ $S_{14} = 0.006 \angle 90^\circ$
 $= 20 \log \frac{0.2}{0.006} = \underline{30.4576 \text{ dB}}$

Isolation (7.20c), $I = -20 \log |S_{14}|$
 $= -20 \log 0.006 = \underline{44.438975 \text{ dB}}$

Insertion loss (7.20d), $IL = -20 \log |S_{12}|$ $S_{12} = 0.96 \angle 88^\circ$
 $= -20 \log 0.96 = \underline{0.3546 \text{ dB}}$

return loss = 21.938 dB coupling factor = 13.979 dB directivity = 30.458 dB
isolation = 44.437 dB insertion loss = 0.355 dB

- 4) Design a third-order, 0.5 dB equal-ripple, lumped-element, **low-pass filter** prototype using the architecture of Figure 8.25b (use Thevenin equivalent source) and draw a fully labeled sketch in the appropriate box. Then, use Richards's transformation to implement the filter using series/shunt open/short-circuit stubs and draw a fully labeled sketch in the appropriate box. The lengths ℓ may be left in terms of λ at f_c .

TABLE 8.4 Element Values for Equal-Ripple Low-Pass Filter Prototypes ($g_0 = 1, \omega_c = 1, N = 1$ to 10, 0.5 dB ripple)

N	0.5 dB Ripple										
	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

$$L_1 = g_1 = 1.5963 H$$


$$R_0 = g_0 = 1 \Omega$$

$$C_2 = g_2 = 1.0967 F$$

$$R_L = g_4 = 1 \Omega$$

$$L_3 = g_3 = 1.5963 H$$

low-pass filter prototype

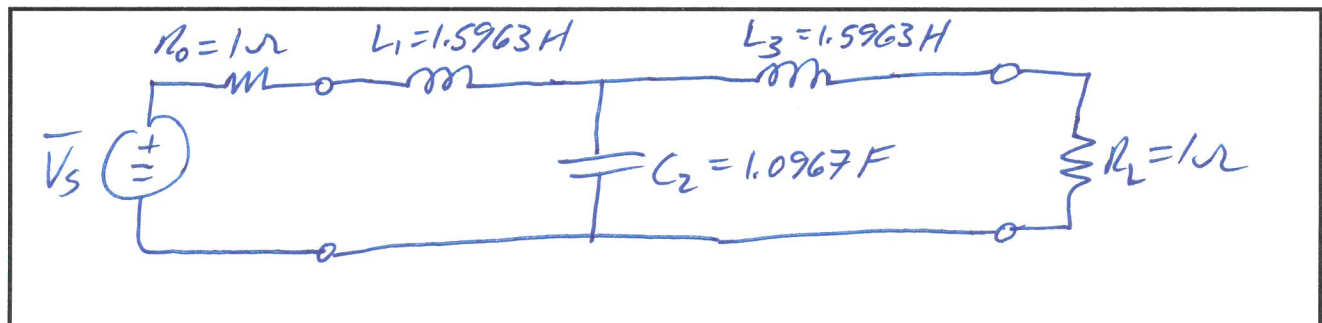

$\Rightarrow$ Not doing any freq. or impedance scaling.


* per Fig 8.34a), The series inductors

become series short-circuit stubs

w/ $z_0 = L$ and length $\ell = \lambda/8$ @ $\omega_c = 1 \text{ rad/s}$

$$\text{Here, } z_0 = L = \underline{1.5963 \Omega}$$

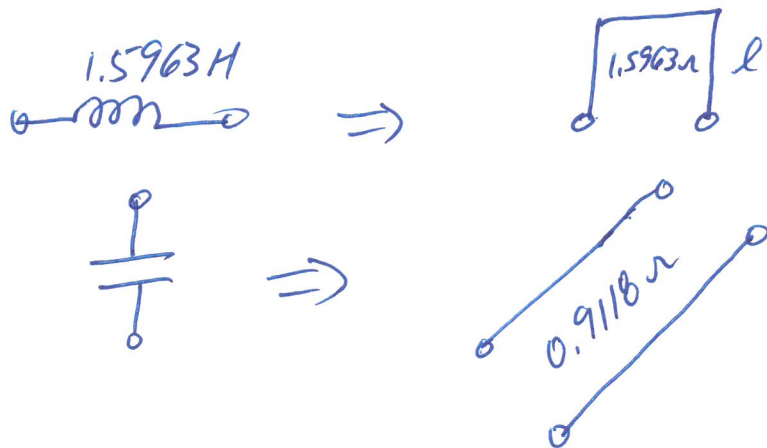* Per Fig 8.34 b), the shunt capacitor becomes
 a shunt open-circuit stub w/ $Z_0 = \frac{1}{C}$
 and length $l = \lambda/8 @ \omega_c$. $Z_0 = \frac{1}{1.0967} = 0.911826 \Omega$



low-pass filter w/ stubs

