EE 481/581 Microwave Engineering (Fall 2024) Homework 3 Monday, September 16, 2024

- 1) A Victorian brass and beeswax coaxial transmission line operates at 2.5 GHz has the distributed parameters $R = 4 \Omega/m$, L = 264 nH/m, G = 4.1 mS/m, and C = 105 pF/m. Calculate the a) propagation constant, b) attenuation constant (both Np/m and dB/m), c) phase constant, d) characteristic impedance (both polar & rectangular forms), e) wavelength, and f) phase velocity (m/s and fraction of *c*).
- 2) Use a 2 m length of the Victorian coaxial transmission line to create a TL circuit with V_g=20∠0° V, Z_g=50 j10 Ω, and Z_L=100-j50 Ω operating at 2.5 GHz. Find: a) the load reflection coefficient, b) input reflection coefficient, c) V₀⁺, d) the general phasor voltage & current equations.
- 3) Use information from problem 2) to find the exact: a) input power, b) load power, c) power lost in TL, d) power from generator, and e) power consumed by Z_g .
- 4) Repeat problem 3) to get low-loss TL approximations for: a) input power, b) load power, and c) power lost in TL. Compare with problem 3) answers.
- 5) A lossless transmission line (75 Ω , 2.1 × 10⁸ m/s) of length 10 cm has a measured input impedance of 16.5 *j*34.5 Ω at 4.6 GHz. Using a Smith chart, find: a) input reflection coefficient, b) input admittance, c) load reflection coefficient, d) SWR, e) return loss, and f) load impedance.
- 6) 2.20
- 7) 2.23 Use Smith Chart.
- 8) 2.29 Analytic solution. Find both P_{in} and P_{Vg} .
- 9) EE 581 only- Using computer, plot |V|, |I|, and P for $-\ell/\lambda \le z/\lambda \le 0$ for problem 2.29.
- Where relevant, one Smith chart per problem. **Clearly label** all work on Smith charts (e.g., label all points, arcs, problem number, distances, ...).
- Put all complex quantities in phasor form (e.g., $A/\underline{\theta}^{\circ}$) except <u>admittances</u>, <u>impedances</u> and <u>propagation constants</u> which should be in rectangular form.

Due Friday, September 20, 2024.