

EE 481/581 Microwave Engineering (Fall 2024)

Homework 4

Friday, September 20, 2024

- 1) For a circuit operating at 100 MHz, design and sketch a single series inductor matching network for a load $Z_L = 100 + j150 \, \Omega$ connected to a lossless transmission line ($250 \, \Omega$, $2 \times 10^8 \, \text{m/s}$). Use Smith chart solution method.
- 2) For a circuit operating at 2.5 GHz, design and sketch a single parallel capacitor matching network for a load $Z_L = 100 - j50 \, \Omega$ connected to a lossless transmission line ($25 \, \Omega$, $2 \times 10^8 \, \text{m/s}$). Use Smith chart solution method.
- 3) For a circuit operating at 2.5 GHz, design and sketch a lossless L -network using a parallel capacitor to match a load $Z_L = 100 - j50 \, \Omega$ to a lossless transmission line ($25 \, \Omega$, $2 \times 10^8 \, \text{m/s}$). Use Smith chart solution method. Confirm **component values** using analytic equations.
- 4) For a circuit operating at 125 MHz, design and sketch a lossless L -network using **a series inductor** match a load $Z_L = 150 + j120 \, \Omega$ to a lossless transmission line ($300 \, \Omega$, $2.8 \times 10^8 \, \text{m/s}$). Use Smith chart solution method. Confirm **component values** using analytic equations.
- 5) For problem 3), using the L -network designed, calculate the component impedances, input impedance (at terminals of matching network), input reflection coefficient, and SWR at 2.45, 2.5, & 2.55 GHz. Tabulate results. Format: col. 1 frequency, col. 2 Z_{cap} , col. 3 Z_{ind} , col. 4 Z_{in} , col. 4 Γ_{in} , & col. 5 SWR.
- 6) EE 581 only: For problem 1), using the designed match, calculate the match-point impedance, inductor impedance, input impedance (at terminals of matching network), input reflection coefficient, and SWR at 95, 100, & 105 MHz. Tabulate results. Format: col. 1 frequency, col. 2 Z_m , col. 3 Z_{ind} , col. 4 Z_{in} , col. 5 Γ_{in} , & col. 6 SWR.

Due Wednesday, September 25, 2024.

- Where relevant, one Smith chart per problem. **Clearly label** all work on Smith charts (e.g., label problem number, Z_0 , f or λ , all points, arcs, distances, ...).
- Put all complex quantities in phasor/polar form (e.g., $A \angle \theta^\circ$) except admittances, impedances, and propagation constants which should be in rectangular form.