

EE 481/581 Microwave Engineering Quiz #4 (Fall 2024)

Name KEY A

Instructions: Open book & notes. Place answers in indicated spaces and show all work for credit.

A lossless transmission line ($60\ \Omega$, $2.4 \times 10^8\ \text{m/s}$) has a load with a measured reflection coefficient of $0.52\angle 100.5^\circ$ at 600 MHz. Calculate the wavelength (cm). Then, using a Smith chart, find the load impedance and standing wave ratio (SWR). Finally, design a single series capacitor matching network (distance d and C) with the capacitor positioned as close as possible to the load. Sketch in box provided with all relevant quantities. **Show and clearly label** all work on the Smith chart (this will be graded).


➤ Wavelength $\lambda = v_p/f = 2.4 \times 10^8 / 600 \times 10^6 \Rightarrow \underline{\lambda = 0.4\ \text{m} = 40\ \text{cm}}$.


Steps

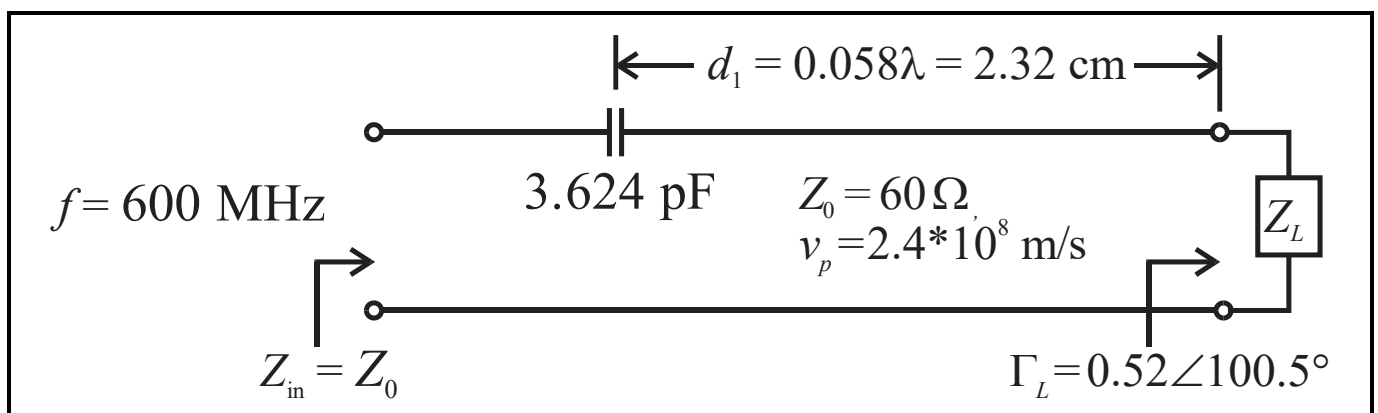- 1) Plot $\Gamma_L = 0.52\angle 100.5^\circ$ on Smith chart.
- 2) Read $z_L = 0.5 + j\ 0.7\ \Omega/\Omega$. Compute $Z_L = Z_0 z_L = 60(0.5 + j\ 0.7) \Rightarrow \underline{Z_L = 30 + j\ 42\ \Omega}$.
- 3) Draw circle, centered on Smith chart, through Γ_L/z_L point and arc on SWR scale. Read SWR = 3.17.
- 4) The two points are $z_{m,i} = 1 \pm j1.22\ \Omega/\Omega$. Choose $z_{m,1} = 1 + j1.22\ \Omega/\Omega$ (inductive x).
- 5) Find the distance d_1 from z_L to $z_{m,1}$ using the “WAVELENGTHS TOWARD GENERATOR” scale as $d_1 = (0.1681 - 0.1101)\lambda \Rightarrow \underline{d_1 = 0.058\lambda = 2.32\ \text{cm}}$.
- 6) At $z_{m,1}$ add a series capacitor with reactance $Z_{\text{cap}} = -j1.22(60) = -j73.2\ \Omega = -j/\omega C$. Solving for $C = 1/(2\pi 600 \times 10^6 73.2) \Rightarrow \underline{C = 3.624\ \text{pF}}$.

wavelength = $\lambda = 0.4\ \text{m} = 40\ \text{cm}$ $Z_L = \underline{30 + j\ 42\ \Omega}$ SWR = 3.17

$d = \underline{d_1 = 0.058\lambda = 2.32\ \text{cm}}$ $C = \underline{3.624\ \text{pF}}$



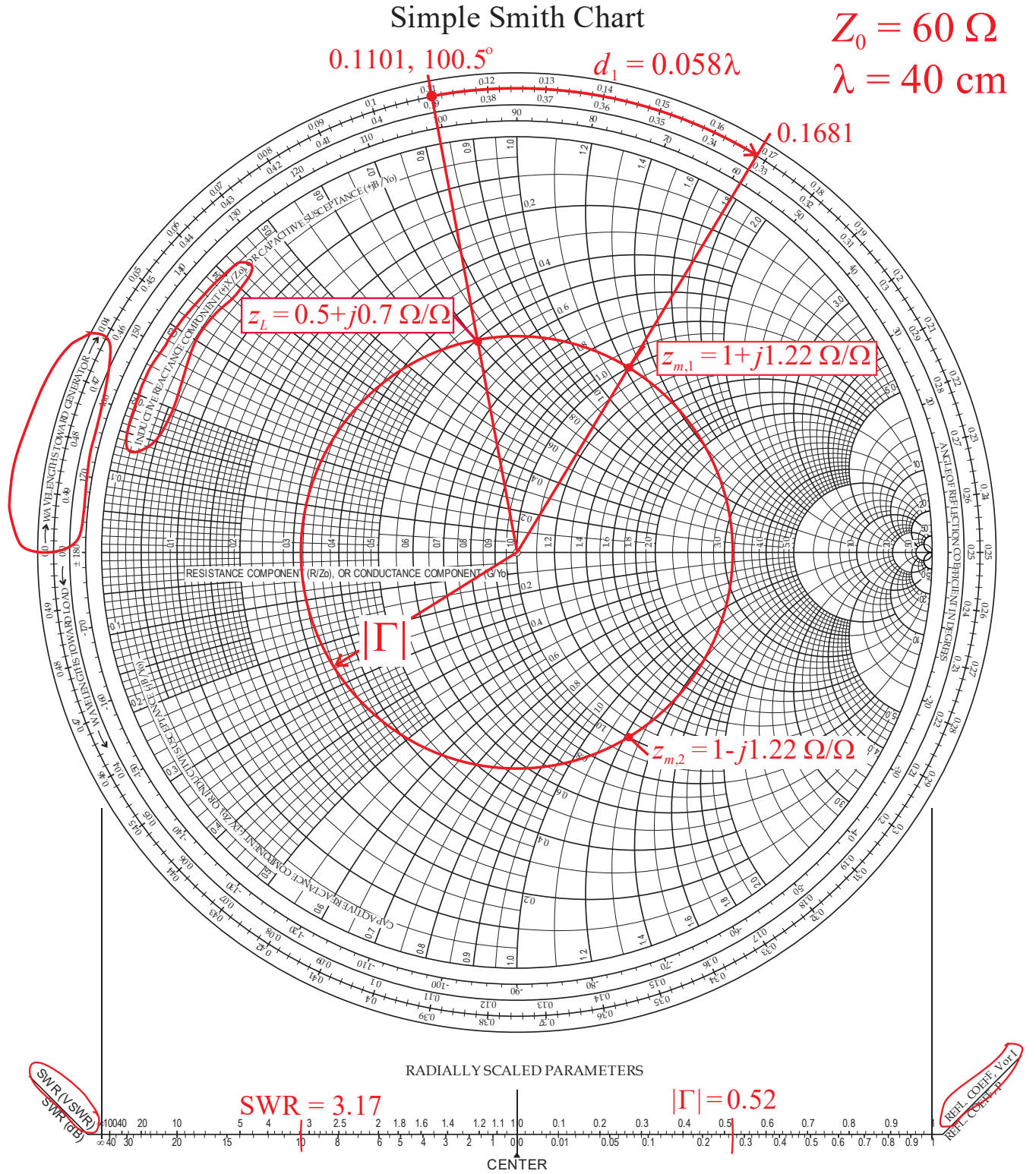

EE 481/581 Microwave Engineering Quiz #4 (Fall 2024)

Name KEY B

Instructions: Open book & notes. Place answers in indicated spaces and show all work for credit.

A lossless transmission line (80Ω , 2.4×10^8 m/s) has a load with a measured reflection coefficient of $0.382 \angle -111.3^\circ$ at 800 MHz. Calculate the wavelength (cm). Then, using a Smith chart, find the load impedance and standing wave ratio (SWR). Finally, design a single series capacitor matching network (distance d and C) with the capacitor positioned as close as possible to the load. Sketch in box provided with all relevant quantities. **Show and clearly label** all work on the Smith chart (this will be graded).


➤ Wavelength $\lambda = v_p/f = 2.4 \times 10^8 / 800 \times 10^6 \Rightarrow \underline{\lambda = 0.3 \text{ m} = 30 \text{ cm}}$.

Steps

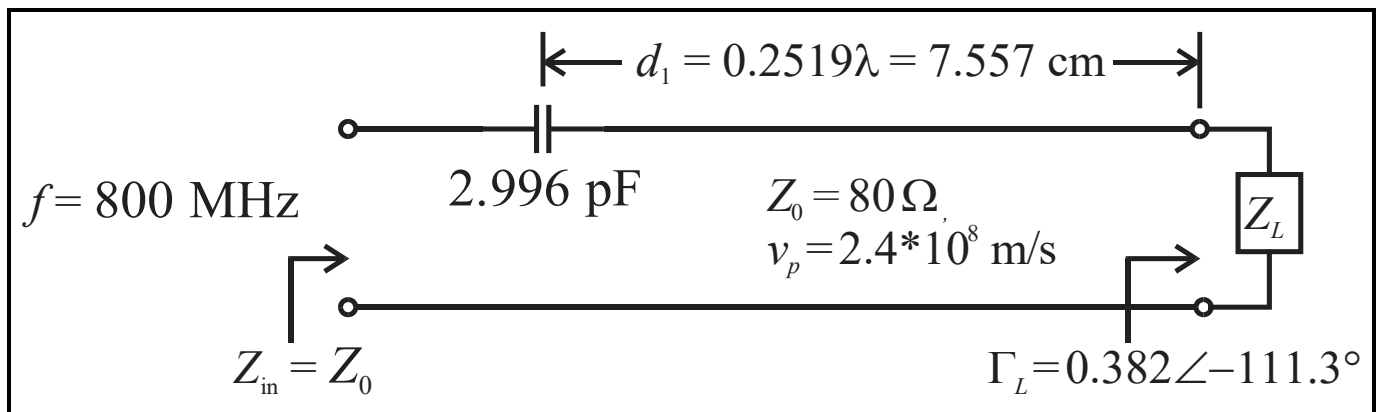- 1) Plot $\Gamma_L = 0.382 \angle -111.3^\circ$ on Smith chart.
- 2) Read $z_L = 0.6 - j0.5 \Omega/\Omega$. Compute $Z_L = Z_0 z_L = 80 (0.6 - j0.5) \Rightarrow \underline{Z_L = 48 - j40 \Omega}$.
- 3) Draw circle, centered on Smith chart, through Γ_L/z_L point and arc on SWR scale. Read SWR = 2.24.
- 4) The two points are $z_{m,i} = 1 \pm j0.83 \Omega/\Omega$. Choose $z_{m,1} = 1 + j0.83 \Omega/\Omega$ (inductive x).
- 5) Find the distance d_1 from z_L to $z_{m,1}$ using the “WAVELENGTHS TOWARD GENERATOR” scale as $d_1 = (0.0958 + 0.1561)\lambda \Rightarrow \underline{d_1 = 0.2519\lambda = 7.557 \text{ cm}}$.
- 6) At $z_{m,1}$ add a series capacitor with reactance $Z_{\text{cap}} = -j0.83(80) = -j66.4 \Omega = -j/\omega C$. Solving for $C = 1/(2\pi 800 \times 10^6 66.4) \Rightarrow \underline{C = 2.996 \text{ pF}}$.

wavelength = $\lambda = 0.3 \text{ m} = 30 \text{ cm}$ $Z_L = \underline{48 - j40 \Omega}$ SWR = 2.24

$d = \underline{d_1 = 0.2519\lambda = 7.557 \text{ cm}}$ $C = \underline{2.996 \text{ pF}}$



Simple Smith Chart

$Z_0 = 80 \Omega$
 $\lambda = 30 \text{ cm}$

