

EE 481/581 Microwave Engineering Quiz #6 (Fall 2024)


Name

Key A + B

Instructions: Open notes & text. Place answers in indicated spaces. Show & clearly label all work for partial credit.


Find the $[Z]$ -matrix for the two-port L -section shown below.

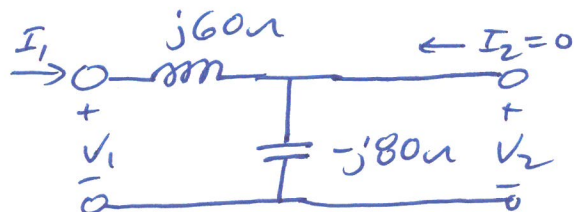$Z_{11} + Z_{21} \rightarrow \text{set } I_2 = 0$



$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{-j20I_1}{I_1} = \underline{-j20\Omega}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{-j80I_1}{I_1} = \underline{-j80\Omega}$$

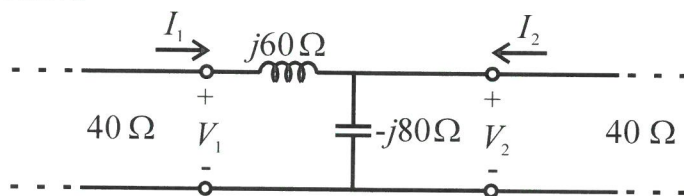


By KVL and Ohm's Law

$$V_1 = I_1(j60 - j80) = -j20I_1$$

$$V_2 = I_1(-j80) = -j80I_1$$

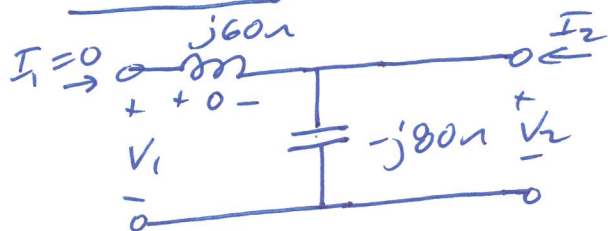$Z_{22} + Z_{12} \rightarrow \text{set } I_1 = 0$



By KVL and Ohm's Law

$$V_1 = V_2 = -j80I_2$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{-j80I_2}{I_2} = \underline{-j80\Omega}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{-j80I_2}{I_2} = \underline{-j80\Omega}$$

$$[Z] = \begin{bmatrix} -j20\Omega & -j80\Omega \\ -j80\Omega & -j80\Omega \end{bmatrix}$$