


EE 481/581 Microwave Engineering Quiz #7 (Fall 2024)

Name


Key A

Instructions: Open notes & text. Place answers in given spaces. Show & clearly label all work for partial credit.

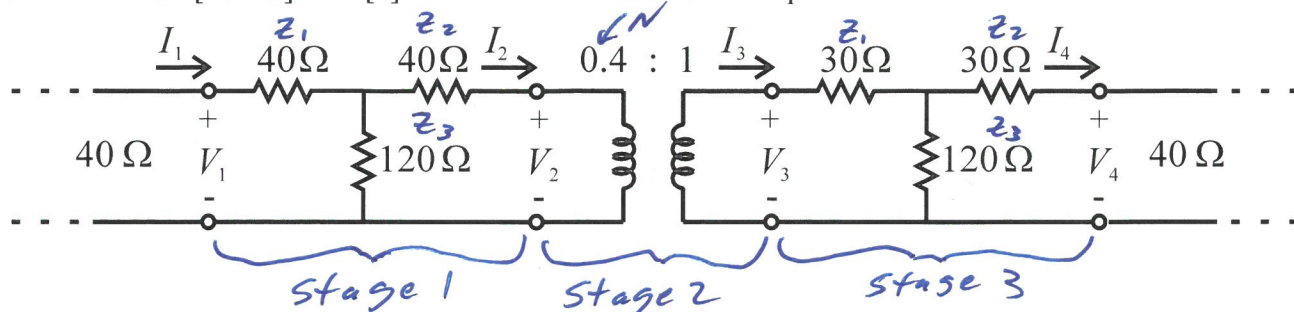
Find the overall $[ABCD]$ - and $[S]$ -matrices for the cascaded two-port networks shown.



From Table 4.1

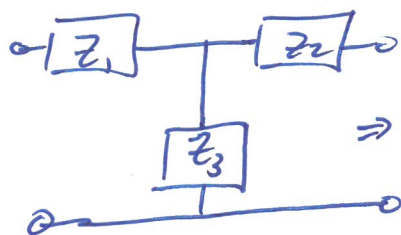
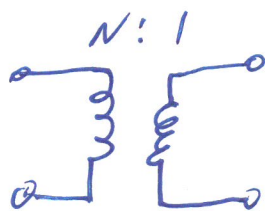
$$\Rightarrow ABCD = \begin{bmatrix} 1 + z_1/z_3 & z_1 + z_2 + \frac{z_1 z_2}{z_3} \\ 1/z_3 & 1 + z_2/z_3 \end{bmatrix}$$



$$\Rightarrow ABCD = \begin{bmatrix} N & 0 \\ 0 & 1/N \end{bmatrix}$$

$$[ABCD]_1 = \begin{bmatrix} 1 + 40/120 & 40 + 40 + \frac{40^2}{120} \\ 1/120 & 1 + 40/120 \end{bmatrix} = \begin{bmatrix} 1.3 & 93.3 \Omega \\ 8.3 \times 10^{-3} S & 1.3 \end{bmatrix}$$

$$[ABCD]_2 = \begin{bmatrix} 0.4 & 0 \\ 0 & 1/0.4 \end{bmatrix} = \begin{bmatrix} 0.4 & 0 \\ 0 & 2.5 \end{bmatrix}$$

$$[ABCD]_3 = \begin{bmatrix} 1 + 30/120 & 30 + 30 + \frac{30^2}{120} \\ 1/120 & 1 + 30/120 \end{bmatrix} = \begin{bmatrix} 1.25 & 67.5 \Omega \\ 8.3 \times 10^{-3} S & 1.25 \end{bmatrix}$$

Overall

$$\begin{aligned}
 [ABCD] &= [ABCD]_1 [ABCD]_2 [ABCD]_3 \\
 &= \begin{bmatrix} 1.3 & 93.3 \\ 8.3 \times 10^{-3} & 1.3 \end{bmatrix} \begin{bmatrix} 0.4 & 0 \\ 0 & 2.5 \end{bmatrix} \begin{bmatrix} 1.25 & 67.5 \\ 8.3 \times 10^{-3} & 1.25 \end{bmatrix} \\
 &= \begin{bmatrix} 0.53 & 233.3 \\ 8.3 \times 10^{-3} & 3.3 \end{bmatrix} \begin{bmatrix} 1.25 & 67.5 \\ 8.3 \times 10^{-3} & 1.25 \end{bmatrix} = \underline{\underline{\begin{bmatrix} 2.61 & 327.6 \Omega \\ 0.031945 & 4.3916 \end{bmatrix}}}
 \end{aligned}$$

From Table 4.2 w/ $z_0 = 40 \Omega$

$$\begin{aligned}
 S_{11} &= \frac{A + B/z_0 - Cz_0 - D}{A + B/z_0 + Cz_0 + D} = \frac{2.61 + \frac{327.6}{40} - 0.03194(40) - 4.3916}{2.61 + 327.6/40 + 0.03194(40) + 4.3916} \\
 &= \frac{5.13}{16.472} = 0.311636
 \end{aligned}$$

$$\begin{aligned}
 S_{12} &= \frac{2(AD - BC)}{A + B/z_0 + Cz_0 + D} = \frac{2[2.61(4.3916) - 327.6(0.03194)]}{16.472} \\
 &= \frac{2}{16.472} = 0.121417
 \end{aligned}$$

$$S_{21} = \frac{2}{A + B/z_0 + Cz_0 + D} = \frac{2}{16.472} = 0.121417 = S_{12}$$

$$\begin{aligned}
 S_{22} &= \frac{-A + B/z_0 - Cz_0 + D}{A + B/z_0 + Cz_0 + D} = \frac{-2.61 + \frac{327.6}{40} - 0.03194(40) + 4.3916}{16.472} \\
 &= \frac{8.694}{16.472} = 0.527825
 \end{aligned}$$

[ABCD]

[S]

$ \begin{bmatrix} 2.61 & 327.6 \Omega \\ 0.031945 & 4.3916 \end{bmatrix} $	$ \begin{bmatrix} 0.31164 & 0.12142 \\ 0.12142 & 0.52782 \end{bmatrix} $
--	--


EE 481/581 Microwave Engineering Quiz #7 (Fall 2024)

Name


Key B

Instructions: Open notes & text. Place answers in given spaces. Show & clearly label all work for partial credit.

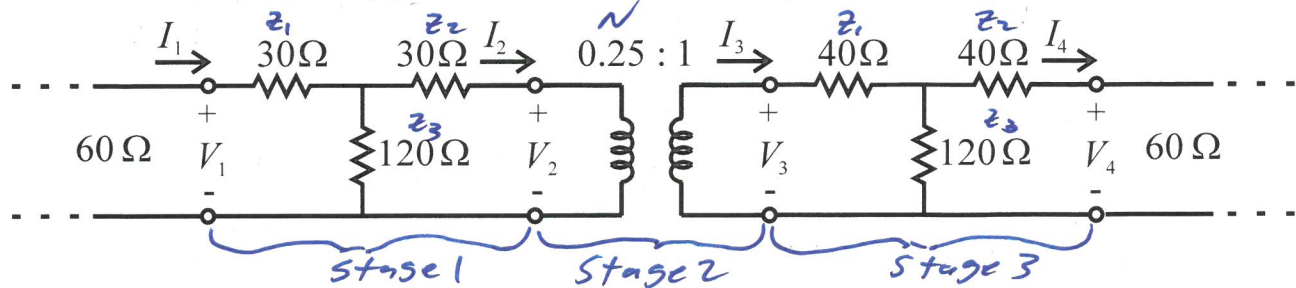
Find the overall $[ABCD]$ - and $[S]$ -matrices for the cascaded two-port networks shown.



From Table 4.3

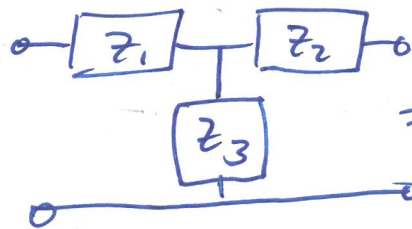
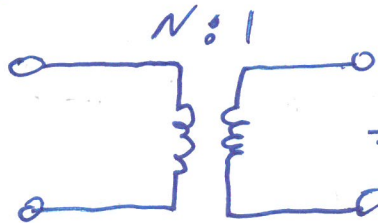
$$\Rightarrow ABCD = \begin{bmatrix} 1 + z_1/z_3 & z_1 + z_2 + \frac{z_1 z_2}{z_3} \\ 1/z_3 & 1 + z_2/z_3 \end{bmatrix}$$



$$\Rightarrow ABCD = \begin{bmatrix} N & 0 \\ 0 & 1/N \end{bmatrix}$$

$$[ABCD]_1 = \begin{bmatrix} 1 + \frac{30}{120} & 30 + 30 + \frac{30^2}{120} \\ 1/120 & 1 + \frac{30}{120} \end{bmatrix} = \begin{bmatrix} 1.25 & 67.5 \Omega \\ 8.3 \times 10^{-3} S & 1.25 \end{bmatrix}$$

$$[ABCD]_2 = \begin{bmatrix} 0.25 & 0 \\ 0 & 1/0.25 \end{bmatrix} = \begin{bmatrix} 0.25 & 0 \\ 0 & 4 \end{bmatrix}$$

$$[ABCD]_3 = \begin{bmatrix} 1 + \frac{40}{120} & 40 + 40 + \frac{40^2}{120} \\ 1/120 & 1 + \frac{40}{120} \end{bmatrix} = \begin{bmatrix} 1.3 & 93.3 \Omega \\ 8.3 \times 10^{-3} S & 1.3 \end{bmatrix}$$

Overall $[ABCD] = [ABCD]_1 [ABCD]_2 [ABCD]_3$

$$[ABCD] = \begin{bmatrix} 1.25 & 67.5 \\ 8.3 \times 10^{-3} & 1.25 \end{bmatrix} \begin{bmatrix} 0.25 & 0 \\ 0 & 4 \end{bmatrix} \begin{bmatrix} 1.3 & 93.3 \\ 8.3 \times 10^{-3} & 1.3 \end{bmatrix}$$

$$= \begin{bmatrix} 0.3125 & 270 \\ 2.083 \times 10^{-3} & 5 \end{bmatrix} \begin{bmatrix} 1.3 & 93.3 \\ 8.3 \times 10^{-3} & 1.3 \end{bmatrix} = \begin{bmatrix} 2.6 & 389.16 \Omega \\ 0.045 & 6.86 \Gamma \end{bmatrix}$$

From Table 4.2 w/ $z_0 = 60 \Omega$

$$S_{11} = \frac{A + B/z_0 - Cz_0 - D}{A + B/z_0 + Cz_0 + D} = \frac{2.6 + 389.16/60 - 0.04(60) - 6.86\Gamma}{2.6 + 389.16/60 + 0.04(60) + 6.86\Gamma}$$

$$= \frac{-0.375}{18.6805} = -0.02007435$$

$$S_{12} = \frac{2(AD - BC)}{A + B/z_0 + Cz_0 + D} = \frac{2[2.6(6.86\Gamma) - 389.16(0.04)]}{18.6805} = \frac{2}{18.68}$$

$$= 0.10706318$$

$$S_{21} = \frac{2}{A + B/z_0 + Cz_0 + D} = S_{12} = 0.10706318$$

$$S_{22} = \frac{-A + B/z_0 - Cz_0 + D}{A + B/z_0 + Cz_0 + D} = \frac{-2.6 + 389.16/60 - 0.04(60) + 6.86\Gamma}{18.6805}$$

$$= \frac{8.0138}{18.6805} = 0.4289963$$

[ABCD]

[S]

$\begin{bmatrix} 2.6 & 389.16 \Omega \\ 0.045 & 6.86 \Gamma \end{bmatrix}$	$\begin{bmatrix} -0.02007 & 0.10706 \\ 0.10706 & 0.42900 \end{bmatrix}$
--	---