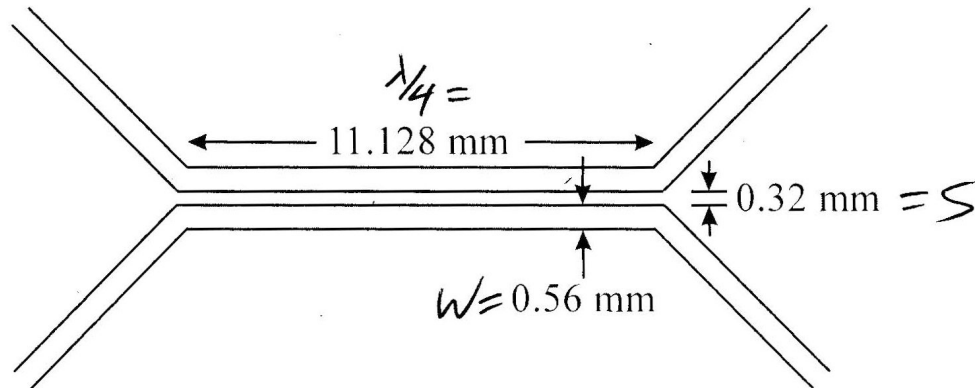


## EE 481/581 Microwave Engineering Quiz #9 (Fall 2024)

Name KEY A**Instructions:** Open notes/text. Place answers in indicated spaces. Show & clearly label *all* work for partial credit.

- 1) An edge-coupled **stripline** directional coupler is pictured below. Given that it is built using a board with ground plane separation of 1.6 mm and dielectric constant 3.5, determine the even- and odd-mode characteristic impedances, the coupling factor (unitless and in dB), and center frequency.



$$b = 1.6 \text{ mm}, \epsilon_r = 3.5$$

$$w/b = \frac{0.56}{1.6} = 0.35 \quad \& \quad s/b = \frac{0.32}{1.6} = 0.2$$

↳ Plot on Fig 7.29. Read-off:

$$\sqrt{\epsilon_r} Z_{0e} = 145.509 \Rightarrow Z_{0e} = \frac{145.509}{\sqrt{3.5}} = 77.78 \Omega$$

$$\sqrt{\epsilon_r} Z_{0o} = 93.371 \Rightarrow Z_{0o} = \frac{93.371}{\sqrt{3.5}} = 49.909 \Omega$$

$$\text{Per (7.81), } C = \frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}} = \frac{77.78 - 49.9}{77.78 + 49.9} = 0.21826$$

$$C(\text{dB}) = -20 \log_{10} 0.21826 = +13.22 \text{ dB}$$

$$\lambda/4 = 11.128 \text{ mm} \Rightarrow \lambda = 44.512 \text{ mm} \Rightarrow \text{from } v_p = \frac{c}{\sqrt{\epsilon_r}} = f \lambda$$

$$\hookrightarrow f = \frac{2.9979 \times 10^8}{\sqrt{3.5} (0.044512)} = 3.6 \times 10^9 \text{ Hz}$$


even-mode char. impedance = 77.78  $\Omega$

odd-mode char. impedance = 49.91  $\Omega$

coupling factor = 0.218 or 13.22 dB

center frequency = 3.6 GHz

## Quiz A

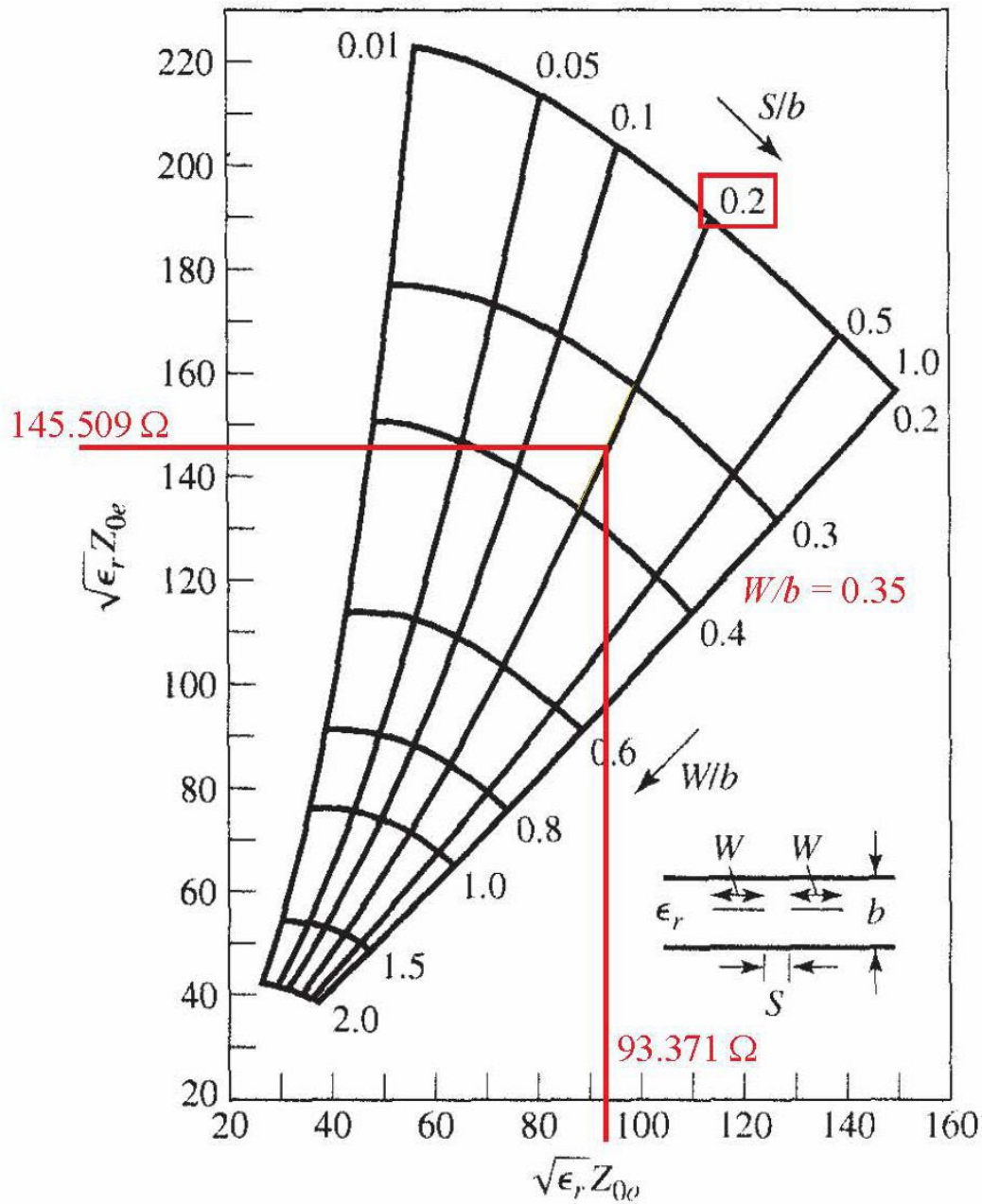


**FIGURE 7.29**

Normalized even- and odd-mode characteristic impedance design data for symmetric edge-coupled striplines.

## EE 481/581 Microwave Engineering Quiz #9 (Fall 2024)

Name KEY B**Instructions:** Open notes/text. Place answers in indicated spaces. Show & clearly label *all* work for partial credit.

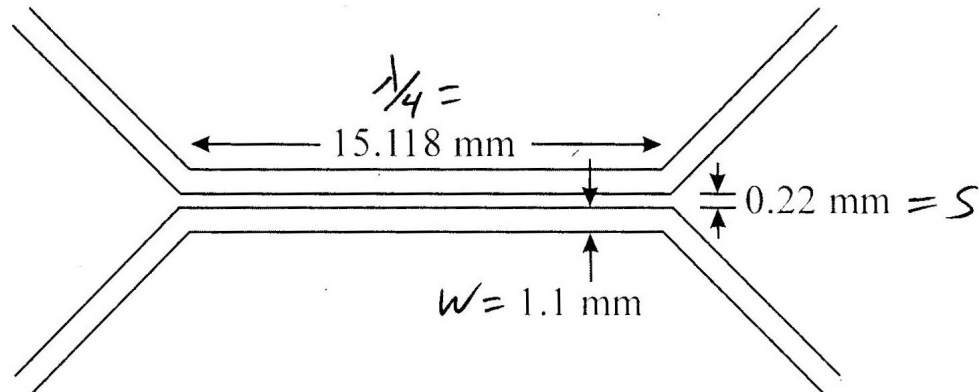- 2) An edge-coupled **stripline** directional coupler is pictured below. Given that it is built using a board with ground plane separation of 2.2 mm and dielectric constant 2.4, determine the even- and odd-mode characteristic impedances, the coupling factor (unitless and in dB), and center frequency.



$$b = 2.2 \text{ mm}, \epsilon_r = 2.4$$

$$w/b = \frac{1.1}{2.2} = 0.5 + s/b = \frac{0.22}{2.2} = 0.1 \rightarrow \text{Plot on Fig 7.29}$$

$$\text{Read-off } \sqrt{\epsilon_r} Z_{0e} = 125.367 \Rightarrow Z_{0e} = \frac{125.367}{\sqrt{2.4}} = \underline{80.924 \Omega}$$

$$\sqrt{\epsilon_r} Z_{0o} = 70 \Rightarrow Z_{0o} = \frac{70}{\sqrt{2.4}} = \underline{45.185 \Omega}$$

$$\text{Per (7.81), } C = \frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}} = \frac{80.9 - 45.2}{80.9 + 45.2} = \underline{0.2834}$$

$$C(\text{dB}) = -20 \log_{10} 0.2834 = \underline{10.952 \text{ dB}}$$


$$\lambda/4 = 15.118 \text{ mm} \rightarrow \lambda = 60.472 \text{ mm}$$

$$\text{From } v_p = \frac{c}{\sqrt{\epsilon_r}} = f \lambda, f = \frac{2.9979 \times 10^8}{\sqrt{2.4} (0.060472)} = \underline{3.2 \times 10^9 \text{ Hz}}$$

even-mode char. impedance = 80.92  $\Omega$       odd-mode char. impedance = 45.185  $\Omega$

coupling factor = 0.283 or 10.95 dB      center frequency = 3.2 GHz

## Quiz B

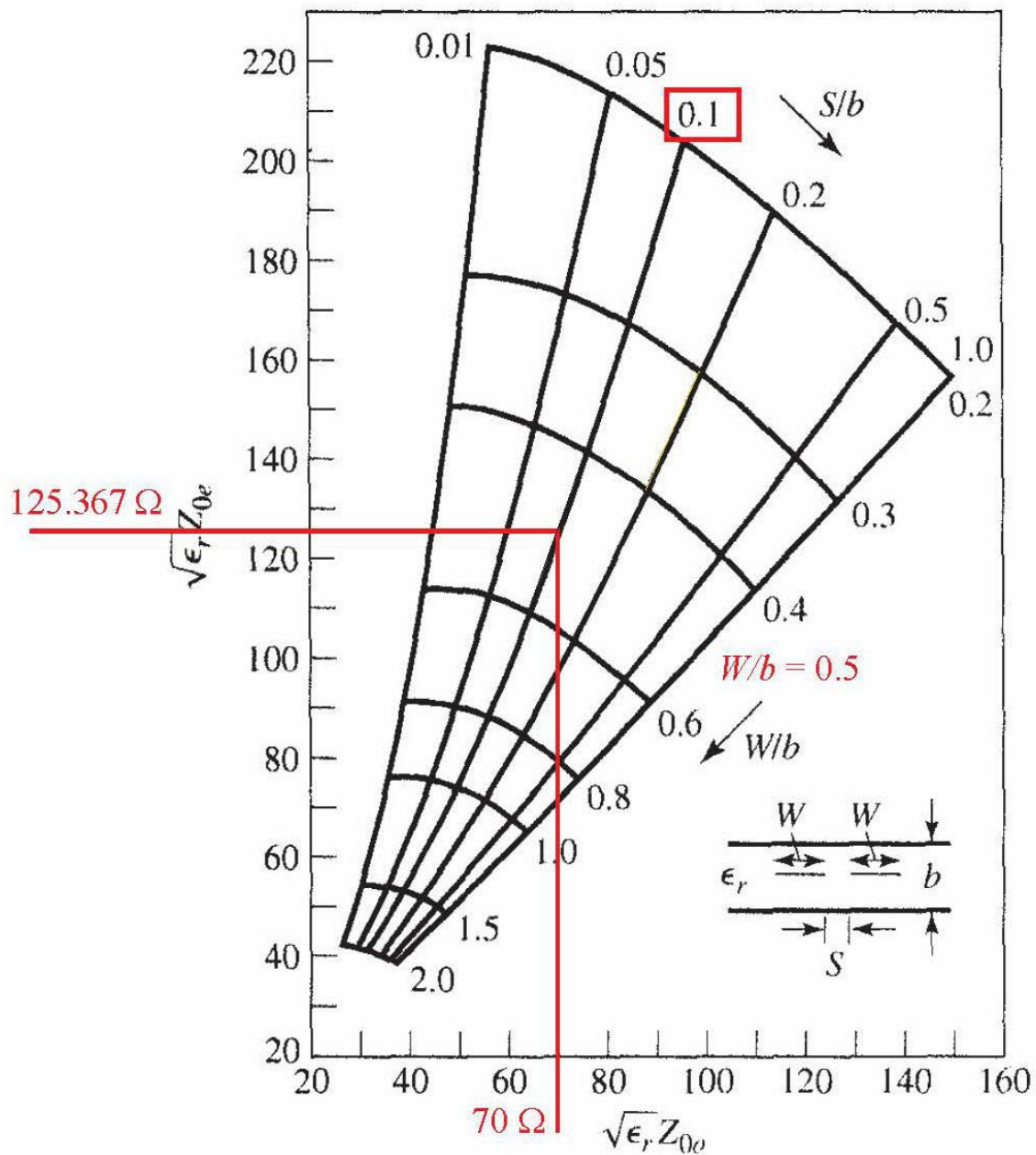

**FIGURE 7.29**

Normalized even- and odd-mode characteristic impedance design data for symmetric edge-coupled striplines.