

EE 481/581 Microwave Engineering Quiz #11 (Fall 2024)


Name Key A**Instructions:** Open notes/text. Place answers in indicated spaces. Show & clearly label *all* work for partial credit.

Design a maximally flat low-pass filter prototype with an attenuation of at least 25 dB at three times the cutoff frequency of the minimum order N , and the immittance values g_0 to g_{N+1} . Assume a prototype design with the use of inductors maximized. The filter is to be implemented using a stepped-impedance design in a $65\ \Omega$ system where the lowest and highest practical impedances are $25\ \Omega$ and $120\ \Omega$. Fill out the table provided with the immittance (F or H), impedance (highest or lowest practical value), and electrical length βl_i (rad and degrees) of each section going from 1 to N . [Rows may be added or skipped as necessary.]

$$\left| \frac{\omega}{\omega_c} \right| - 1 = \left| \frac{3\omega}{\omega_c} \right| - 1 = 2 \rightarrow \text{Mark on Fig 8.26}$$

along $\omega/25\ \text{dB} \Rightarrow \text{Need 3rd order filter. (3 sections)}$

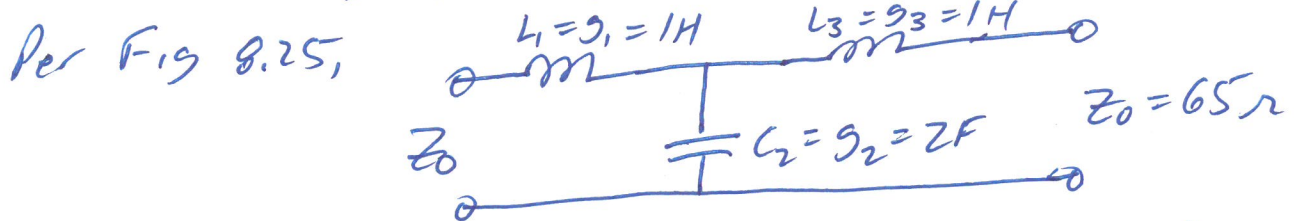Per Table 8.3, $g_1 = 1, g_2 = 2, \& g_3 = 1$



Inductors βl (8.86a), $\beta l_1 = \beta l_3 = \frac{L R_0}{Z_h} = \frac{1(65)}{120}$
 (use $Z_h = 120\ \Omega$)
 $= 0.541\bar{6}\ \text{rad} = 31.035^\circ$

Capacitor βl (8.86b), $\beta l_2 = \frac{C Z_e}{R_0} = \frac{2(25)}{65}$
 (use $Z_e = 25\ \Omega$)
 $= 0.76923\ \text{rad} = 44.074^\circ$

Prototype: $N = \underline{3}$

Section	Prototype immittance	Characteristic Impedance (Ω)	βl_i (rad)	βl_i (deg)
1	1H	120	0.5416	31.035
2	2F	25	0.76923	44.074
3	1H	120	0.5416	31.035

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

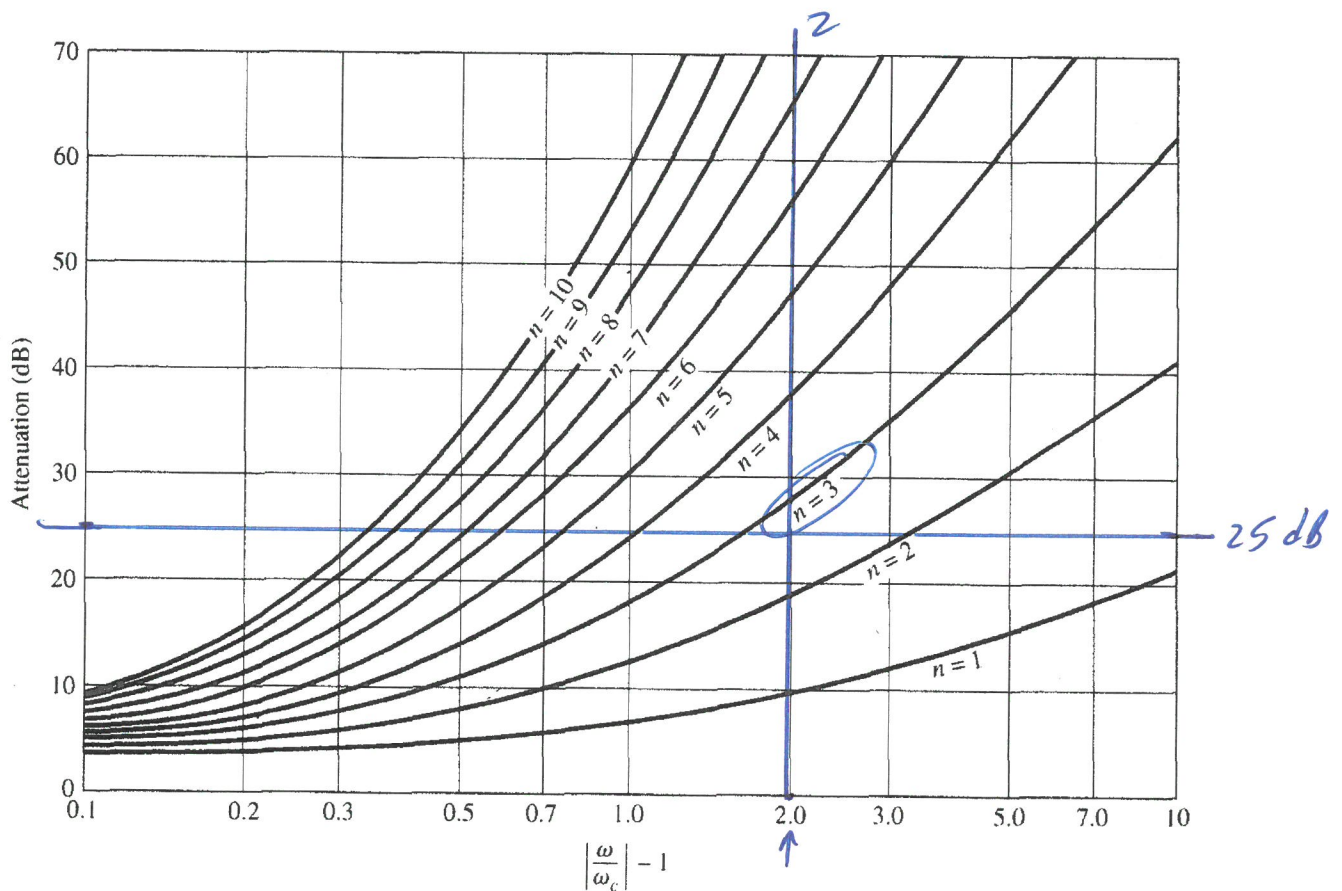


FIGURE 8.26 Attenuation versus normalized frequency for maximally flat filter prototypes. Adapted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

EE 481/581 Microwave Engineering Quiz #11 (Fall 2024)

Name


Key B

Instructions: Open notes/text. Place answers in indicated spaces. Show & clearly label all work for partial credit.

Design a maximally flat low-pass filter prototype with an attenuation of at least 32 dB at four times the cutoff frequency of the minimum order N , and the immittance values g_0 to g_{N+1} . Assume a prototype design with the use of inductors maximized. The filter is to be implemented using a stepped-impedance design in a 55Ω system where the lowest and highest practical impedances are 20Ω and 100Ω . Fill out the table provided with the immittance (F or H), impedance (highest or lowest practical value), and electrical length $\beta\ell_i$ (rad and degrees) of each section going from 1 to N . [Rows may be added or skipped as necessary.]

$$\left| \frac{\omega}{\omega_c} \right| - 1 = \left| \frac{4\omega_c}{\omega_c} \right| - 1 = 3 \Rightarrow \text{Mark on Fig 8.26 along w/ 32 dB} \Rightarrow \text{Need 3rd order filter (3 sections)}$$

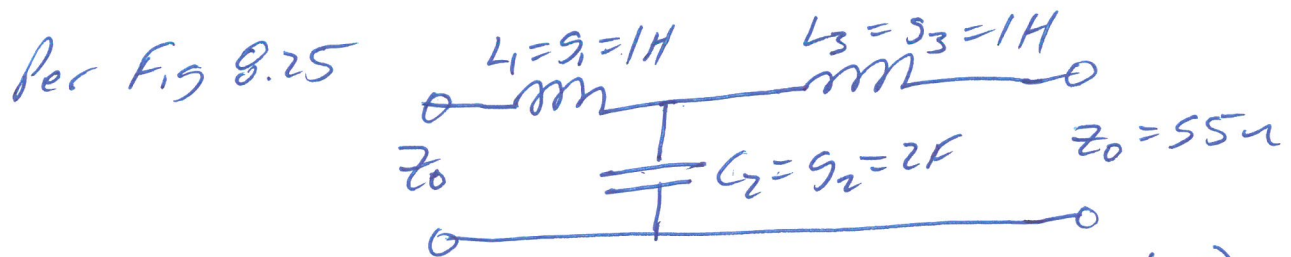Per Table 8.3, $g_1 = 1$, $g_2 = 2$, & $g_3 = 1$



Inductors $\beta\ell$ (8.86a), $\beta\ell_1 = \beta\ell_3 = \frac{L R_0}{Z_n} = \frac{1(55)}{100} = 0.55 \text{ rad} = 31.513^\circ$
(use $Z_n = 100 \Omega$)

Capacitor (8.86b), $\beta\ell_2 = \frac{C Z_e}{R_0} = \frac{2(20)}{55} = 0.72 \text{ rad} = 41.66966^\circ$
(use $Z_e = 20 \Omega$)

Prototype: $N = 3$

Section	Prototype immittance	Characteristic Impedance (Ω)	$\beta\ell_i$ (rad)	$\beta\ell_i$ (deg)
1	1H	100	0.55	31.513
2	2F	20	0.72	41.67
3	1H	100	0.55	31.513

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

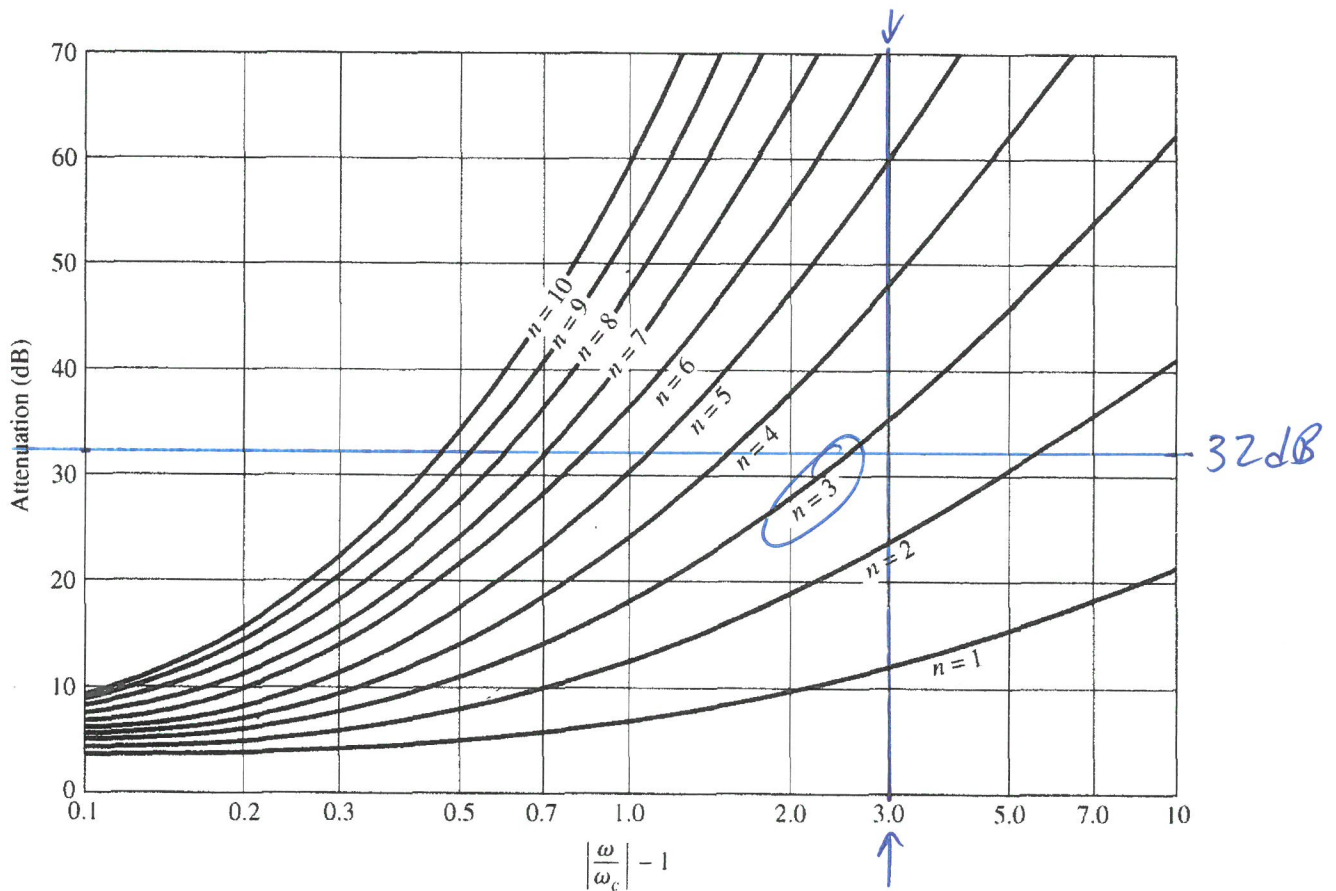


FIGURE 8.26 Attenuation versus normalized frequency for maximally flat filter prototypes. Adapted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.