

EE 481/581 Microwave Engineering (Fall 2025)

Homework 2

Tuesday, September 9, 2025

- 1) We have made a parallel plate transmission line by cutting a 0.75" wide strip from a 0.25" thick plexiglass board from Ace Hardware covered with lead tape (24 μm thick). If the transmission line is operated at 3 GHz at room temperature, determine: a) the effective conductivity and complex permittivity of the plexiglass, and b) the skin depth & distributed parameters R , L , G , & C of the transmission line. [Hint: Appendices E, F, & G.]
- 2) For the plexiglass parallel plate transmission line in 1), calculate: a) propagation constant, b) attenuation constant (both Np/m and dB/m), c) phase constant, d) characteristic impedance (both polar & rectangular forms), e) wavelength, and f) phase velocity.
- 3) Similar to equations (2.40a) & (2.40b), determine equations for I_{max} & I_{min} and the corresponding reflection coefficient conditions for each. Note that I_{max} & I_{min} pair up with V_{max} & V_{min} at corresponding locations, which goes with which?
- 4) For each current & voltage pair in 3), define an impedance as the ratio of phasor voltage to current and determine equations for Z_{max} and Z_{min} .
- 5) 2.1
- 6) 2.8
- 7) Using a lossless transmission line ($75\ \Omega$ and $v_p = 2.3 \times 10^8\ \text{m/s}$), find the shortest a) open and b) short circuit stubs that appear as a 1 pF capacitor at 1.6 GHz.
- 8) 2.19
- 9) EE 581 only- For the transmission line of problem 2.8, analytically determine the locations (in terms of λ) of all possible current and voltage maxima and/or minima.

Due Monday, September 15, 2025.

- Solve all problems analytically.
- Express all currents, voltages, & reflection coefficients in the polar/phasor format with angles in degrees (e.g., $10\angle 30^\circ\ \text{V}$). Express complex permittivity & impedances in rectangular format (e.g., $10 + j30\ \Omega$).