## EE 481/581 Microwave Engineering (Fall 2025) Homework 3

## Monday, September 15, 2025

- 1) A coaxial transmission line, operating at 3.6 GHz, has the distributed parameters  $R = 3.8 \,\Omega/\text{m}$ ,  $L = 248 \,\text{nH/m}$ ,  $G = 6.4 \,\text{mS/m}$ , and  $C = 112 \,\text{pF/m}$ . Calculate the a) propagation constant, b) attenuation constant (both Np/m and dB/m), c) phase constant, d) characteristic impedance (both polar & rectangular forms), e) wavelength, and f) phase velocity (m/s and fraction of c).
- 2) Use a 1 m length of the coaxial transmission line from 1) to create a TL circuit with  $V_g = 16 \angle 0^\circ \text{ V}$ ,  $Z_g = 45 j10 \Omega$ , and  $Z_L = 100 j50 \Omega$  operating at 3.6 GHz. Find: a) the load reflection coefficient, b) input reflection coefficient, c)  $V_0^+$ , d) the general phasor voltage & current equations.
- 3) Use information from problem 2) to find the **exact**: a) input power, b) load power, c) power lost in TL, d) power from generator, and e) power consumed by  $Z_g$ .
- 4) Repeat problem 3) to get low-loss TL approximations for: a) input power, b) load power, and c) power lost in TL. Compare with problem 3) answers.
- 5) A lossless transmission line  $(50 \Omega, 2.4 \times 10^8 \text{ m/s})$  of length 15 cm has a measured input impedance of  $18 + j32 \Omega$  at 2 GHz. <u>Using a Smith chart</u>, find: a) input reflection coefficient, b) input admittance, c) load reflection coefficient, d) SWR, e) return loss, and f) load impedance.
- 6) 2.20 Change load to  $40-j70 \Omega$
- 7) 2.23 Change SWR to 3. Use Smith Chart.
- 8) 2.29 Change attenuation to 0.6 dB/ $\lambda$  and TL length to 1.8 $\lambda$ . Find both  $P_{in}$  and  $P_{Vg}$ . Analytic solution.
- 9) EE 581 only- 2.17

## Due Friday, September 19, 2025.

- Where relevant, one Smith chart per problem. Clearly label all work on Smith charts (e.g., label  $Z_0$ ,  $f \& v_p$  or  $\lambda$ , all points, arcs, problem number, distances, ...).
- Put all complex quantities in phasor form (e.g.,  $A/\underline{\theta}^{\circ}$ ) except <u>admittances</u>, <u>impedances</u> and <u>propagation constants</u> which should be in rectangular form.