

EE 481/581 Microwave Engineering (Fall 2025)

Homework 10

Wednesday, November 19, 2025

- 1) For a $50\ \Omega$ system, design a lumped-element, 0.5 dB ripple, Chebyshev low-pass filter with a cut-off frequency of 2.4 GHz with an attenuation of at least 15 dB at 4.8 GHz using the architecture of Fig. 8.25a. a) Determine the filter order N and the low-pass filter prototype element values. b) Draw a labeled sketch of the scaled filter with component values. c) Draw a labeled sketch of the filter in phasor form with $V_s = 1\angle 0^\circ$ V. d) Plot the amplitude response $|V_L|$ in decibels with horizontal dashed lines at $20\log(0.5)$ & $20\log(0.5) - 0.5$ and a vertical dashed line at 2.4 GHz for $0 \leq f \leq 5$ GHz and $-25\text{ dB} \leq |V_L| \leq 0$.
- 2) For a $50\ \Omega$ system, design a lumped-element, Butterworth high-pass filter with a cut-off frequency of 2.4 GHz with an attenuation of at least 15 dB at 1.2 GHz using the architecture of Fig. 8.25a. a) Determine the filter order N and the low-pass filter prototype element values. b) Draw a labeled sketch of the scaled and transformed filter with component values. c) Draw a labeled sketch of the filter in phasor form with $V_s = 1\angle 0^\circ$ V. d) Plot the amplitude response $|V_L|$ in decibels with horizontal dashed lines at $20\log(0.5)$ & $20\log(0.25)$ and a vertical dashed line at 2.4 GHz for $0 \leq f \leq 5$ GHz and $-25\text{ dB} \leq |V_L| \leq 0$.
- 3) For a $50\ \Omega$ system, design a 4th-order, lumped-element, linear phase bandpass filter with a center frequency of 2.4 GHz and a bandwidth of 20% using the architecture of Fig. 8.25a. a) Determine the low-pass filter prototype element values. b) Draw a labeled sketch of the scaled and transformed filter with component values. c) Draw a labeled sketch of the filter in phasor form with $V_s = 1\angle 0^\circ$ V. d) Plot the amplitude response $|V_L|$ in decibels with horizontal dashed lines at $20\log(0.5)$ & $20\log(0.25)$ and vertical dashed lines at $2.4 \pm 10\%$ GHz for $0 \leq f \leq 5$ GHz and $-20\text{ dB} \leq |V_L| \leq 0$.
- 4) **EE 581 only:** 8.6 with ripple specification changed to 1.5 dB. a) Find the parameter k^2 as well as values k_{neg} & k_{pos} . b) Find the equations for the P_{LR} in terms of ω and the circuit component values. c) Find the two possible values for R , i.e., R_{small} & R_{big} . d) Find equations for realizable values of the inductance $L_{k\text{neg}}$ and $L_{k\text{pos}}$ in terms of R , C , and k_{neg} or k_{pos} . e) Equate ω^2 coefficients and then use the $L_{k\text{neg}}$ & $L_{k\text{pos}}$ equations to generate two polynomials in terms of C . f) Find R_s , L , C , & R and draw prototype low-pass filter circuit with component values. [Hints: Try all four permutations of k_{neg} , k_{pos} , R_{small} , and R_{big} in the polynomials to find the solution with realizable components. Consider using quadratic formula or numerical polynomial root solver.]

Due Monday, November 24, 2025 at my office or EECS dept. mail box by 4PM.

Note: For plots, you can use MathCAD or Matlab. Include either worksheet (MathCAD) or m-file & plots (Matlab) with each solution.