

EE 481/581 Microwave Engineering Quiz #2 (Fall 2025)

Name KEY A

Instructions: Open book & notes. Place answers in indicated spaces and show all work for credit.

A lossless transmission line (35Ω , 2.2×10^8 m/s) is 0.64λ long at 1.6 GHz. First, find the phase constant and length ℓ (cm) of the line. If the line is terminated with a load of $70 + j30 \Omega$, determine the SWR, load reflection coefficient (polar format w/ angle in degrees), and input impedance (rectangular format).

$$\text{Per (2.16), } v_p = \frac{\omega}{\beta} \Rightarrow \beta = \frac{\omega}{v_p} = \frac{2\pi(1.6 \times 10^9)}{2.2 \times 10^8} \Rightarrow \underline{\beta = 45.695893 \text{ rad/m.}}$$

$$\text{Per (2.15), } \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{45.695893} = 0.1375 \text{ m.}$$

$$\text{Therefore, the TL length is } \ell = 0.64\lambda = 0.64(13.75 \text{ cm}) \Rightarrow \underline{\ell = 8.8 \text{ cm.}}$$

$$\text{Per (2.35), } \Gamma = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(70 + j30) - 35}{(70 + j30) + 35} \Rightarrow \underline{\Gamma_L = 0.422134 \angle 24.6559^\circ.}$$

$$\text{Per (2.41), } \text{SWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.422134}{1 - 0.422134} \Rightarrow \underline{\text{SWR} = 2.461.}$$

$$\text{Per (2.44), } Z_{\text{in}} = Z_0 \frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)} = 35 \frac{(70 + j30) + j35 \tan(2\pi \cdot 0.64)}{35 + j(70 + j30) \tan(2\pi \cdot 0.64)} \\ \Rightarrow \underline{Z_{\text{in}} = 29.47006 - j29.39467 \Omega.}$$

$$\text{phase constant} = \underline{\beta = 45.696 \text{ rad/m}} \quad \ell = \underline{8.8 \text{ cm}} \quad \text{SWR} = \underline{2.461}$$

$$\text{load refl. coeff.} = \underline{\Gamma_L = 0.4221 \angle 24.656^\circ} \quad \text{input imp.} = \underline{Z_{\text{in}} = 29.47 - j29.395 \Omega}$$

EE 481/581 Microwave Engineering Quiz #2 (Fall 2025)

Name KEY B

Instructions: Open book & notes. Place answers in indicated spaces and show all work for credit.

A lossless transmission line (65Ω , 2.4×10^8 m/s) is 0.68λ long at 1.4 GHz. First, find the phase constant and length ℓ (cm) of the line. If the line is terminated with a load of $30 + j70 \Omega$, determine the SWR, load reflection coefficient (polar format w/ angle in degrees), and input impedance (rectangular format).

$$\text{Per (2.16), } v_p = \frac{\omega}{\beta} \Rightarrow \beta = \frac{\omega}{v_p} = \frac{2\pi(1.4 \times 10^9)}{2.4 \times 10^8} \Rightarrow \underline{\beta = 36.65191 \text{ rad/m.}}$$

$$\text{Per (2.15), } \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{36.65191} = 0.171429 \text{ m} = 17.1429 \text{ cm.}$$

$$\text{Therefore, the TL length is } \ell = 0.68\lambda = 0.68(17.1429 \text{ cm}) \Rightarrow \underline{\ell = 11.6571 \text{ cm.}}$$

$$\text{Per (2.35), } \Gamma = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(30 + j70) - 65}{(30 + j70) + 65} \Rightarrow \underline{\Gamma_L = 0.663217 \angle 80.1807^\circ.}$$

$$\text{Per (2.41), } \text{SWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.663217}{1 - 0.663217} \Rightarrow \underline{\text{SWR} = 4.9385.}$$

$$\begin{aligned} \text{Per (2.44), } Z_{\text{in}} &= Z_0 \frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)} = 65 \frac{(30 + j70) + j65 \tan(2\pi \cdot 0.68)}{65 + j(30 + j70) \tan(2\pi \cdot 0.68)} \\ &\Rightarrow \underline{Z_{\text{in}} = 63.1025 - j113.4893 \Omega.} \end{aligned}$$

$$\text{phase constant} = \underline{\beta = 36.652 \text{ rad/m}} \quad \ell = \underline{11.657 \text{ cm}} \quad \text{SWR} = \underline{4.9385}$$

$$\text{load refl. coeff.} = \underline{\Gamma_L = 0.6632 \angle 80.181^\circ} \quad \text{input imp.} = \underline{Z_{\text{in}} = 63.103 - j113.489 \Omega}$$