

EE 481/581 Microwave Engineering

Quiz #3 (Fall 2025)

Name KEY A

Instructions: Closed book & notes. Place answers in indicated spaces and show all work for credit.

A lossless transmission line ($80\ \Omega$, $2.42 \times 10^8\ \text{m/s}$) of length $18.235\ \text{cm}$ has a measured input impedance of $128 + j144\ \Omega$ at $2.2\ \text{GHz}$. Then, using a Smith chart, find the input admittance & reflection coefficient, load impedance & reflection coefficient, standing wave ratio (SWR), and return loss (RL). **Show and clearly label** all work on the Smith chart (this will be graded).

- Normalize $z_{\text{in}} = Z_{\text{in}} / Z_0 = (128 + j144) / 80 \Rightarrow z_{\text{in}} = \mathbf{1.6 + j1.8\ \Omega/\Omega}$.
- Plot z_{in} on Smith chart by finding intersection of $r=1.6$ circle with $x=1.8$ arc.
- Set compass to distance from center of Smith chart to z_{in} point. Draw circle, centered on Smith Chart, through z_{in} point.
- Use compass to make marks on 'RFL COEFF, E or I', 'SWR', and 'RTN LOSS (dB)' scales. Read off $|\Gamma| = \mathbf{0.6}$, $\mathbf{SWR = 4}$, and $\mathbf{RL = 4.4\ dB}$.
- Use straightedge to draw radial line from center of Smith chart to outer rings. Use "ANGLE OF REFLECTION COEFFICIENT IN DEGREES" scale to read $\angle\Gamma_{\text{in}} = \mathbf{36.9^\circ}$. Put the magnitude and angle together to get the input reflection coefficient $\mathbf{\Gamma_{\text{in}} = 0.6\angle 36.9^\circ}$.
- Use straightedge to extend radial line across Smith chart. Read normalized input admittance $y_{\text{in}} = \mathbf{0.275 - j0.31\ S/S}$ where radial line intersects circle of constant $|\Gamma|$ opposite to z_{in} (i.e., 180°). Unnormalize to get $Y_{\text{in}} = y_{\text{in}} / Z_0 = (0.275 - j0.31) / 80 \Rightarrow \mathbf{Y_{\text{in}} = 0.00344 - j0.00388\ S = 3.44 - j3.88\ mS}$.
- Calculate wavelength to be $\lambda = v_p / f = 2.42 \times 10^8 / 2.2 \times 10^9 = 0.11\ \text{m} = 11\ \text{cm}$. The TL length in wavelengths is $\ell/\lambda = 18.235 / 11 = 1.6577$. Subtract $3(0.5) = 1.5$ (i.e., remove integer multiples of $n\lambda/2$) to get $\ell/\lambda = \mathbf{0.1577}$.
- Move $\ell/\lambda = \mathbf{0.1577}$ in the "WAVELENGTHS TOWARD LOAD" direction on arc of constant $|\Gamma|$ from input point (0.3012) to load point ($0.3012 + 0.1577 = 0.4589$) and draw radial line from center of Smith chart.
- At load point, read $\angle\Gamma_L = \mathbf{150.4^\circ}$ on "ANGLE OF REFLECTION COEFFICIENT IN DEGREES" scale and $z_L = \mathbf{0.27 + j0.244\ \Omega/\Omega}$. The load reflection coefficient is then $\mathbf{\Gamma_L = 0.6\angle 150.4^\circ}$ and load impedance is $Z_L = z_L Z_0 = (0.27 + j0.244) 80 \Rightarrow \mathbf{Z_L = 21.6 + j19.52\ \Omega}$.

SWR = 4 $Y_{\text{in}} = \mathbf{3.44 - j3.88\ mS}$ input refl. coeff. = $\mathbf{\Gamma_{\text{in}} = 0.6\angle 36.9^\circ}$

RL = 4.4 dB load refl. coeff. = $\mathbf{\Gamma_L = 0.6\angle 150.4^\circ}$ $Z_L = \mathbf{21.6 + j19.52\ \Omega}$

Exact answers-

$$\text{SWR} = \underline{4}$$


$$Y_{\text{in}} = \underline{3.45 - j 3.88 \text{ mS}}$$

$$\text{input refl. coeff.} = \underline{\Gamma_{\text{in}} = 0.6 \angle 36.87^\circ}$$

$$\text{RL} = \underline{4.44 \text{ dB}}$$

$$\text{load refl. coeff.} = \underline{\Gamma_L = 0.6 \angle 150.43^\circ}$$
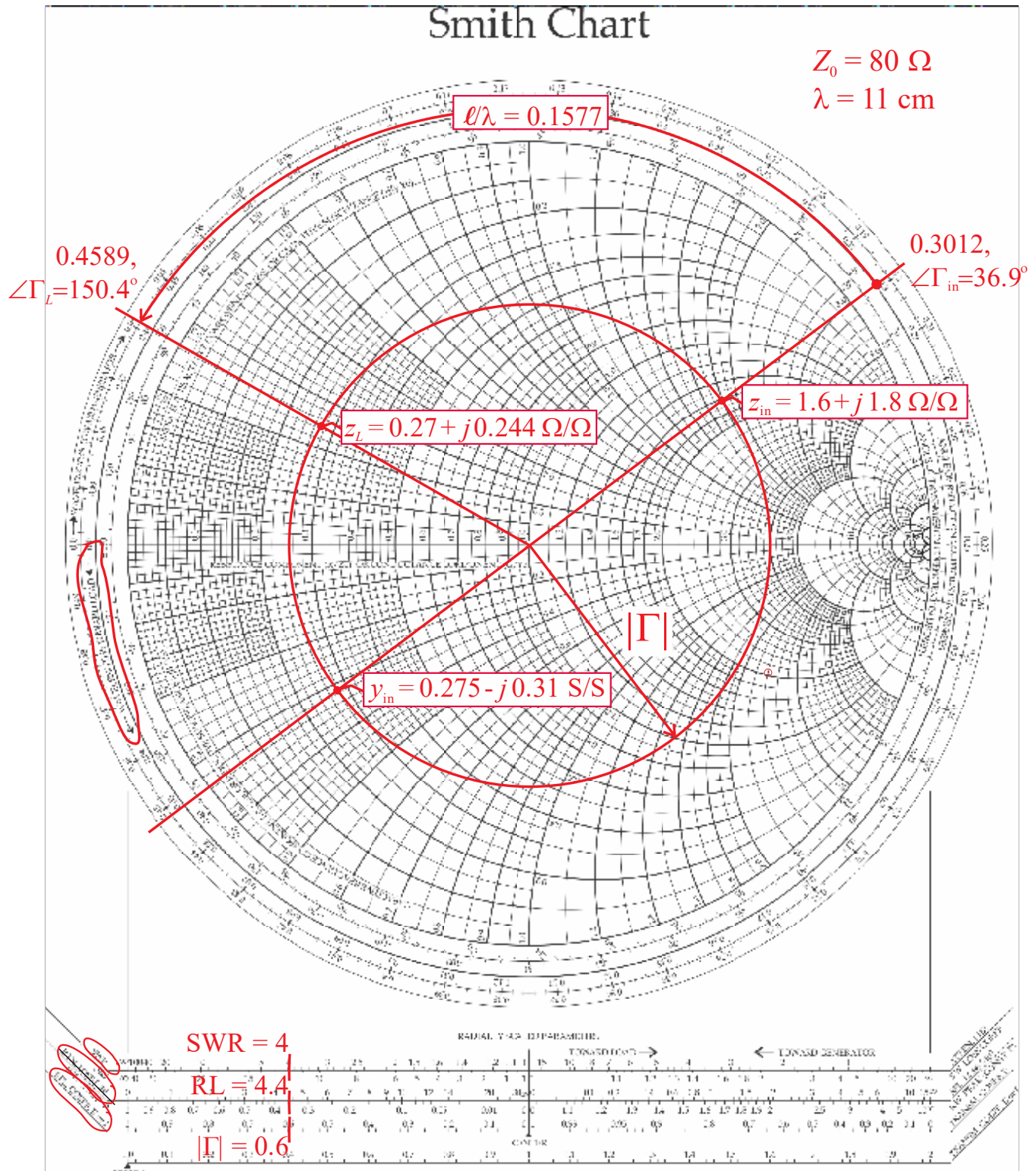
$$Z_L = \underline{21.3 + j 19.71 \Omega}$$



EE 481/581 Microwave Engineering

Quiz #3 (Fall 2025)

Name KEY B

Instructions: Closed book & notes. Place answers in indicated spaces and show all work for credit.

A lossless transmission line ($120\ \Omega$, $2.208 \times 10^8\ \text{m/s}$) of length $24.99\ \text{cm}$ has a measured input impedance of $72 - j96\ \Omega$ at $2.4\ \text{GHz}$. Then, using a Smith chart, find the input admittance & reflection coefficient, load impedance & reflection coefficient, standing wave ratio (SWR), and return loss (RL). **Show and clearly label** all work on the Smith chart (this will be graded).

- Normalize $z_{\text{in}} = Z_{\text{in}} / Z_0 = (72 - j96) / 120 \Rightarrow z_{\text{in}} = \mathbf{0.6 - j0.8\ \Omega/\Omega}$.
- Plot z_{in} on Smith chart by finding intersection of $r=0.6$ circle with $x=-0.8$ arc.
- Set compass to distance from center of Smith chart to z_{in} point. Draw circle, centered on Smith Chart, through z_{in} point.
- Use compass to make marks on 'RFL COEFF, E or I', 'SWR', and 'RTN LOSS (dB)' scales. Read off $|\Gamma| = \mathbf{0.5}$, $\mathbf{SWR = 3}$, and $\mathbf{RL = 6\ dB}$.
- Use straightedge to draw radial line from center of Smith chart to outer rings. Use "ANGLE OF REFLECTION COEFFICIENT IN DEGREES" scale to read $\angle\Gamma_{\text{in}} = \mathbf{-90^\circ}$. Put the magnitude and angle together to get the input reflection coefficient $\mathbf{\Gamma_{\text{in}} = 0.5 \angle -90^\circ}$.
- Use straightedge to extend radial line across Smith chart. Read normalized input admittance $y_{\text{in}} = \mathbf{0.6 + j0.8\ S/S}$ where radial line intersects circle of constant $|\Gamma|$ opposite to z_{in} (i.e., 180°). Unnormalize to get $Y_{\text{in}} = y_{\text{in}} / Z_0 = (0.6 + j0.8) / 120 \Rightarrow \mathbf{Y_{\text{in}} = 0.005 + j0.00667\ S = 5 + j6.67\ mS}$.
- Calculate wavelength to be $\lambda = v_p / f = 2.208 \times 10^8 / 2.4 \times 10^9 = 0.092\ \text{m} = 9.2\ \text{cm}$. The TL length in wavelengths is $\ell/\lambda = 24.99 / 9.2 = 2.7163$. Subtract $5(0.5) = 2.5$ (i.e., remove integer multiples of $n\lambda/2$) to get $\ell/\lambda = \mathbf{0.2163}$.
- Move $\ell/\lambda = \mathbf{0.2163}$ in the "WAVELENGTHS TOWARD LOAD" direction on arc of constant $|\Gamma|$ from input point (0.125) to load point ($0.125 + 0.2163 = 0.3413$) and draw radial line from center of Smith chart.
- At load point, read $\angle\Gamma_L = \mathbf{65.8^\circ}$ on "ANGLE OF REFLECTION COEFFICIENT IN DEGREES" scale and $\mathbf{z_L = 0.9 + j1.09\ \Omega/\Omega}$. The load reflection coefficient is then $\mathbf{\Gamma_L = 0.5 \angle 65.8^\circ}$ and load impedance is $Z_L = z_L Z_0 = (0.9 + j1.09) 120 \Rightarrow \mathbf{Z_L = 108 + j130.8\ \Omega}$.

SWR = 3 $Y_{\text{in}} = \mathbf{5 + j6.67\ mS}$ input refl. coeff. = $\mathbf{\Gamma_{\text{in}} = 0.5 \angle -90^\circ}$

RL = 6 dB load refl. coeff. = $\mathbf{\Gamma_L = 0.5 \angle 65.8^\circ}$ $Z_L = \mathbf{108 + j130.8\ \Omega}$

Exact answers-

$$\text{SWR} = \underline{3} \quad Y_{\text{in}} = \underline{5 + j 6.67 \text{ mS}} \quad \text{input refl. coeff.} = \underline{\Gamma_{\text{in}} = 0.5 \angle -90^\circ}$$

$$\text{RL} = \underline{6.02 \text{ dB}} \quad \text{load refl. coeff.} = \underline{\Gamma_L = 0.5 \angle 65.74^\circ} \quad Z_L = \underline{107.26 + j 130.379 \Omega}$$

