

EE 481/581 Microwave Engineering Quiz #10 (Fall 2025)

Name

Key A

Instructions: Open notes/text. Place answers in indicated spaces. Show & clearly label all work for partial credit.

Design a maximally flat low-pass filter prototype with an attenuation of at least 30 dB at three times the cutoff frequency of the minimum order N and the immittance values g_0 to g_{N+1} . Assume a prototype design which starts with an inductor. The filter is to be implemented using a stepped-impedance design in a $60\ \Omega$ system where the lowest and highest practical impedances are $25\ \Omega$ and $120\ \Omega$. Fill out the table provided with the immittance (F or H), impedance (highest or lowest practical value), and electrical length βl_i (rad and degrees) of each section going from 1 to N . [Rows may be added or skipped as necessary.]


$$\left| \frac{\omega}{\omega_c} \right| - 1 = \left| \frac{3\omega_c}{\omega_c} \right| - 1 = 2 \rightarrow \text{plot on Fig 8.26}$$

Read $N=4$, as first trace above 30dB.

$g_0 = g_5 = 1$ are for source & load resistances.

$$g_1 = 0.7654 = L_1, \quad g_2 = 1.8478 = C_2,$$
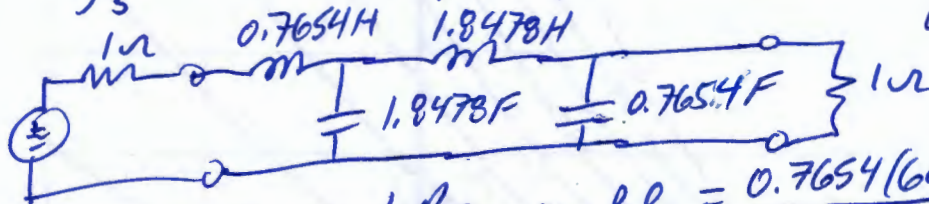
$$g_3 = 1.8478 = L_3, \quad g_4 = 0.7654 = C_4 \quad \left. \begin{array}{l} \text{Filter} \\ \text{Prototype} \end{array} \right\}$$



$$(8.86a) \beta l = \frac{L R_0}{Z_n} \Rightarrow \beta l_1 = \frac{0.7654(60)}{120} = 0.3827 = 21.927^\circ$$

$$(inductor) \Rightarrow \beta l_3 = \frac{1.8478(60)}{120} = 0.9239 = 52.936^\circ$$

$$(8.86b) \beta l = \frac{C Z_0}{R_0} \Rightarrow \beta l_2 = \frac{1.8478(25)}{60} = 0.7699 = 44.113^\circ$$

$$(capacitor) \Rightarrow \beta l_4 = \frac{0.7654(25)}{60} = 0.3189 = 18.273^\circ$$

Prototype: $N = 4$

Section	Prototype immittance	Characteristic Impedance (Ω)	βl_i (rad)	βl_i (deg)
1	0.7654H	120	0.3827	21.93
2	1.8478F	25	0.7699	44.11
3	1.8478H	120	0.9239	52.94
4	0.7654F	25	0.3189	18.27

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

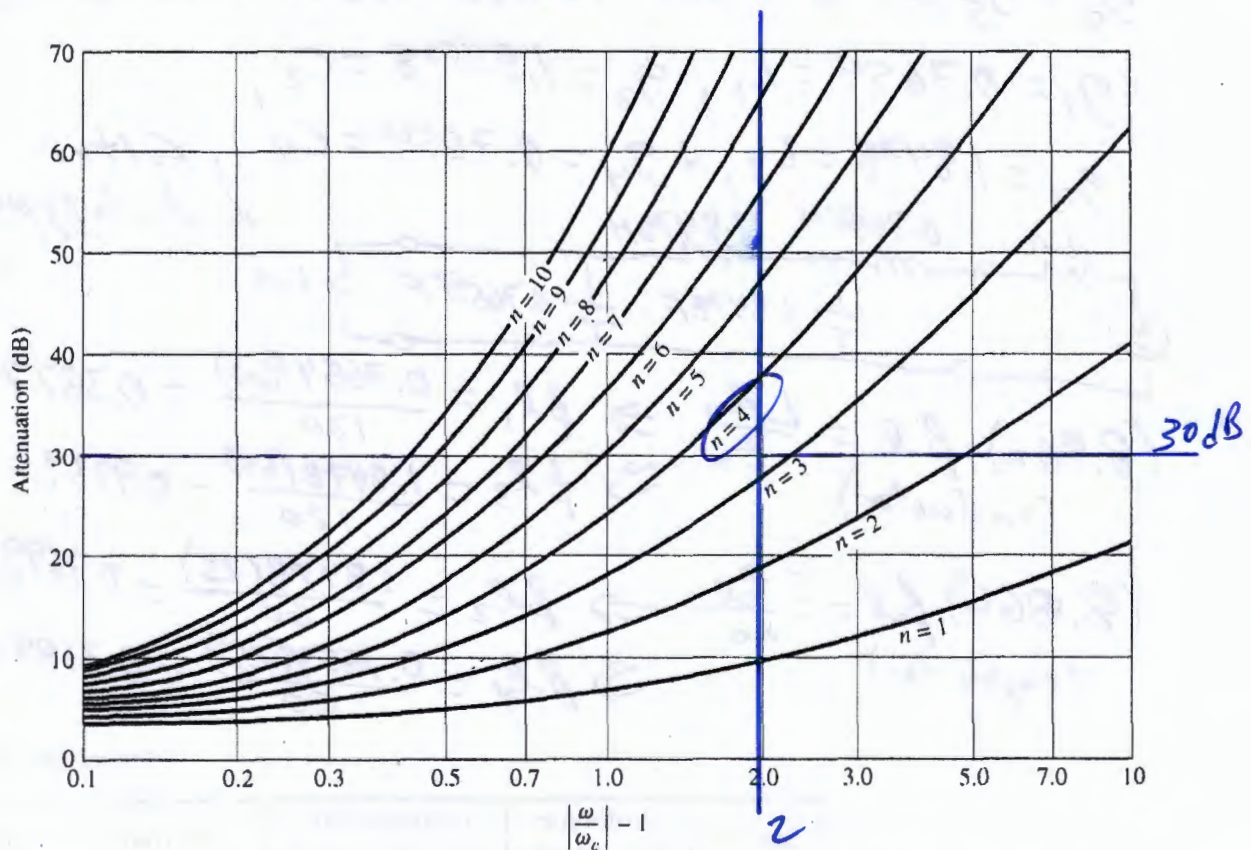


FIGURE 8.26 Attenuation versus normalized frequency for maximally flat filter prototypes. Adapted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

EE 481/581 Microwave Engineering Quiz #10 (Fall 2025)

Name

Key B

Instructions: Open notes/text. Place answers in indicated spaces. Show & clearly label all work for partial credit.

Design a maximally flat low-pass filter prototype with an attenuation of at least 40 dB at four times the cutoff frequency of the minimum order N and the immittance values g_0 to g_{N+1} . Assume a prototype design which starts with an inductor. The filter is to be implemented using a stepped-impedance design in a 55Ω system where the lowest and highest practical impedances are 20Ω and 110Ω . Fill out the table provided with the immittance (F or H), impedance (highest or lowest practical value), and electrical length βl_i (rad and degrees) of each section going from 1 to N . [Rows may be added or skipped as necessary.]

$$\left| \frac{\omega}{\omega_c} \right| - 1 = \left| \frac{4\omega_c}{\omega_c} \right| - 1 = 3 \rightarrow \text{Plot on Fig 8.26}$$


Read $N=4$, as first trace above 40dB.

$g_0 = g_5 = 1$ are for source & load resistances,

$$g_1 = 0.7654 = L_1, \quad g_2 = 1.8478 = C_2, \quad g_3 = 1.8478 = L_3, \quad \&$$

$$g_4 = 0.7654 = C_4.$$

LPF prototype

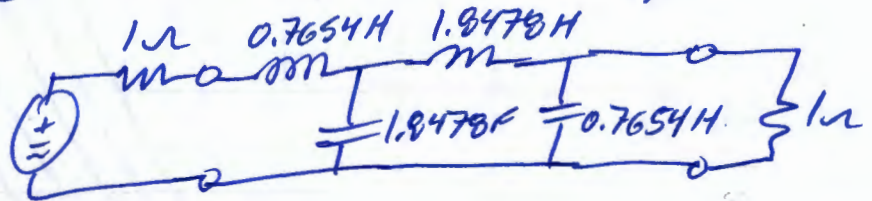

$$(8.86a) \quad \beta l = \frac{L \eta_0}{Z_h} \Rightarrow \frac{0.7654(55)}{110} = 0.3827 = 21.927^\circ = \beta l_1$$

$$\Rightarrow \frac{1.8478(55)}{110} = 0.9239 = 52.936^\circ = \beta l_3$$

$$(8.86b) \quad \beta l = \frac{C Z_e}{\eta_0} \Rightarrow \frac{1.8478(20)}{55} = 0.6719 = 38.4986^\circ = \beta l_2$$

$$\Rightarrow \frac{0.7654(20)}{55} = 0.2783 = 15.947^\circ = \beta l_4$$

Prototype: $N = 4$

Section	Prototype immittance	Characteristic Impedance (Ω)	βl_i (rad)	βl_i (deg)
1	0.7654H	110	0.3827	21.93
2	1.8478F	20	0.6719	38.50
3	1.8478H	110	0.9239	52.94
4	0.7654F	20	0.2783	15.95

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

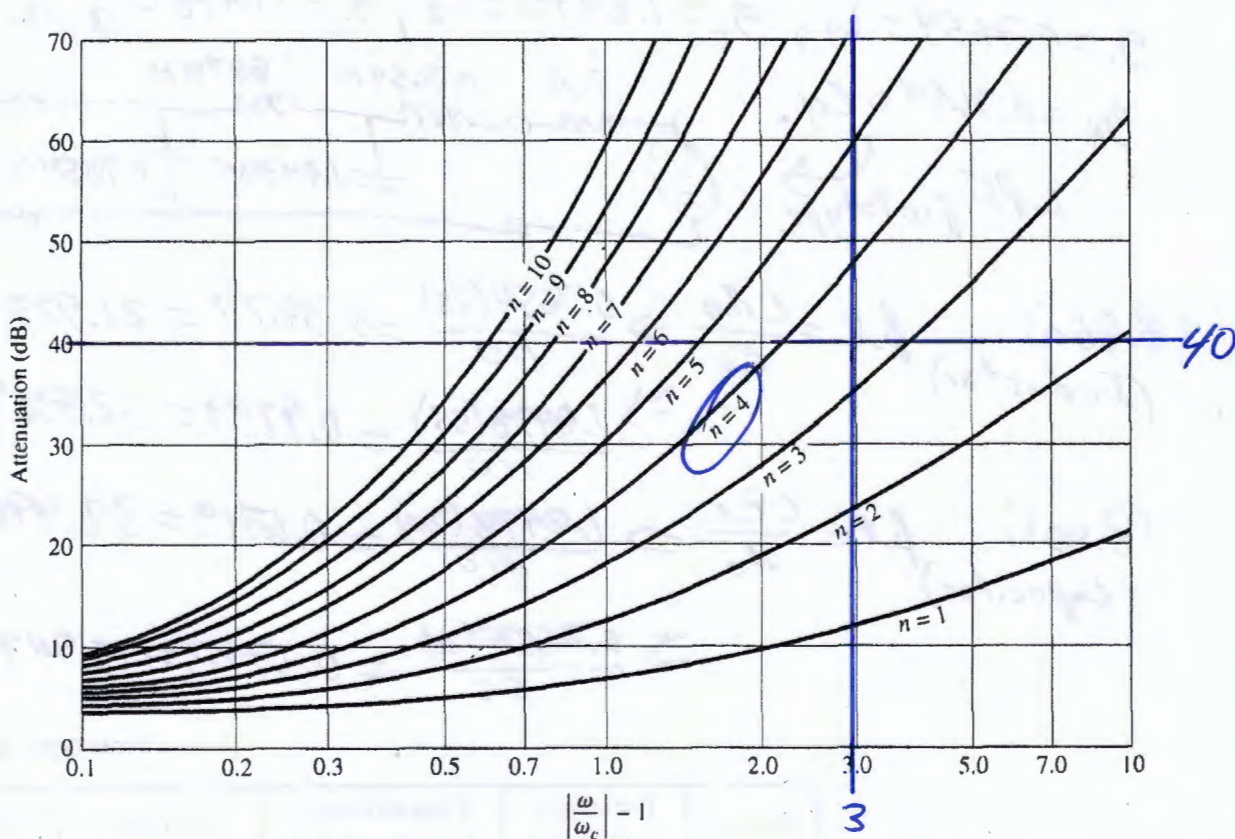


FIGURE 8.26 Attenuation versus normalized frequency for maximally flat filter prototypes. Adapted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.