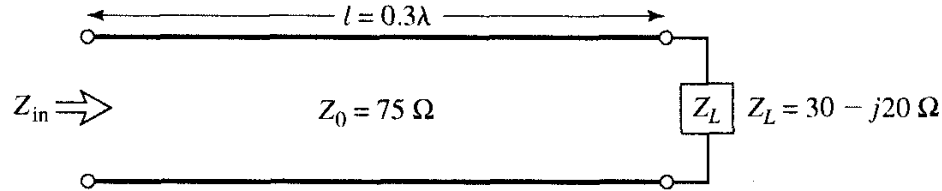


For the transmission line of problem 2.8, analytically determine the locations (in terms of λ) of all possible current and voltage maxima and/or minima.

2.8 A lossless transmission line of electrical length $\ell = 0.3\lambda$ is terminated with a complex load impedance as shown in the accompanying figure. Find the reflection coefficient at the load, the SWR on the line, the reflection coefficient at the input of the line, and the input impedance to the line.



$$\text{Per (2.35), } \Gamma = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(30 - j20) - 75}{(30 - j20) + 75} \Rightarrow \underline{\Gamma_L = 0.46071 \angle -145.2532^\circ}.$$

Using (2.10), $\beta = 2\pi / \lambda$. Therefore, $\beta \ell = 2\pi (0.3) = 0.6 \pi = 1.88496 \text{ rad}$.

$$\text{Per (2.42), } \Gamma(\ell) = \Gamma_{in} = \Gamma(0)e^{-2j\beta\ell} = \Gamma_L e^{-2j\beta\ell} = (0.46071 \angle -145.2532^\circ)e^{-2j1.88496} \Rightarrow \underline{\Gamma_{in} = 0.46071 \angle -1.2532^\circ}.$$

$$\text{Per (2.43), } Z_{in} = \frac{1 + \Gamma e^{-2j\beta\ell}}{1 - \Gamma e^{-2j\beta\ell}} Z_0 = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 75 \left(\frac{1 + 0.4607 \angle -1.253^\circ}{1 - 0.4607 \angle -1.253^\circ} \right) \Rightarrow \underline{Z_{in} = 202.99 - j5.19 \Omega}.$$

Per (2.39), $|V(z)| = |V_0^+| |1 + |\Gamma| e^{j(\theta - 2\beta\ell)}|$ where $\ell = -z$ (distance from the load).

As covered on page 58, the voltage maxima (and current minima) occur at locations where $e^{j(\theta - 2\beta\ell)} = 1 \Rightarrow \theta - 2\beta\ell = 2\pi n$ ($n = 0, \pm 1, \pm 2, \dots$). Using (2.10), $\beta = 2\pi / \lambda$ and $\theta = -145.2532^\circ = -2.53515 \text{ rad}$, we get

$$\ell_{V_{\max}} = \ell_{I_{\min}} = [(\theta - 2\pi n) / 4\pi] \lambda = [(-2.53515 - 2\pi n) / 4\pi] \lambda$$

The smallest positive value (& only point on the TL) for $\ell_{V_{\max}}$ occurs when $n = -1$,

$$\ell_{V_{\max}} = \ell_{I_{\min}} = [(-2.53515 + 2\pi) / 4\pi] \lambda = 0.29826 \lambda \Rightarrow \underline{\ell_{V_{\max}} = \ell_{I_{\min}} = 0.29826 \lambda}.$$

As covered on p. 58, the voltage minima (& current maxima) occur at locations where $e^{j(\theta - 2\beta\ell)} = -1 \Rightarrow \theta - 2\beta\ell = \pi(2n+1)$ ($n = 0, \pm 1, \pm 2, \dots$). This yields-

$$\ell_{V_{\min}} = \ell_{I_{\max}} = [(\theta - \pi(2n+1)) / 4\pi] \lambda = [(-2.53515 - \pi(2n+1)) / 4\pi] \lambda$$

The smallest positive value (& only point on the TL) for ℓ_{Vmin} occurs when $n = -1$,

$$\ell_{Vmin} = \ell_{I_{max}} = [(-2.53515 + \pi)/4\pi]\lambda = 0.048259\lambda \Rightarrow \underline{z_{Vmin} = z_{I_{max}} = -0.04826\lambda}.$$

Verified answers using MathCad-

$$\lambda \coloneqq 0.3 \quad Z_L \coloneqq 30 - j \cdot 20 \quad \Omega \quad Z_0 \coloneqq 75 \quad \Omega \quad Z_g \coloneqq 75 \quad \Omega \quad V_g \coloneqq 10 \quad V$$

$$Z_{in} \coloneqq Z_L$$

$$(2.35) \quad \Gamma_L \coloneqq \frac{Z_L - Z_0}{Z_L + Z_0} \quad |\Gamma_L| = 0.46071 \quad \arg(\Gamma_L) \cdot \frac{180}{\pi} = -145.2532 \quad \text{deg}$$

$$\Gamma_{in} \coloneqq \Gamma_L \cdot e^{-j \cdot 2 \cdot \pi \cdot \lambda} \quad |\Gamma_{in}| = 0.46071 \quad \arg(\Gamma_{in}) \cdot \frac{180}{\pi} = -1.2532 \quad \text{deg}$$

$$\underline{Z_{in}} \coloneqq Z_0 \cdot \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \quad Z_{in} = 202.99 - 5.193i \quad \Omega$$

$$V_{in} \coloneqq V_g \cdot \frac{Z_{in}}{Z_g + Z_{in}} \quad |V_{in}| = 7.30317 \quad V \quad \arg(V_{in}) \cdot \frac{180}{\pi} = -0.3953 \quad \text{deg}$$

$$(2.36a) \quad V_{0p} \coloneqq \frac{V_{in}}{e^{j \cdot 2 \cdot \pi \cdot \lambda} + \Gamma_L \cdot e^{-j \cdot 2 \cdot \pi \cdot \lambda}} \quad |V_{0p}| = 5 \quad V \quad \arg(V_{0p}) \cdot \frac{180}{\pi} = -108 \quad \text{deg}$$

$$(2.40a) \quad V_{max} \coloneqq |V_{0p}| \cdot (1 + |\Gamma_L|) \quad V_{max} = 7.3036 \quad V$$

$$(2.40b) \quad V_{min} \coloneqq |V_{0p}| \cdot (1 - |\Gamma_L|) \quad V_{min} = 2.6964 \quad V$$

$$n \coloneqq 0..100 \quad z_n \coloneqq -0.3 + \frac{n \cdot 0.3}{100} \quad (2.36a) \quad \underline{V(z)} \coloneqq V_{0p} \cdot (e^{-j \cdot 2 \cdot \pi \cdot z} + \Gamma_L \cdot e^{j \cdot 2 \cdot \pi \cdot z})$$

