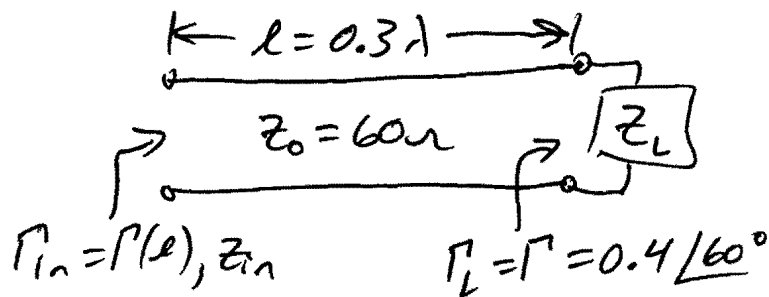


- 2.10** A terminated transmission line with $Z_0 = 60 \Omega$ has a reflection coefficient at the load of $\Gamma = 0.4 \angle 60^\circ$.
 (a) What is the load impedance? (b) What is the reflection coefficient 0.3λ away from the load? (c) What is the input impedance at this point?



a) Per (2.35), re-arranged,
$$Z_L = Z_0 \left(\frac{1 + \Gamma}{1 - \Gamma} \right) = 60 \left(\frac{1 + 0.4 \angle 60^\circ}{1 - 0.4 \angle 60^\circ} \right)$$

$$\underline{\underline{Z_L = 66.316 + j54.696 \Omega}}$$

b) Per (2.42)

$$\begin{aligned} \Gamma_{in} = \Gamma(l = 0.3\lambda) &= \Gamma_L e^{-j2\beta l} \\ &= (0.4 \angle 60^\circ) e^{-j2 \frac{2\pi}{\lambda} 0.3\lambda} \end{aligned}$$

$$\underline{\underline{\Gamma_{in} = 0.4 \angle -156^\circ}}$$

c) Per (2.43)

$$Z_{in} = \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} Z_0 = \left(\frac{1 + 0.4 \angle -156^\circ}{1 - 0.4 \angle -156^\circ} \right) 60$$

$$\underline{\underline{Z_{in} = 26.655 - j10.325 \Omega}}$$