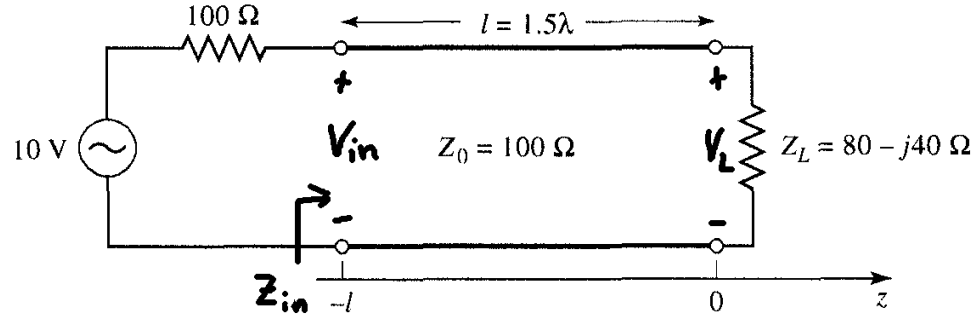


**2.19** A generator is connected to a transmission line as shown in the accompanying figure. Find the voltage as a function of  $z$  along the transmission line. Plot the magnitude of this voltage for  $-\ell \leq z \leq 0$ .



Per (2.35),  $\Gamma = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(80 - j40) - 100}{(80 - j40) + 100} \Rightarrow \Gamma_L = 0.24253 \angle -104.04^\circ$ .

Note that the TL is  $1.5\lambda$  long, an integer multiple of  $\lambda/2$  long. Therefore, the input impedance  $Z_{in} = Z_L$  and  $V_{in} = V_L$ . By voltage division

$$V_{in} = V_L = V_g \frac{Z_{in}}{Z_g + Z_{in}} = 10 \frac{80 - j40}{100 + (80 - j40)} \Rightarrow V_{in} = V_L = 4.8507 \angle -14.036^\circ.$$

Using (2.36a)  $V(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$ , we can solve for  $V_0^+$  at  $z = 0$  as

$$V_0^+ = \frac{V(0)}{1 + \Gamma} = \frac{V_L}{1 + \Gamma} = \frac{4.8507 \angle -14.036^\circ}{1 + 0.24253 \angle -104.04^\circ} \Rightarrow V_0^+ = 5 \angle 0^\circ.$$

Using  $\beta = 2\pi/\lambda$ , we can now express the phasor voltage as

$$V(z) = 5 \left( e^{-j2\pi z} + (0.24253 \angle -104.04^\circ) e^{j2\pi z} \right) \text{ where } -1.5\lambda \leq z \leq 0.$$

As shown below, these equations were implemented in MathCAD to get the desired plot of  $|V(z)|$  for  $-1.5\lambda \leq z \leq 0$ .

As expected, per (2.40a),  $V_{\max} = |V_0^+| (1 + |\Gamma|) = 5 (1 + 0.24253) = 6.213 \text{ V}$ .

As expected, per (2.40b),  $V_{\min} = |V_0^+| (1 - |\Gamma|) = 5 (1 - 0.24253) = 3.787 \text{ V}$ .

$$\lambda := 1.5 \quad Z_L := 80 - j40 \quad \Omega \quad Z_0 := 100 \quad \Omega \quad Z_g := 100 \quad \Omega \quad V_g := 10 \quad V$$

$$Z_{in} := Z_L$$

$$(2.35) \quad \Gamma_L := \frac{Z_L - Z_0}{Z_L + Z_0} \quad |\Gamma_L| = 0.24254 \quad \arg(\Gamma_L) \cdot \frac{180}{\pi} = -104.0362 \quad \text{deg}$$

$$V_{in} := V_g \cdot \frac{Z_{in}}{Z_g + Z_{in}} \quad |V_{in}| = 4.85071 \quad V \quad \arg(V_{in}) \cdot \frac{180}{\pi} = -14.0362 \quad \text{deg}$$

$$(2.36a) \quad V_{0p} := \frac{V_{in}}{1 + \Gamma_L} \quad V_{0p} = 5 \quad V$$

$$(2.40a) \quad V_{max} := V_{0p} \cdot (1 + |\Gamma_L|) \quad V_{max} = 6.2127 \quad V$$

$$(2.40b) \quad V_{min} := V_{0p} \cdot (1 - |\Gamma_L|) \quad V_{min} = 3.7873 \quad V$$

$$n := 0..100 \quad z_n := -1.5 + \frac{n \cdot 1.5}{100} \quad (2.36a) \quad \underline{V(z)} := V_{0p} \cdot (e^{-j \cdot 2 \cdot \pi \cdot z} + \Gamma_L \cdot e^{j \cdot 2 \cdot \pi \cdot z})$$

