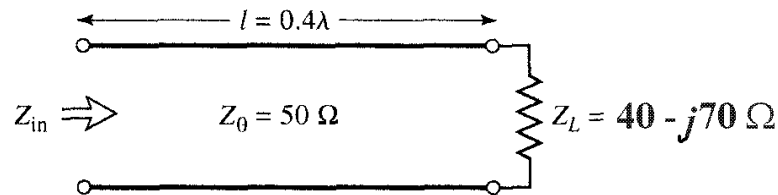


**2.20** Use the Smith chart to find the following quantities for the transmission line circuit shown in the accompanying figure:

- The SWR on the line.
- The reflection coefficient at the load.
- The load admittance.
- The input impedance of the line.
- The distance from the load to the first voltage minimum.
- The distance from the load to the first voltage maximum.



Normalize and plot load impedance

- $z_L = Z_L / Z_0 = (40 - j70) / 50 \Rightarrow z_L = 0.8 - j1.4 \Omega/\Omega$ .
- Plot  $z_L$  on Smith chart by finding intersection of  $r=0.8$  circle with  $x=-1.4$  arc.

**a) Find SWR**

- Use compass to draw  $|\Gamma|$  circle centered on Smith chart through  $z_L$ .
- Then, go to 'SWR (VSWR)' scale below Smith chart on left side and make mark using compass. Read  $\Rightarrow \text{SWR} = 4.25$ .

**b) Find load reflection coefficient**

- Use compass to mark the "RFL COEFF, E or I" scale below Smith chart on right side to determine  $|\Gamma_L| = 0.62$ .
- Use a straight edge to draw radial line from center of Smith chart through  $z_L$  and outer rings of Smith chart. Use the "ANGLE OF REFLECTION COEFFICIENT IN DEGREES" scale to read  $\angle \Gamma_L = -60.2^\circ$ .
- Put magnitude and angle together to get  $\Rightarrow \Gamma_L = 0.62 \angle -60.2^\circ$ .

**c) Find load admittance**

- Use a straight edge to extend radial line from center of Smith chart through  $z_L$  to other side of Smith chart.
- Read normalized input admittance at intersection of  $|\Gamma|$  circle and radial line at  $180^\circ$  opposite to  $z_L$  as  $y_L = 0.31 + j0.54 \text{ S/S}$ .
- Find input admittance by dividing  $y_L$  by  $Z_0$ .  $Y_L = y_L / Z_0 = (0.31 + j0.54 \text{ S/S}) / 50 \Omega \Rightarrow Y_L = 6.2 + j10.8 \text{ mS}$ .

**d) Find input impedance**

- Move  $\ell/\lambda = 0.4$  on circle of constant  $|\Gamma|$  from  $z_L$  point at  $0.166\lambda$  on 'WAVELENGTHS TOWARD LOAD' scale to  $0.234\lambda$  on 'WAVELENGTHS TOWARD GENERATOR' scale ( $0.166\lambda + 0.234\lambda = 0.4\lambda$ ). Draw radial line from center to outer edge of Smith chart. Intersection of line and circle is  $z_{in}$  point.
- At  $z_{in}$  point, read-off the normalized input resistance  $r_{in} = 3.6$  and input reactance  $x_{in} = 1.5$ , giving  $z_{in} = 3.6 + j 1.5 \Omega/\Omega$ .
- Find input impedance by multiplying  $z_{in}$  with  $Z_0$  to get  $Z_{in} = Z_0 z_{in} = 50(3.6 + j 1.5)$   
 $\Rightarrow \underline{Z_{in} = 180 + j 75 \Omega}$ .

**e) Find distance from load to  $V_{min}$** 

- The  $z_L$  point is at  $0.166\lambda$  on the 'WAVELENGTHS TOWARD LOAD' scale. If we move  $0.166\lambda$  in the 'WAVELENGTHS TOWARD GENERATOR' direction, we arrive at the  $V_{min}$  (and  $r_{min}$ ) point.  
 $\Rightarrow \underline{d_{min} = 0.166\lambda}$ .

**f) Find distance from load to  $V_{max}$** 

- The  $z_L$  point is at  $0.166\lambda$  on the 'WAVELENGTHS TOWARD LOAD' scale. If we move  $0.166\lambda + 0.25\lambda$  in the 'WAVELENGTHS TOWARD GENERATOR' direction, we arrive at the  $V_{max}$  (and  $r_{max}$ ) point.  
 $\Rightarrow \underline{d_{max} = 0.416\lambda}$ .

\*\*\*\*\*

**Bonus:**

For comparison, the exact values are-

$$\underline{SWR = 4.2656}$$

$$\underline{\Gamma_L = 0.6202 \angle -60.255^\circ}$$

$$\underline{Y_L = 6.154 + j 10.769 \text{ mS}}$$

$$\underline{\Gamma = 0.6022 \angle 109.8^\circ}$$

$$\underline{Z_{in} = 180.744 + j 74.155 \Omega}$$

$$\underline{d_{min} = 0.16631\lambda}$$

$$\underline{d_{max} = 0.41631\lambda}$$

2.20 mod1

Simple  
Smith Chart $Z_0 = 50\Omega$  $\lambda$  unspecified