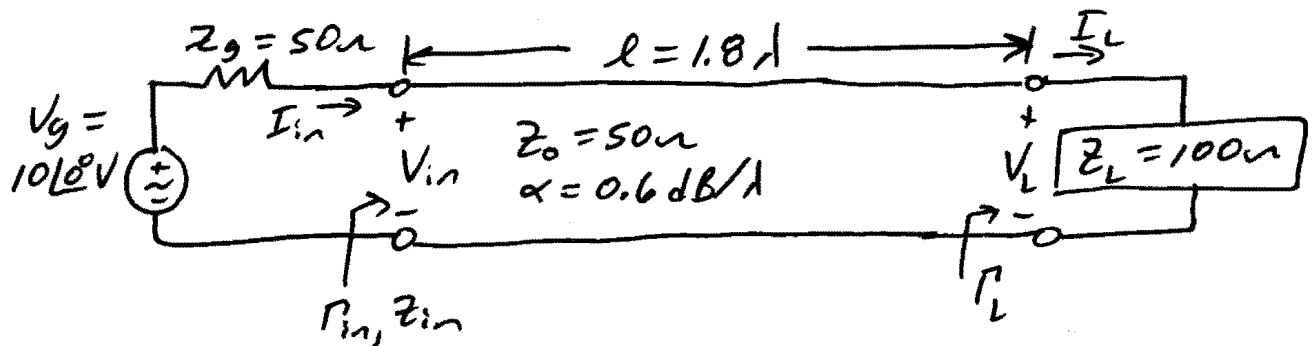


2.29 A $50\ \Omega$ transmission line is matched to a 10 V source and feeds a load $Z_L = 100\ \Omega$. If the line is 1.8λ long and has an attenuation constant $\alpha = 0.6\text{ dB}/\lambda$, find the powers that are delivered by the source, lost in the line, and delivered to the load.

➤ Find both P_{in} and P_{Vg} . Analytic solution.



$$\alpha = 0.6\text{ dB}/\lambda \left(\frac{1\text{ Np}}{20 \log e\text{ dB}} \right) = 0.069078\text{ Np}/\lambda$$

$$(2.10) \lambda = \frac{2\pi}{\beta} \Rightarrow \beta = \frac{2\pi}{\lambda}$$

$$(2.5) \gamma = \alpha + j\beta = (0.069078 + j2\pi)/\lambda$$

$$(2.35) \Gamma = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - 50}{100 + 50} = 0.33$$


$$(2.90) \Gamma(l) = \Gamma_{in} = \Gamma_L e^{-2\gamma l} = 0.33 e^{-2(0.069 + j2\pi)1.8}$$

$$\Gamma_{in} = 0.25994 \angle 144^\circ$$

$$(\text{notes}) Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 50 \frac{1 + 0.2599 \angle 144^\circ}{1 - 0.2599 \angle 144^\circ}$$

$$Z_{in} = 31.328 + j10.267\ \Omega$$

Equiv. input circuit

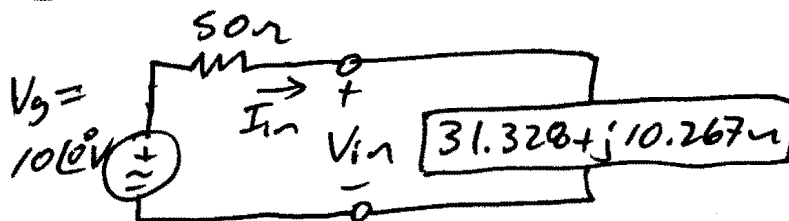

$$I_{in} = \frac{10\angle 0^\circ}{50 + (31.33 + j10.27)} = 0.12199 \angle -7.1951^\circ\text{ A}$$

$$V_{in} = 10\angle 0^\circ \frac{31.33 + j10.27}{50 + (31.33 + j10.27)} = 4.0217 \angle 10.9502^\circ\text{ V}$$

$$(2.92) P_{in} = \frac{1}{2} \operatorname{Re}(V_{in} I_n^*) = \frac{1}{2} \operatorname{Re}\{4.02 \angle 10.95^\circ (0.122 \angle 7.195^\circ)\}$$

$$\underline{P_{in} = 0.233107 \text{ W}}$$

$$(\text{Circuits}) P_g = \frac{1}{2} \operatorname{Re}\{V_g I_n^*\} = \frac{1}{2} \operatorname{Re}\{10 \angle 0^\circ (0.122 \angle 7.195^\circ)\}$$

$$\underline{P_g = 0.60515 \text{ W}}$$

Use (2.89a), $V(z) = V_0^+ (e^{-\gamma z} + \Gamma e^{\gamma z})$ and $V_n = V(z = -l)$

$$\text{to get } V_0^+ = \frac{4.0217 \angle 10.95^\circ}{e^{+(0.0691 + j2\pi)1.8} + 0.33 e^{-(0.0691 + j2\pi)1.8}}$$

$$V_0^+ = 4.4154 \angle 72^\circ \text{ V}$$

We can now compute V_L & I_L .

$$V_L = V(0) = 4.4154 \angle 72^\circ (e^{-10.0691 + j2\pi} + 0.33 e^{10.0691 + j2\pi})$$

$$V_L = 5.8872 \angle 72^\circ \text{ V}$$

$$I_L = V_L / Z_L = \frac{5.8872 \angle 72^\circ}{100} = 0.058872 \angle 72^\circ \text{ A}$$

$$\text{Per (2.93), } P_L = \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} = \frac{1}{2} \operatorname{Re}\{5.8872 \angle 72^\circ (0.058872 \angle -72^\circ)\}$$

$$\underline{P_L = 0.173296 \text{ W}}$$

$$\text{Per (2.94), } P_{loss} = P_{in} - P_L = 0.233107 - 0.173296$$

$$\underline{P_{loss} = 0.059812 \text{ W}}$$