

Using a lossless transmission line (75Ω and $v_p = 2.3 \times 10^8$ m/s), find the shortest a) open and b) short circuit stubs that appear as a 1 pF capacitor at 1.6 GHz.

Find phase constant (2.11): $\beta = \frac{\omega}{v_p} = \frac{2\pi(1.6 \times 10^9)}{2.3 \times 10^8} \Rightarrow \beta = 43.709115 \text{ rad/m}.$

Find 1 pF capacitor impedance:

$$Z_{1\text{pF}} = \frac{1}{j\omega C} = \frac{1}{j2\pi(1.6 \times 10^9)1 \times 10^{-12}} \Rightarrow Z_{1\text{pF}} = -j99.47184 \Omega.$$

a) Determine shortest possible length for an open circuit stub:

$$\begin{aligned} Z_{OC} &= Z_{2nH} \\ \frac{Z_0}{j \tan(\beta \ell_{oc})} &= \frac{75}{j \tan(43.709115 \ell_{oc})} = -j99.47184 \Omega \\ \ell_{oc} &= \frac{\tan^{-1}(75 / 99.47184)}{43.709115} \\ &\Rightarrow \underline{\ell_{oc} = 0.01478055 \text{ m} = 1.4781 \text{ cm}.} \end{aligned}$$

b) Determine shortest possible length for a short circuit stub:

$$\begin{aligned} Z_{SC} &= Z_{2nH} \\ jZ_0 \tan(\beta \ell_{sc}) &= j75 \tan(43.709 \ell_{sc}) = -j99.472 \Omega \\ \ell_{sc} &= \frac{\tan^{-1}(-99.472 / 75)}{43.709} \\ &\Rightarrow \underline{\ell_{sc} = -0.02115695 \text{ m (not realizable)}} \end{aligned}$$

Remember that one can always add integer multiples of half wavelength to transmission line lengths and get same impedance. Here the wavelength is:

$$\lambda = \frac{u}{f} = \frac{2.3 \times 10^8}{1.6 \times 10^9} = 0.14375 \text{ m} = 14.375 \text{ cm} \Rightarrow \underline{\lambda / 2 = 7.1875 \text{ cm}.}$$

So, the shortest possible realizable short circuit stub would have length:

$$\ell_{sc} = -2.115695 + 7.1875 \Rightarrow \underline{\ell_{sc} = 5.0718 \text{ cm}.}$$

Open circuit stub wins! However, both are equivalent to a 1 pF capacitor at 1.6 GHz.