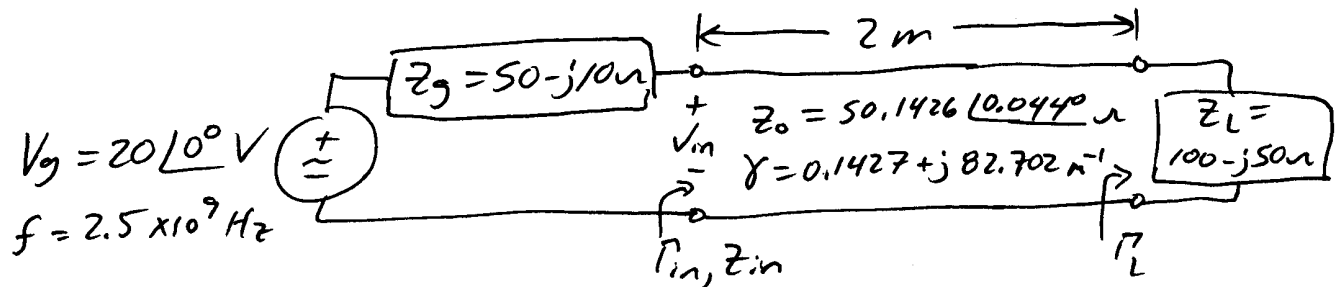


Use a 2 m length of the Victorian coaxial transmission line to create a TL circuit with  $V_g = 20\angle 0^\circ$  V,  $Z_g = 50 - j10 \Omega$ , and  $Z_L = 100 - j50 \Omega$  operating at 2.5 GHz. Find: a) the load reflection coefficient, b) input reflection coefficient, c)  $V_0^+$ , d) the general phasor voltage & current equations.



$$a) (2.35) \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(100 - j50) - (50.1426 + j0.0381)}{(100 - j50) + (50.1426 + j0.0381)}$$

$$\Gamma = \Gamma_L = 0.4464 \angle -26.6981^\circ$$

$$b) (2.90) \quad \Gamma_{in} = \Gamma(l) = \Gamma_L e^{-2\gamma l} = (0.4464 \angle -26.7^\circ) e^{-2(0.1427 + j82.7)2}$$

$$\Gamma_{in} = 0.2523 \angle 99.3733^\circ$$

$$c) \quad Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = (50.1426 \angle 0.044^\circ) \left( \frac{1 + 0.2523 \angle 99.37^\circ}{1 - 0.2523 \angle 99.37^\circ} \right)$$

$$= 40.96 + j21.8158 \Omega$$

$$\text{By voltage division} \quad V_{in} = V_g \frac{Z_{in}}{Z_g + Z_{in}} = (20 \angle 0^\circ) \frac{40.96 + j21.816}{(50 - j10) + (40.96 + j21.816)}$$

$$V_{in} = 10.1189 \angle 20.639^\circ \text{ V}$$

$$V_0^+ = \frac{V_{in}}{e^{\gamma l} + \Gamma_L e^{-\gamma l}} = \frac{10.1189 \angle 20.639^\circ}{e^{(0.1427 + j82.7)2} + 0.4464 \angle -26.7^\circ e^{-(0.1427 + j82.7)2}}$$

$$V_0^+ = 7.6783 \angle -110.876^\circ \text{ V}$$

$$d) (2.89a) \quad V(z) = V_0^+ [e^{-\gamma z} + \Gamma e^{\gamma z}]$$

$$V(z) = (7.678 \angle -110.88^\circ \text{ V}) \left[ e^{-(0.143 + j82.7)z} + (0.4464 \angle -26.7^\circ) e^{(0.143 + j82.7)z} \right]$$


---

$$(2.89b) \quad I(z) = \frac{V_0^+}{Z_0} [e^{-\gamma z} - \Gamma e^{\gamma z}] = \frac{7.678 \angle -110.88^\circ}{50.1426 \angle 0.044^\circ} [e^{-\gamma z} - \Gamma e^{\gamma z}]$$

$$I(z) = (0.1531 \angle -110.92^\circ) \left[ e^{-(0.143 + j82.7)z} - (0.4464 \angle -26.7^\circ) e^{(0.143 + j82.7)z} \right] \text{ A}$$


---

Both valid for  $-2\text{ m} \leq z \leq 0$