


Use a 1 m length of the coaxial transmission line from 1) to create a TL circuit with $V_g = 16\angle 0^\circ$ V, $Z_g = 45 - j10 \Omega$, and $Z_L = 100 - j50 \Omega$ operating at 3.6 GHz. Find: a) the load reflection coefficient, b) input reflection coefficient, c) V_0^+ , d) the general phasor voltage & current equations.

A coaxial transmission line, operating at 3.6 GHz, has the distributed parameters $R = 3.8 \Omega/\text{m}$, $L = 248 \text{ nH}/\text{m}$, $G = 6.4 \text{ mS}/\text{m}$, and $C = 112 \text{ pF}/\text{m}$. Calculate the a) propagation constant, b) attenuation constant (both Np/m and dB/m), c) phase constant, d) characteristic impedance (both polar & rectangular forms), e) wavelength, and f) phase velocity (m/s and fraction of c).

From earlier problem-

$$\gamma = 0.19096 + j119.2113 \text{ 1/m}, Z_0 = 47.0561 + j0.435 \Omega = 47.0561\angle 0.05297^\circ \Omega,$$
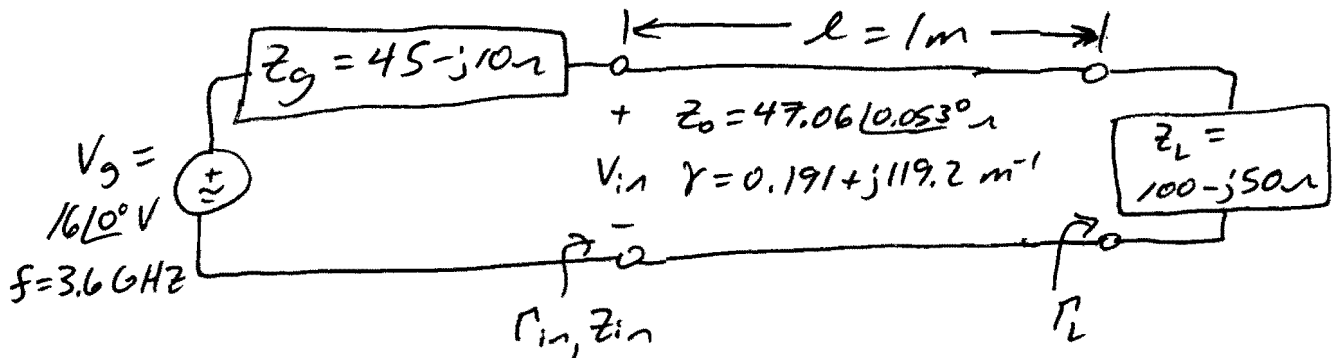
$$\lambda = 0.052706 \text{ m} = 5.2706 \text{ cm}, \text{ and } v_p = 1.89743 \times 10^8 \text{ m/s} = 0.6329c$$



$$a) (2.35) \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(100 - j50) - (47.056 + j0.435)}{(100 - j50) + (47.056 + j0.435)}$$

$$\Gamma = \Gamma_L = 0.469\angle -24.6237^\circ$$


$$b) (2.90) \Gamma_{in} = \Gamma(l) = \Gamma e^{-2\gamma l} = 0.469\angle -24.6^\circ e^{-2(0.191 + j119.2)1}$$

$$\Gamma_{in} = 0.3202\angle -5.2318^\circ$$

$$c) (notes) Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = (47.056 + j0.435) \frac{1 + 0.3202\angle -5.23^\circ}{1 - 0.3202\angle -5.23^\circ}$$

$$Z_{in} = 90.86 - j5.83 \Omega$$

c) cont. Equiv. circuit

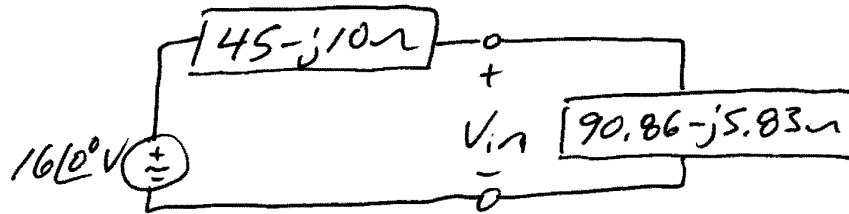

$$V_{in} = 16\angle 0^\circ \frac{90.86 - j5.83}{(45 - j10) + (90.86 - j5.83)} = 10.6504\angle 2.9753^\circ \text{ V}$$

Per (2.89a) $V(z) = V_0^+ (e^{-\gamma z} + \Gamma e^{\gamma z})$. At the input $z = -lm$ $V(z = -lm) = V_{in}$, we find

$$V_0^+ = \frac{V_{in}}{e^{\gamma(l)} + \Gamma_L e^{\gamma(-l)}} = \frac{10.6504\angle 2.9753^\circ}{e^{0.191 + j119.2} + (0.469\angle -24.6^\circ) e^{-0.191 - j119.2}}$$

$$\underline{\underline{V_0^+ = 6.6702\angle 13.9394^\circ \text{ V}}}$$

d) Per (2.89a),

$$V(z) = (6.67\angle 13.94^\circ) \left[e^{-(0.191 + j119.2)z} + (0.469\angle -24.6^\circ) e^{(0.191 + j119.2)z} \right] \text{ V}$$

$-lm \leq z \leq 0$

Per (2.89b), $I(z) = \frac{V_0^+}{Z_0} (e^{-\gamma z} - \Gamma e^{\gamma z})$

$$I(z) = \frac{6.67\angle 13.94^\circ}{47.06\angle 0.053^\circ} \left(e^{-(0.191 + j119.2)z} - (0.469\angle -24.6^\circ) e^{(0.191 + j119.2)z} \right)$$

$$I(z) = (0.14175\angle 13.886^\circ) \left[e^{-(0.191 + j119.2)z} - (0.469\angle -24.6^\circ) e^{(0.191 + j119.2)z} \right] \text{ A}$$

$-lm \leq z \leq 0$