

- 4.4 A two-port network is driven at both ports such that the port voltages and currents have the following values ($Z_0 = 50 \Omega$):

$$\begin{aligned} V_1 &= 10\angle 90^\circ, & I_1 &= 0.2\angle 90^\circ, \\ V_2 &= 8\angle 0^\circ, & I_2 &= 0.16\angle -90^\circ. \end{aligned}$$

Determine the input impedance seen at each port, and find the incident and reflected voltages at each port.

Port 1 $Z_{in,1} = \frac{V_1}{I_1} = \frac{10\angle 90^\circ}{0.2\angle 90^\circ} \Rightarrow \underline{\underline{Z_{in,1} = 50\Omega}}$

Port 2 $Z_{in,2} = \frac{V_2}{I_2} = \frac{8\angle 0^\circ}{0.16\angle -90^\circ} \Rightarrow \underline{\underline{Z_{in,2} = 50\angle 90^\circ = j50\Omega}}$

Per (2.14a) & (2.14b),
$$\begin{aligned} V(0) &= V_0^+ + V_0^- \\ I(0) &= \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0} \end{aligned} \quad \left. \vphantom{\begin{aligned} V(0) &= V_0^+ + V_0^- \\ I(0) &= \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0} \end{aligned}} \right\} \begin{array}{l} \text{solve} \\ \downarrow \end{array}$$

$$\begin{aligned} V_0^+ &= \frac{1}{2} [V_0 + Z_0 I_0] \\ V_0^- &= \frac{1}{2} [V_0 - Z_0 I_0] \end{aligned} \quad \text{where } Z_0 = 50\Omega$$

Port 1
$$\begin{aligned} V_1^+ &= \frac{1}{2} [10\angle 90^\circ + 50(0.2\angle 90^\circ)] \Rightarrow \underline{\underline{V_1^+ = 10\angle 90^\circ V}} \\ V_1^- &= \frac{1}{2} [10\angle 90^\circ - 50(0.2\angle 90^\circ)] \Rightarrow \underline{\underline{V_1^- = 0}} \end{aligned}$$

Port 2
$$\begin{aligned} V_2^+ &= \frac{1}{2} [8\angle 0^\circ + 50(0.16\angle -90^\circ)] \Rightarrow \underline{\underline{V_2^+ = 5.657\angle -45^\circ V}} \\ V_2^- &= \frac{1}{2} [8\angle 0^\circ - 50(0.16\angle -90^\circ)] \Rightarrow \underline{\underline{V_2^- = 5.657\angle 45^\circ V}} \end{aligned}$$