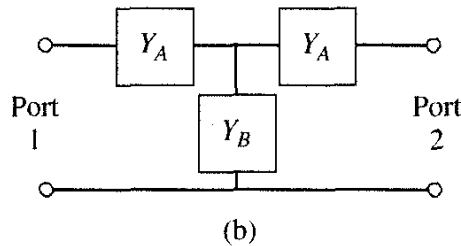



4.7 Derive the $[Z]$ and $[Y]$ matrices for the two-port networks shown in the figure below.



Note that the Tee-network is symmetric.

Per (4.28), $z_{ij} = \frac{V_i}{I_j} \big|_{I_k=0 \text{ for } k \neq j}$

$[z_{11}]$ Here $z_{11} = \frac{V_1}{I_1} \big|_{I_2=0}$ and the circuit is

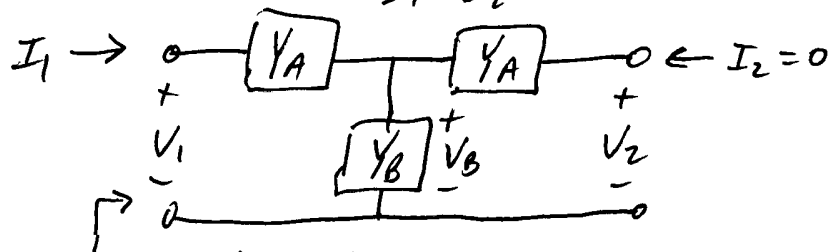

Find I_1 in terms of V_1 .

$$z_{eq} = \frac{1}{Y_A} + \frac{1}{Y_B}$$

$$I_1 = V_1 / z_{eq} = V_1 / \left(\frac{1}{Y_A} + \frac{1}{Y_B} \right)$$

$$z_{11} = \frac{V_1}{I_1} = \frac{V_1}{V_1 / \left(\frac{1}{Y_A} + \frac{1}{Y_B} \right)} = \frac{1}{Y_A} + \frac{1}{Y_B} \Rightarrow z_{11} = \frac{Y_A + Y_B}{Y_A Y_B} = z_{22}$$

$[z_{21}]$ Here $z_{21} = \frac{V_2}{I_1} \big|_{I_2=0}$ w/ same circuit.


By Ohm's Law, $V_B = I_1 / Y_B$. By KVL, $-V_B + 0 + V_2 = 0$
 $\Rightarrow V_2 = V_B$

$$V_B = V_2 = I_1 / Y_B \Rightarrow z_{21} = \frac{I_1 / Y_B}{I_1} \Rightarrow z_{21} = \frac{1}{Y_B} = z_{12}$$

$$[Z] = \begin{bmatrix} \frac{Y_A + Y_B}{Y_A Y_B} & \frac{1}{Y_B} \\ \frac{1}{Y_B} & \frac{Y_A + Y_B}{Y_A Y_B} \end{bmatrix}$$

Per (4.29), $Y_{ij} = \frac{I_j}{V_i} \big|_{V_k=0, k \neq j}$.

$[Y_{11}]$ Here $Y_{11} = \frac{I_1}{V_1} \big|_{V_2=0}$ and the circuit is

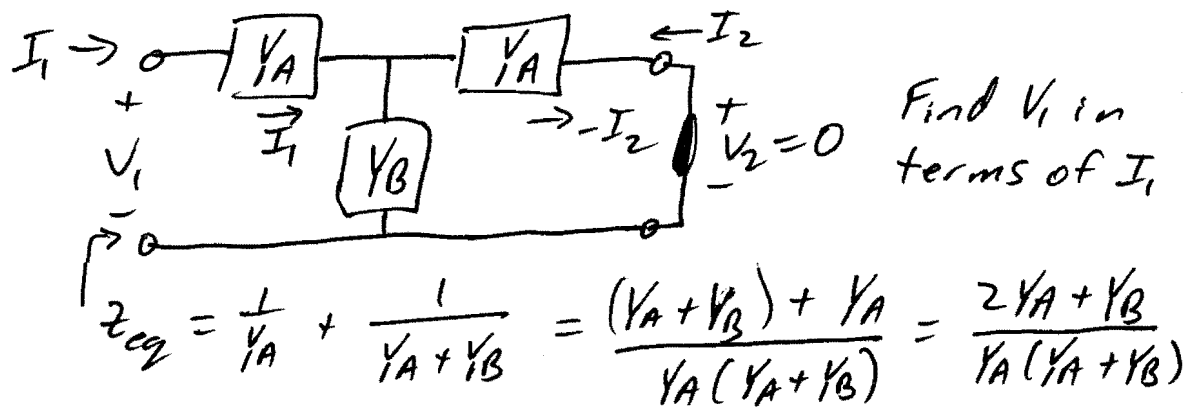

$$Z_{eq} = \frac{1}{Y_A} + \frac{1}{Y_A + Y_B} = \frac{(Y_A + Y_B) + Y_A}{Y_A(Y_A + Y_B)} = \frac{2Y_A + Y_B}{Y_A(Y_A + Y_B)}$$

$$V_1 = I_1 Z_{eq} = I_1 \frac{2Y_A + Y_B}{Y_A(Y_A + Y_B)}$$

$$Y_{11} = \frac{I_1}{I_1 \frac{2Y_A + Y_B}{Y_A(Y_A + Y_B)}} \Rightarrow Y_{11} = \frac{Y_A(Y_A + Y_B)}{2Y_A + Y_B} = Y_{22}$$

$[Y_{21}]$ Here $Y_{21} = \frac{I_2}{V_1} \big|_{V_2=0}$ w/ same circuit.

By current division, $-I_2 = I_1 \frac{Y_A}{Y_A + Y_B}$. So,

$$I_2 = -I_1 \frac{Y_A}{Y_A + Y_B} = \frac{-V_1}{Z_{eq}} \left(\frac{Y_A}{Y_A + Y_B} \right) = -V_1 \frac{Y_A(Y_A + Y_B)}{2Y_A + Y_B} \left(\frac{Y_A}{Y_A + Y_B} \right)$$

$$Y_{21} = \frac{-V_1 Y_A^2 / (2Y_A + Y_B)}{V_1} \Rightarrow Y_{21} = \frac{-Y_A^2}{2Y_A + Y_B} = Y_{12}$$

$$[Y] = \begin{bmatrix} \frac{Y_A(Y_A + Y_B)}{2Y_A + Y_B} & \frac{-Y_A^2}{2Y_A + Y_B} \\ \frac{-Y_A^2}{2Y_A + Y_B} & \frac{Y_A(Y_A + Y_B)}{2Y_A + Y_B} \end{bmatrix}$$