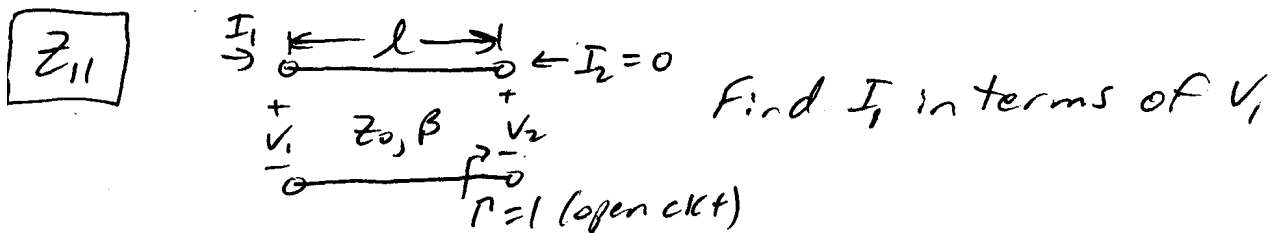


- 4.9 Find the impedance parameters of a section of transmission line with length ℓ , characteristic impedance Z_0 , and propagation constant β .

Per (4.28), $z_{ij} = \frac{V_i}{I_j} \Big|_{I_k=0 \text{ for } k \neq j}$



From (2.36a) & (2.36b),

$$V(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$

$$I(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z})$$

$$V_1 = V(-\ell) = V_0^+ (e^{+j\beta\ell} + (1)e^{-j\beta\ell}) = 2V_0^+ \cos \beta\ell$$

$$I_1 = I(-\ell) = \frac{V_0^+}{Z_0} (e^{+j\beta\ell} - (1)e^{-j\beta\ell}) = j \frac{2V_0^+}{Z_0} \sin \beta\ell$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{2V_0^+ \cos(\beta\ell)}{j \frac{2V_0^+}{Z_0} \sin(\beta\ell)} = \frac{-jZ_0 \cot(\beta\ell)}{1} = Z_{22} \quad (\text{symmetry})$$

$\boxed{Z_{21}}$ Same circuit.

$$V_2 = V(0) = V_0^+ (e^0 + 1e^0) = 2V_0^+$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{2V_0^+}{j \frac{2V_0^+}{Z_0} \sin(\beta\ell)} = \frac{-jZ_0}{\sin(\beta\ell)} = \frac{-jZ_0 \csc(\beta\ell)}{1} = Z_{12} \quad (\text{symmetry})$$

$$\boxed{[Z] = \begin{bmatrix} -jZ_0 \cot(\beta\ell) & -jZ_0 \csc(\beta\ell) \\ -jZ_0 \csc(\beta\ell) & -jZ_0 \cot(\beta\ell) \end{bmatrix}}$$