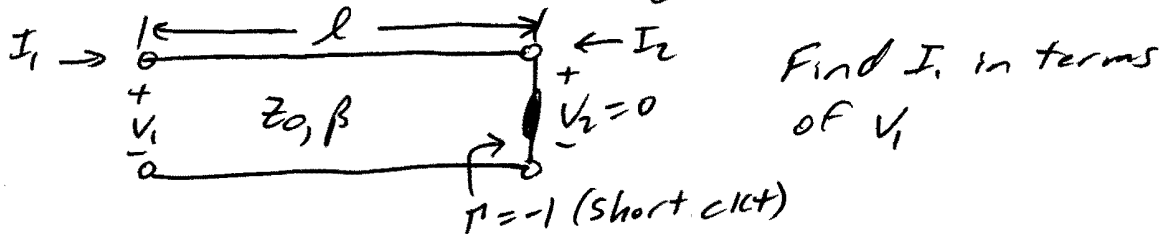


4.9 Find the **admittance** parameters of a section of transmission line with length ℓ , characteristic impedance Z_0 , and propagation constant β .

Per (4.29), $Y_{ij} = \frac{I_j}{V_i} \big|_{V_k=0 \text{ for } k \neq j}$

Y_{11} Here, $Y_{11} = \frac{I_1}{V_1} \big|_{V_2=0}$



From (2.36a) + (2.36b), $V(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$

$I(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z})$ Euler's

So, $V_1 = V(-\ell) = V_0^+ (e^{j\beta \ell} + (-1) e^{-j\beta \ell}) = V_0^+ (2j \sin \beta \ell)$

$I_1 = I(-\ell) = \frac{V_0^+}{Z_0} (e^{j\beta \ell} - (-1) e^{-j\beta \ell}) = \frac{V_0^+}{Z_0} (2 \cos \beta \ell)$

$Y_{11} = \frac{\frac{V_0^+}{Z_0} (2 \cos \beta \ell)}{V_0^+ (2j \sin \beta \ell)} = \frac{1}{j Z_0 \tan(\beta \ell)} = Y_{22} \text{ (Symmetry)}$
or $-\frac{j \cot(\beta \ell)}{Z_0}$

Y_{21} Here, $Y_{21} = \frac{I_2}{V_1} \big|_{V_2=0}$

So, $V_1 = V(-\ell) = V_0^+ (2j \sin \beta \ell)$

$I_2 = -I(0) = -\frac{V_0^+}{Z_0} (1 + 1) = -\frac{2V_0^+}{Z_0}$

$Y_{21} = \frac{I_2}{V_1} = \frac{-2V_0^+/Z_0}{V_0^+ (2j \sin \beta \ell)} = \frac{-1}{j Z_0 \sin \beta \ell} = Y_{12} \text{ (Symmetry)}$
or $+\frac{j \csc \beta \ell}{Z_0}$

$$[Y] = \begin{bmatrix} \frac{1}{j Z_0 \tan(\beta \ell)} & \frac{-1}{j Z_0 \sin(\beta \ell)} \\ \frac{-1}{j Z_0 \sin(\beta \ell)} & \frac{1}{j Z_0 \tan(\beta \ell)} \end{bmatrix}$$