
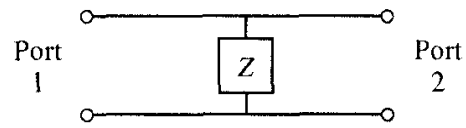


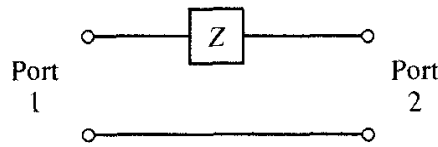
- 4.11 Find the scattering parameters for the series and shunt loads shown below. Show that  $S_{12} = 1 - S_{11}$  for the series case, and that  $S_{12} = 1 + S_{11}$  for the shunt case. Assume a characteristic impedance  $Z_0$ .



Per (4.41),  $S_{ij} = \frac{V_i^-}{V_j^+} \Big|_{V_k^+ = 0 \text{ for } k \neq j}$

**Series**

**$S_{11}$**

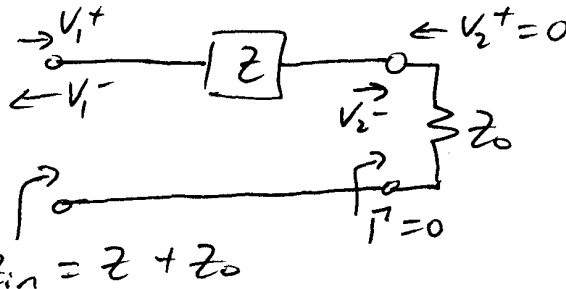

$$S_{11} = \Gamma_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{(Z + Z_0) - Z_0}{(Z + Z_0) + Z_0} = \frac{Z}{2Z_0 + Z} = S_{22} \text{ (Symmetry)}$$

**$S_{21}$**  Same circuit. Find  $V_2^-$  (voltage across  $Z_0$ ) in terms of  $V_1^+$

$$V_2 = V_2^- = V_1 \left( \frac{Z_0}{Z + Z_0} \right) = (V_1^+ + V_1^-) \frac{Z_0}{Z + Z_0} = V_1^+ \left( 1 + \Gamma_{11} \right) \frac{Z_0}{Z + Z_0}$$

$$S_{21} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0} = \frac{V_1^+ \left( 1 + \frac{Z}{2Z_0 + Z} \right) \frac{Z_0}{Z + Z_0}}{V_1^+} = \left( 1 + \frac{Z}{2Z_0 + Z} \right) \frac{Z_0}{Z + Z_0}$$

$$= \frac{Z_0}{Z + Z_0} + \frac{Z Z_0}{(2Z_0 + Z)(Z + Z_0)} = \frac{Z_0(2Z_0 + Z) + Z Z_0}{(2Z_0 + Z)(Z + Z_0)}$$

$$= \frac{2Z_0(Z + Z_0)}{(2Z_0 + Z)(Z + Z_0)} = \frac{2Z_0}{2Z_0 + Z} = S_{12} \text{ (Symmetry)}$$

Series  $[S] = \begin{bmatrix} \frac{Z}{2Z_0 + Z} & \frac{2Z_0}{2Z_0 + Z} \\ \frac{2Z_0}{2Z_0 + Z} & \frac{Z}{2Z_0 + Z} \end{bmatrix}$


$$S_{12} \stackrel{?}{=} 1 - S_{11}$$

$$\frac{2z_0}{2z_0 + z} \stackrel{?}{=} 1 - \frac{z}{2z_0 + z} = \frac{(2z_0 + z) - z}{2z_0 + z} = \frac{2z_0}{2z_0 + z}$$

$$\frac{2z_0}{2z_0 + z} = \frac{2z_0}{2z_0 + z} \quad \therefore \text{Yes!}$$

**Shunt**

**$S_{11}$**

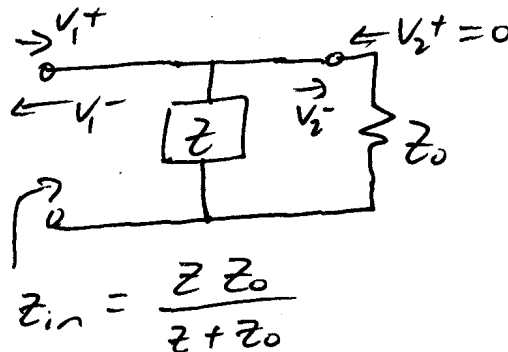

$$\begin{aligned} S_{11} = \Gamma_{11} &= \frac{z_{in} - z_0}{z_{in} + z_0} = \frac{\frac{z z_0}{z + z_0} - z_0}{\frac{z z_0}{z + z_0} + z_0} \left( \frac{z + z_0}{z + z_0} \right) = \frac{z z_0 - z_0(z + z_0)}{z z_0 + z_0(z + z_0)} \\ &= \frac{-z_0^2}{2z z_0 + z_0^2} = \frac{-z_0}{2z + z_0} = S_{22} \text{ (symmetry)} \end{aligned}$$

**$S_{21}$**  Same Circuit. Find  $V_2^-$  (voltage across  $z_0$ ) in terms of  $V_1^+$

$$\begin{aligned} V_2 = V_2^- = V_1 = V_1^+ + V_1^- &= V_1^+ (1 + \Gamma_{11}) \\ &= V_1^+ \left( 1 + \frac{-z_0}{2z + z_0} \right) \end{aligned}$$

$$\begin{aligned} S_{21} &= \frac{V_2^-}{V_1^+} \bigg|_{V_2^+ = 0} = \frac{V_1^+ \left( 1 + \frac{-z_0}{2z + z_0} \right)}{V_1^+} = \frac{(2z + z_0) - z_0}{2z + z_0} \\ &= \frac{2z}{2z + z_0} = S_{12} \text{ (symmetry)} \end{aligned}$$

shunt

$$[S] = \begin{bmatrix} \frac{-z_0}{2z+z_0} & \frac{2z}{2z+z_0} \\ \frac{2z}{2z+z_0} & \frac{-z_0}{2z+z_0} \end{bmatrix}$$

$$S_{12} \stackrel{?}{=} 1 + S_{11}$$

$$\frac{2z}{2z+z_0} \stackrel{?}{=} 1 + \frac{-z_0}{2z+z_0} = \frac{(2z+z_0) - z_0}{2z+z_0}$$

$$\frac{2z}{2z+z_0} = \frac{2z}{2z+z_0} \quad \therefore \text{Yes!}$$