

- 4.14** A four-port network has the scattering matrix shown as follows. (a) Is this network lossless? (b) Is this network reciprocal? (c) What is the return loss at port 1 when all other ports are terminated with matched loads? (d) What is the insertion loss and phase delay between ports 2 and 4 when all other ports are terminated with matched loads? (e) What is the reflection coefficient seen at port 1 if a short circuit is placed at the terminal plane of port 3 and all other ports are terminated with matched loads?

$$[S] = \begin{bmatrix} 0.24\angle 90^\circ & 0.5\angle 45^\circ & 0.6\angle 45^\circ & 0 \\ 0.5\angle 45^\circ & 0 & 0 & 0.2\angle -45^\circ \\ 0.6\angle 45^\circ & 0 & 0 & 0.6\angle -45^\circ \\ 0 & 0.2\angle -45^\circ & 0.6\angle -45^\circ & 0 \end{bmatrix}$$

- a) Per (4.51), $[S]^t [S]^* = [U]$ for a lossless network.

$$\begin{bmatrix} 0.24\angle 90^\circ & 0.5\angle 45^\circ & 0.6\angle 45^\circ & 0 \\ 0.5\angle 45^\circ & 0 & 0 & 0.2\angle -45^\circ \\ 0.6\angle 45^\circ & 0 & 0 & 0.6\angle -45^\circ \\ 0 & 0.2\angle -45^\circ & 0.6\angle -45^\circ & 0 \end{bmatrix} \begin{bmatrix} 0.24\angle -90^\circ & 0.5\angle -45^\circ & 0.6\angle -45^\circ & 0 \\ 0.5\angle -45^\circ & 0 & 0 & 0.2\angle 45^\circ \\ 0.6\angle -45^\circ & 0 & 0 & 0.6\angle 45^\circ \\ 0 & 0.2\angle 45^\circ & 0.6\angle 45^\circ & 0 \end{bmatrix} = [U]?$$

Check to see if first element of matrix multiplication is equal to 1-

$$(0.24\angle 90^\circ)(0.24\angle -90^\circ) + (0.5\angle 45^\circ)(0.5\angle -45^\circ) + (0.6\angle 45^\circ)(0.6\angle -45^\circ) + 0(0) = 1 ?$$

$$0.24^2 + 0.5^2 + 0.6^2 = 0.6676 \neq 1 \Rightarrow \boxed{[S] \text{ is NOT a lossless network}}.$$

- b) To be reciprocal, $[S] = [S]^t$ (4.48).

$$\begin{bmatrix} 0.24\angle 90^\circ & 0.5\angle 45^\circ & 0.6\angle 45^\circ & 0 \\ 0.5\angle 45^\circ & 0 & 0 & 0.2\angle -45^\circ \\ 0.6\angle 45^\circ & 0 & 0 & 0.6\angle -45^\circ \\ 0 & 0.2\angle -45^\circ & 0.6\angle -45^\circ & 0 \end{bmatrix} = \begin{bmatrix} 0.24\angle 90^\circ & 0.5\angle 45^\circ & 0.6\angle 45^\circ & 0 \\ 0.5\angle 45^\circ & 0 & 0 & 0.2\angle -45^\circ \\ 0.6\angle 45^\circ & 0 & 0 & 0.6\angle -45^\circ \\ 0 & 0.2\angle -45^\circ & 0.6\angle -45^\circ & 0 \end{bmatrix}?$$

$$\Rightarrow \boxed{[S] \text{ is a reciprocal network}}.$$

- c) Per (2.38), $RL = -20 \log |\Gamma|$ (dB). When ports 2-4 are matched, $S_{11} = \Gamma_1 = 0.24\angle 90^\circ$ (page 179).

$$RL_1 = -20 \log |S_{11}| = -20 \log 0.24 \Rightarrow \boxed{RL_1 = 12.396 \text{ dB}}.$$

- d) Per (4.40), $[V^-] = [S][V^+]$. The statement that ports 1 & 3 are terminated in matched loads $\Rightarrow V_1^+ = V_3^+ = 0$.

d) cont.

$$\begin{bmatrix} V_1^- \\ V_2^- \\ V_3^- \\ V_4^- \end{bmatrix} = \begin{bmatrix} 0.24\angle 90^\circ & 0.5\angle 45^\circ & 0.6\angle 45^\circ & 0 \\ 0.5\angle 45^\circ & 0 & 0 & 0.2\angle -45^\circ \\ 0.6\angle 45^\circ & 0 & 0 & 0.6\angle -45^\circ \\ 0 & 0.2\angle -45^\circ & 0.6\angle -45^\circ & 0 \end{bmatrix} \begin{bmatrix} V_1^+ = 0 \\ V_2^+ \\ V_3^+ = 0 \\ V_4^+ \end{bmatrix}$$

Compute $V_2^- = 0.5\angle 45^\circ(0) + 0(V_2^+) + 0(0) + 0.2\angle -45^\circ(V_4^+) = 0.2\angle -45^\circ(V_4^+)$.

The transmission coefficient from port 4 to port 2 is $T_{24} = \frac{V_2^-}{V_4^+} = 0.2\angle -45^\circ$.

Use (2.52) $IL = -20 \log |T|$ (dB) to get $IL_{24} = -20 \log 0.2 \Rightarrow \boxed{IL_{24} = 13.979 \text{ dB}}$.

Put the equation for V_2^- in polar/phasor format

$$|V_2^-| \angle \theta_2^- = (0.2\angle -45^\circ) (|V_4^+| \angle \theta_4^+) = 0.2 |V_4^+| \angle (-45^\circ + \theta_4^+).$$

Equating the phase angles gives $\theta_2^- = -45^\circ + \theta_4^+ \Rightarrow \boxed{\text{Phase delay}_{24} = -45^\circ}$.

e) The statement that ports 2 & 4 are terminated in matched loads $\Rightarrow V_2^+ = V_4^+ = 0$.

The statement that port 3 is short-circuited implies $\Gamma_3 = \frac{V_3^-}{V_3^+} = -1 \Rightarrow V_3^+ = -V_3^-$.

Now, (4.40) $[V^-] = [S][V^+]$ becomes

$$\begin{bmatrix} V_1^- \\ V_2^- \\ V_3^- \\ V_4^- \end{bmatrix} = \begin{bmatrix} 0.24\angle 90^\circ & 0.5\angle 45^\circ & 0.6\angle 45^\circ & 0 \\ 0.5\angle 45^\circ & 0 & 0 & 0.2\angle -45^\circ \\ 0.6\angle 45^\circ & 0 & 0 & 0.6\angle -45^\circ \\ 0 & 0.2\angle -45^\circ & 0.6\angle -45^\circ & 0 \end{bmatrix} \begin{bmatrix} V_1^+ \\ 0 \\ -V_3^- \\ 0 \end{bmatrix}$$

Compute $V_1^- = (0.24\angle 90^\circ)V_1^+ + (0.5\angle 45^\circ)(0) + (0.6\angle 45^\circ)(-V_3^-) + 0(0)$. This simplifies to equation (1) $V_1^- = (0.24\angle 90^\circ)V_1^+ - (0.6\angle 45^\circ)V_3^-$.

Compute $V_3^- = (0.6\angle 45^\circ)V_1^+ + 0(0) + 0(-V_3^-) + (0.6\angle 45^\circ)0$.

Next, substitute $V_3^- = (0.6\angle 45^\circ)V_1^+$ into equation (1) to get

$$\begin{aligned} V_1^- &= (0.24\angle 90^\circ)V_1^+ - (0.6\angle 45^\circ)[(0.6\angle 45^\circ)V_1^+] = [(0.24\angle 90^\circ) - (0.6\angle 45^\circ)(0.6\angle 45^\circ)]V_1^+ \\ V_1^- &= (0.12\angle -90^\circ)V_1^+ \end{aligned}$$

By definition, $\Gamma_1 = \frac{V_1^-}{V_1^+} = \frac{(0.12\angle -90^\circ)V_1^+}{V_1^+}$. Solving, we get $\Rightarrow \boxed{\Gamma_1 = 0.12\angle -90^\circ}$.