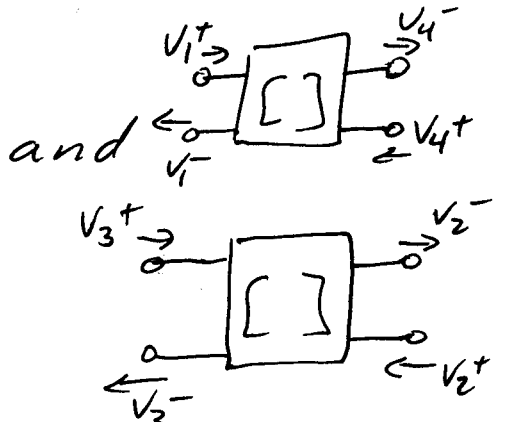


- 4.18** A four-port network has the scattering matrix shown as follows. If ports 3 and 4 are connected with a lossless matched transmission line with an electrical length of 45° , find the resulting insertion loss and phase delay between ports 1 and 2.

$$[S] = \begin{bmatrix} 0.2\angle 50^\circ & 0 & 0 & 0.4\angle -45^\circ \\ 0 & 0.6\angle 45^\circ & 0.7\angle -45^\circ & 0 \\ 0 & 0.7\angle -45^\circ & 0.6\angle 45^\circ & 0 \\ 0.4\angle -45^\circ & 0 & 0 & 0.5\angle 45^\circ \end{bmatrix}$$

From the 'interesting' arrangement of the $[S]$ -matrix, we can create two separate 2×2 systems.


$$\begin{bmatrix} V_1^- \\ V_4^- \end{bmatrix} = \begin{bmatrix} 0.2\angle 50^\circ & 0.4\angle -45^\circ \\ 0.4\angle -45^\circ & 0.5\angle 45^\circ \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_4^+ \end{bmatrix} \quad \text{and} \quad \begin{bmatrix} V_2^- \\ V_3^- \end{bmatrix} = \begin{bmatrix} 0.6\angle 45^\circ & 0.7\angle -45^\circ \\ 0.7\angle -45^\circ & 0.6\angle 45^\circ \end{bmatrix} \begin{bmatrix} V_2^+ \\ V_3^+ \end{bmatrix}$$


Given that ports 3 & 4 are connected w/ a lossless matched TL w/ electrical length $45^\circ = \beta l$


$$V_4^+ = V_3^- (1\angle -45^\circ) = V_2^- e^{-j45^\circ} = V_3^-(T)$$

$$V_3^+ = V_4^- e^{-j45^\circ} = V_4^- (1\angle -45^\circ) = V_4^-(T)$$

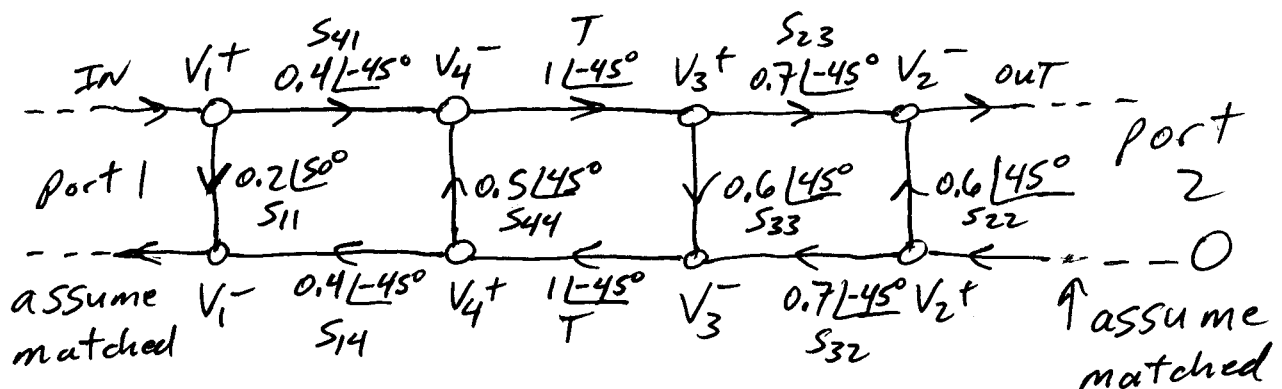
Using the above and Fig 4.14, the SFG below can be created.



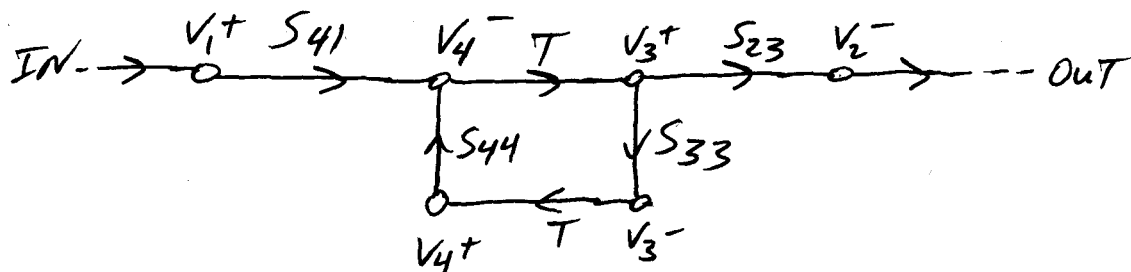
Step 1 Given that ports 1 & 2 are matched, we can eliminate nodes V_1^- (deadend, no impact on forward path) and V_2^+ (nothing coming in port 2)



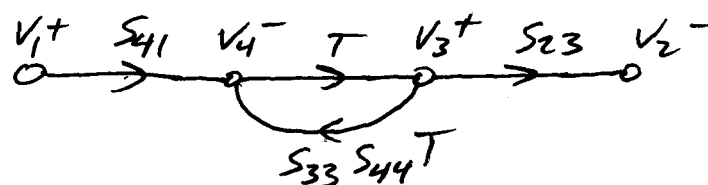
Step 2 Eliminate nodes V_4^+ and V_3^- using series rule.




Step 3 Split node V_3^+

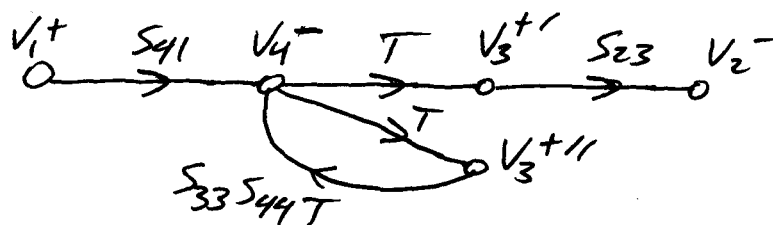

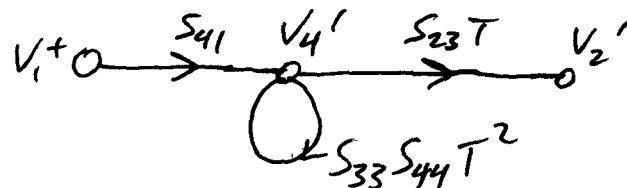Step 4 Apply series rule to eliminate $V_3^{+'}$ & $V_3^{+'}$.



Step 5 Apply self-loop rule

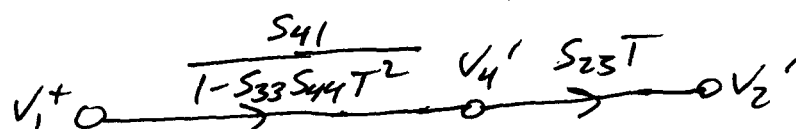

Step 6 Apply series rule to get

$$V_2 = \frac{S_{23} S_{41} T}{1 - S_{33} S_{44} T^2} V_1^+$$

$$T_{21} = \frac{V_2^-}{V_1^+} = \frac{S_{23} S_{41} T}{1 - S_{33} S_{44} T^2}$$

$$= \frac{(0.7 \angle -45^\circ)(0.4 \angle -45^\circ)(1 \angle -45^\circ)}{1 - (0.6 \angle 45^\circ)(0.5 \angle 45^\circ)(1 \angle -45^\circ)^2} = \frac{0.28 \angle -135^\circ}{1 - 0.3}$$

$$\underline{T_{21} = 0.4 \angle -135^\circ}$$

$$\underline{\underline{\text{Phase delay}_{1 \leftrightarrow 2} = 135^\circ}}$$

$$\text{Per (2.52), } IL = -20 \log |T|$$

$$IL_{21} = -20 \log (0.4)$$

$$\underline{\underline{IL_{21} = 7.9588 \text{ dB}}}$$