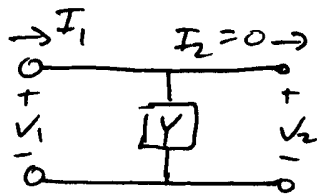



4.21 The $ABCD$ parameters of the first entry in Table 4.1 were derived in Example 4.6. Verify the $ABCD$ parameters for the second, third, and fourth entries.



Use equations per text pp 190-191

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1 \quad (\text{directly in parallel})$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{V_2 Y}{V_2} = Y \quad (\text{Ohm's Law})$$

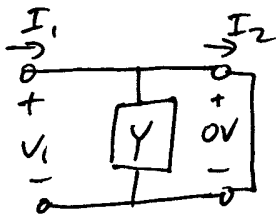

By current division, $I_2 = I_1$


By inspection, $V_1 = V_2 = 0$

$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = \frac{0}{I_2} = 0$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{I_2}{I_2} = 1$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_Y = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

Same as Table 4.1

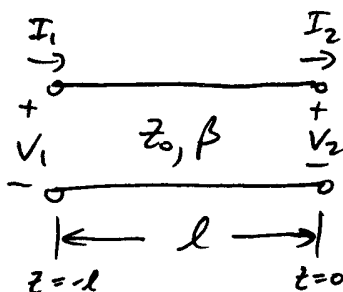

$\Rightarrow$ Open circuit stub situation ($\Gamma = 1$)

$$\text{Per (2.36a), } V(z) = V_0^+ [e^{-j\beta z} + \Gamma e^{j\beta z}]$$

$$V_2 = V(0) = V_0^+ [1 + \Gamma(1)] = 2V_0^+$$

$$V_1 = V(-l) = V_0^+ [e^{j\beta l} + (1) e^{-j\beta l}] = V_0^+ 2 \cos \beta l$$

Trig ID


$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{V_0^+ 2 \cos \beta l}{2 V_0^+} = \cos \beta l$$

$$\text{Per (2.36b), } I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma e^{j\beta z}]$$

$$I_1 = I(-l) = \frac{V_0^+}{Z_0} [e^{j\beta l} - (1) e^{-j\beta l}] = \frac{V_0^+}{Z_0} j 2 \sin \beta l$$

Trig ID

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{\frac{V_0^+}{Z_0} j 2 \sin \beta l}{2 V_0^+} = \frac{j \sin \beta l}{Z_0} = j Y_0 \sin \beta l$$

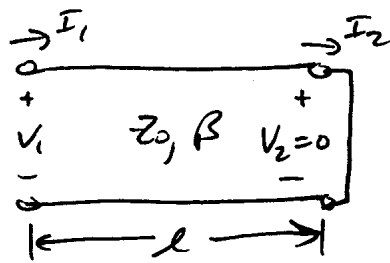

⇒ Short circuit stub situation ($\Gamma = -1$)

$$V_1 = V(-l) = V_0^+ [e^{j\beta l} + (-1)e^{-j\beta l}] = V_0^+ j2\sin\beta l$$


$$I_2 = I(0) = \frac{V_0^+}{Z_0} [1 - (-1)] = \frac{2V_0^+}{Z_0}$$

$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = \frac{V_0^+ j2\sin\beta l}{2V_0^+/Z_0} = jZ_0 \sin\beta l$$

$$I_1 = I(-l) = \frac{V_0^+}{Z_0} [e^{j\beta l} - (-1)e^{-j\beta l}] = \frac{V_0^+}{Z_0} 2\cos\beta l$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{\frac{V_0^+}{Z_0} 2\cos\beta l}{2V_0^+/Z_0} = \cos\beta l$$
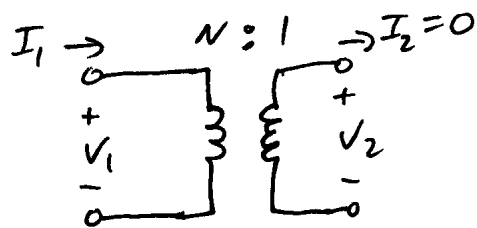
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{TL} = \begin{bmatrix} \cos\beta l & jZ_0 \sin\beta l \\ jY_0 \sin\beta l & \cos\beta l \end{bmatrix} \therefore \text{Same as Table 4.1}$$




From circuits text:

$$V_1 = N V_2$$

$$I_1 = I_2 / N = 0$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{N V_2}{V_2} = N$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{0}{V_2} = 0$$

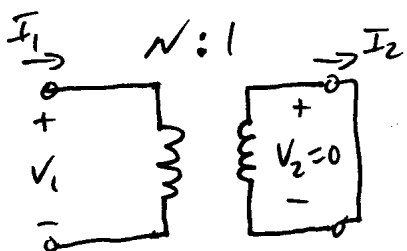

From circuits text:

$$V_1 = N V_2 = N(0) = 0$$

$$I_1 = I_2 / N$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} = \frac{0}{I_2} = \underline{0}$$

$$D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{I_2/N}{I_2} = \underline{\frac{1}{N}}$$

$$\boxed{\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{xfmr}} = \begin{bmatrix} N & 0 \\ 0 & \frac{1}{N} \end{bmatrix}} \therefore \text{Same as Table 4.1}$$