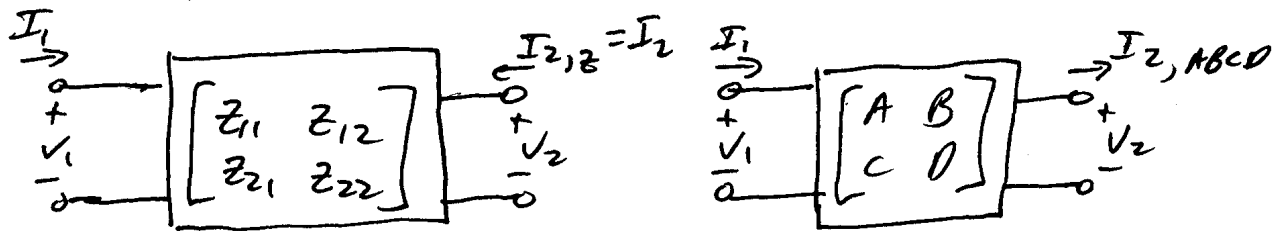


4.22 Derive expressions that give the impedance parameters in terms of the ABCD parameters.



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2, ABCD \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Per (4.28)

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} + Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} + Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

Per Text (pp. 190-191), $A = \frac{V_1}{V_2} \Big|_{I_2=0} + C = \frac{I_1}{V_2} \Big|_{I_2=0}$

$$\frac{A}{C} = \frac{V_1/V_2}{I_1/V_2} \Big|_{I_2=0} = \frac{V_1}{I_1} \Big|_{I_2=0} \Rightarrow \underline{\underline{Z_{11} = A/C}}$$

$$\frac{1}{C} = \frac{1}{\frac{I_1}{V_2}} \Big|_{I_2=0} = \frac{V_2}{I_1} \Big|_{I_2=0} \Rightarrow \underline{\underline{Z_{21} = 1/C}}$$

Multiply out [ABCD] matrices & set $I_1 = 0$

$$V_1 = A V_2 - B I_2 = A \frac{D}{C} I_2 - B I_2 \Rightarrow \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{AD}{C} - B = \underline{\underline{\frac{AD-BC}{C} = Z_{12}}}$$

$$I_1 = 0 = C V_2 - D I_2 \Rightarrow \frac{V_2}{I_2} \Big|_{I_1=0} = \underline{\underline{\frac{D}{C} = Z_{22}}}$$

$$\hookrightarrow C V_2 = D I_2$$

$$\hookrightarrow V_2 = \frac{D}{C} I_2 \text{ (Sub above)}$$

$$\boxed{[Z] = \begin{bmatrix} A/C & \frac{AD-BC}{C} \\ 1/C & D/C \end{bmatrix}}$$